



Introduction to Electronic Systems


Zheng Feng



Part 2

Dynamic Circuit Analysis

(DC+Dynamic/Resistive Element+Topology)

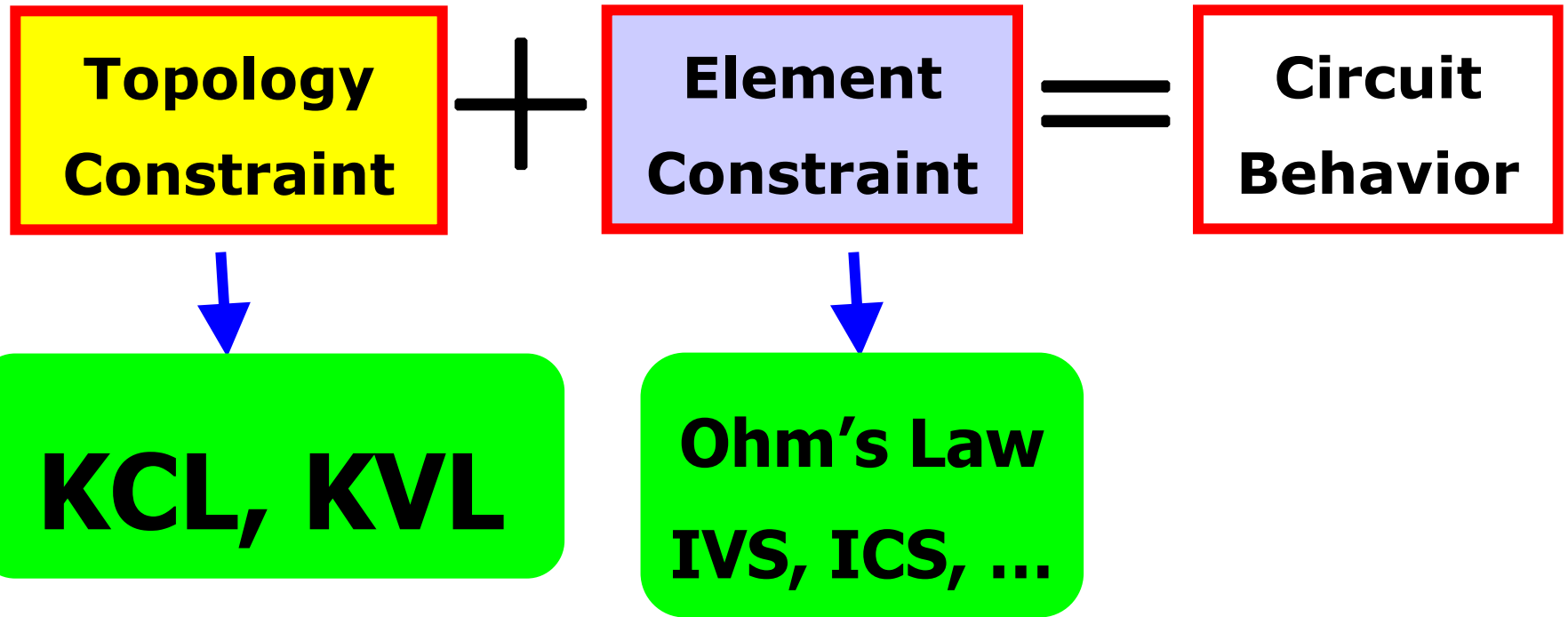

The VCR constraint for non-resistive element?



Part 2: Dynamic Circuit Analysis

5. Capacitors and Inductors

6. Response of First-order RC and RL Circuits


7. Response of Second-order RLC Circuits*




Chapter 5: Capacitors and Inductors

- **Capacitor and Capacitance**
- **Inductor and Inductance**
- **Dynamic Element and Circuit**


5-1 Capacitor and Capacitance

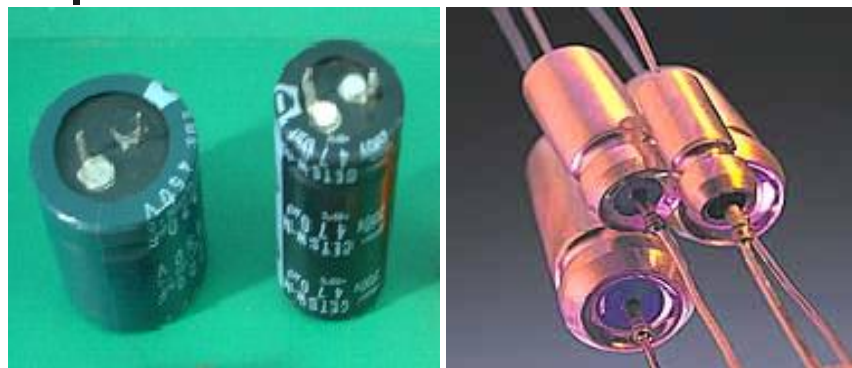

Electrolytic Capacitor

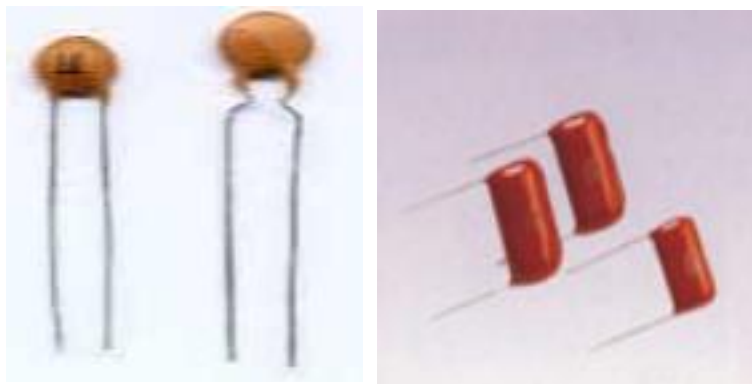


Ceramic Capacitor

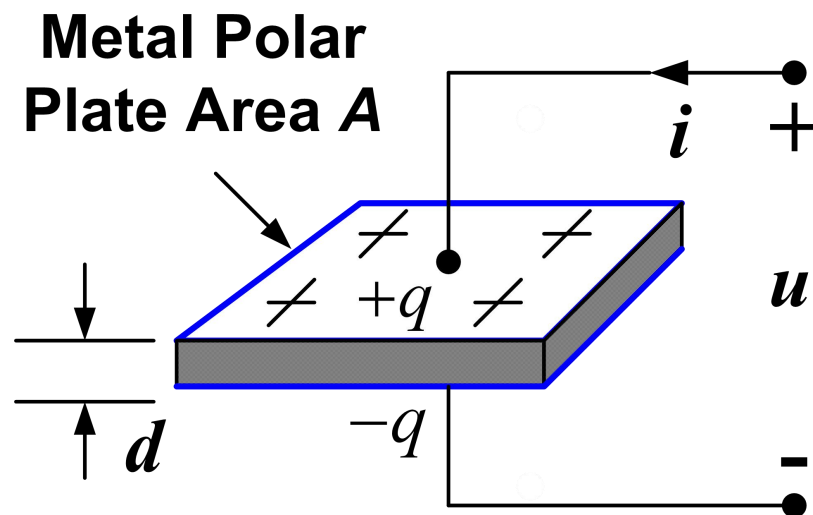

Capacitor and Capacitance

- Capacitor is a charge storing device;
- CVR of ideal capacitor:


$$q(t) = Cu(t)$$

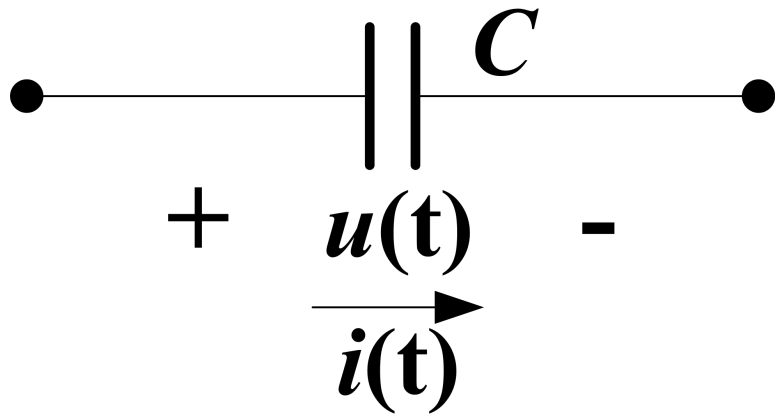


- Reference voltage and current defined with passive sign convention

VCR of Capacitors (1)

$$q(t) = Cu(t)$$

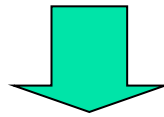
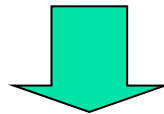
$$i(t) = \frac{dq(t)}{dt} = \frac{dCu(t)}{dt} = C \frac{du(t)}{dt}$$



$$i(t) = C \frac{du(t)}{dt}$$

VCR of Capacitors (2)

$i(t)$ is measured
in amperes

$u(t)$ in volts


$$i(t) = C \frac{du(t)}{dt}$$

C in farads

t in seconds


VCR of Capacitors (3)

$$i(t) = C \frac{du(t)}{dt}$$

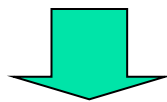

$$u(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = \frac{1}{C} \int_{-\infty}^{t_0} i(\tau) d\tau + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$

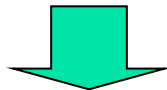
$$= u(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$



$$u(t) = u(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau \quad (t \geq t_0)$$

VCR of Capacitors (4)

$$i(t) = C \frac{du(t)}{dt}$$

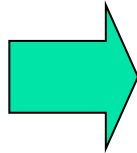


- $u(t)$ is continuous if $i(t)$ is limited;
- For DC, $i(t) = 0$, i.e., capacitor is open.

The voltage across a capacitor can not change abruptly in condition that *current* is limited.

VCR of Capacitors (5)
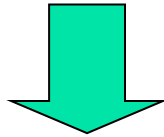
$$u(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$



- $u(t)$ is related to all “historical” current;
- Capacitor is a “Memorial” element;
- Dynamical element



Power and Energy

■ **Power:** $p(t) = u(t)i(t) = Cu(t)\frac{du(t)}{dt}$


■ **Energy:**

$$\begin{aligned} w(t) &= \int_{-\infty}^t p(\lambda) d\lambda \\ &= \int_{-\infty}^t Cu(\lambda) \frac{du(\lambda)}{d\lambda} d\lambda = \int_{-\infty}^t Cu(\lambda) du(\lambda) \\ &= \frac{1}{2} Cu^2(t) \Big|_{-\infty}^t = \frac{1}{2} Cu^2(t) \geq 0 \end{aligned}$$






Power and Energy

$$w(t) = \frac{1}{2} C u^2(t) \geq 0$$

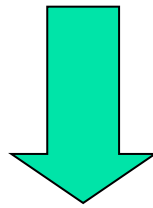

- **Capacitor is a passive element.**


Capacitors in Series

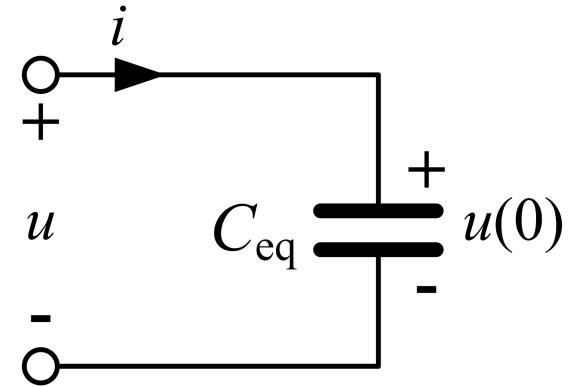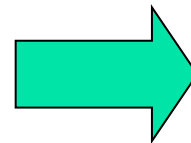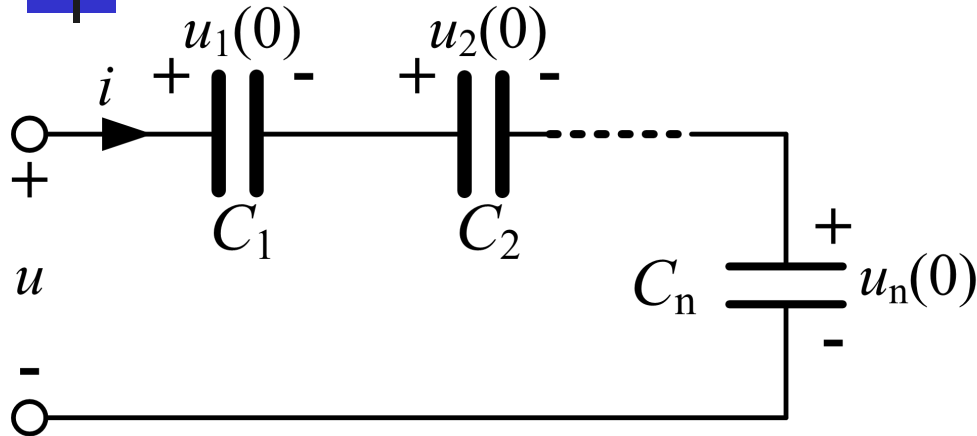

$$u(t) = \sum_{k=1}^n u_k(t)$$


$$= \sum_{k=1}^n u_k(0) + \int_0^t \left(\sum_{k=1}^n \frac{1}{C_k} \right) i(\tau) d\tau$$
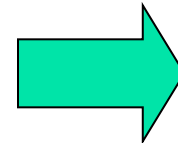
$$= u(0) + \int_0^t \frac{1}{C_{eq}} i(\tau) d\tau$$



$$\begin{cases} \frac{1}{C_{eq}} = \sum_{k=1}^n \left(\frac{1}{C_k} \right) \\ u(0) = \sum_{k=1}^n u_k(0) \end{cases}$$

Capacitors in Parallel

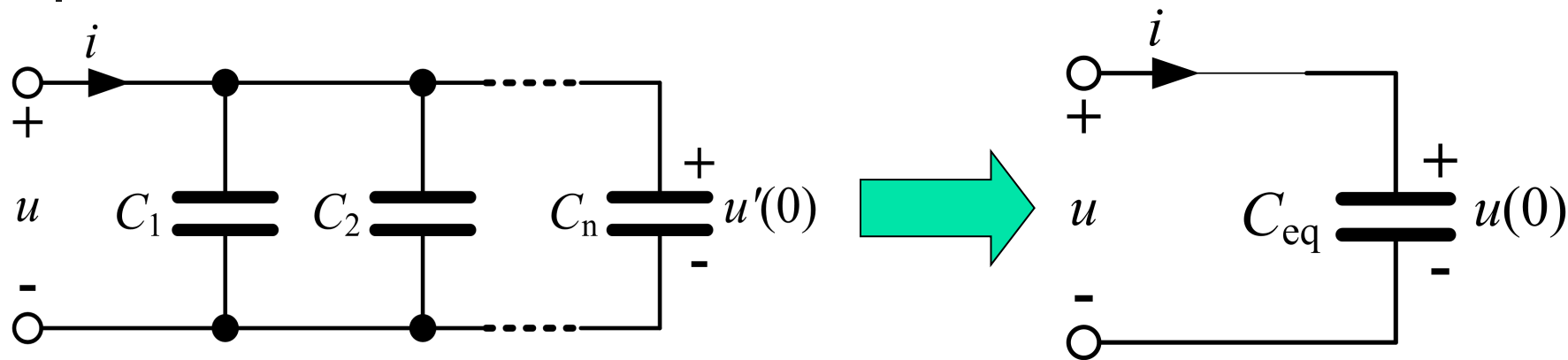

$$i(t) = \sum_{k=1}^n i_k(t)$$



$$= \left(\sum_{k=1}^n C_k \right) \frac{du(t)}{dt}$$

$$= C_{eq} \frac{du(t)}{dt}$$

$$\left\{ \begin{array}{l} C_{eq} = \sum_{k=1}^n C_k \\ u(0) = u_k(0) \end{array} \right.$$

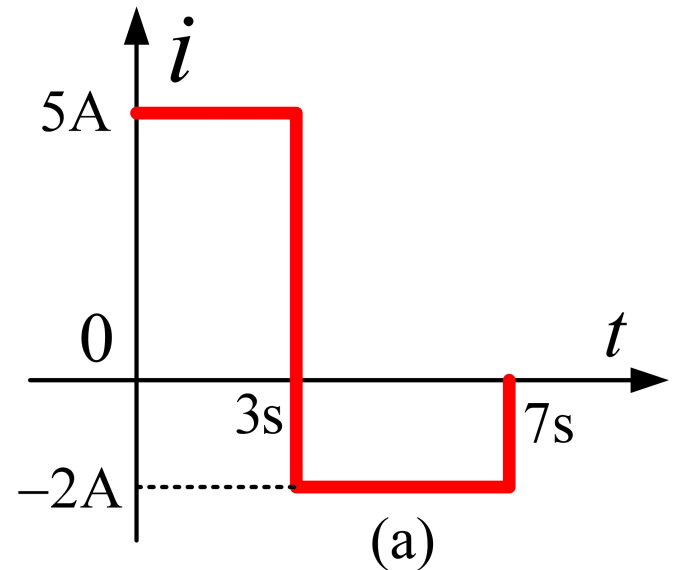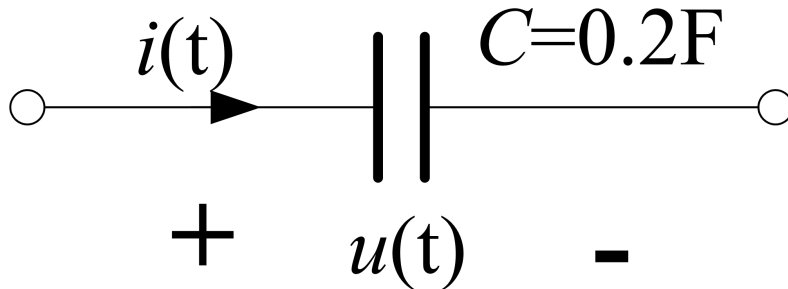Example

A capacitor current has a waveform as shown. The initial voltage $u(0)=30\text{V}$. Find the voltage on the capacitor.





Solution:

(1) $0 \leq t < 3\text{s} : i = 5\text{A} > 0$

$$u = u(0) + \frac{1}{C} \int_0^t i(\tau) d\tau$$

$$= 30 + \frac{1}{0.2} \int_0^t 5 d\tau = (30 + 25t) \text{ V}$$

$$u(t = 3\text{s}) = 30 + 25 \times 3 = 105 \text{ V}$$



(2) $3\text{s} \leq t < 7\text{s} : i = -2\text{A} < 0$

$$u = u(3) + \frac{1}{C} \int_3^t i(\tau) d\tau$$



$$= 105 + \frac{1}{0.2} \int_3^t (-2) d\tau = (135 - 10t) \text{ V}$$

$$u(t = 7\text{s}) = 65\text{V}$$





(3) $t \geq 7\text{s} : i = 0$

$$u(t) = u(7\text{s}) \\ = 65\text{V}$$

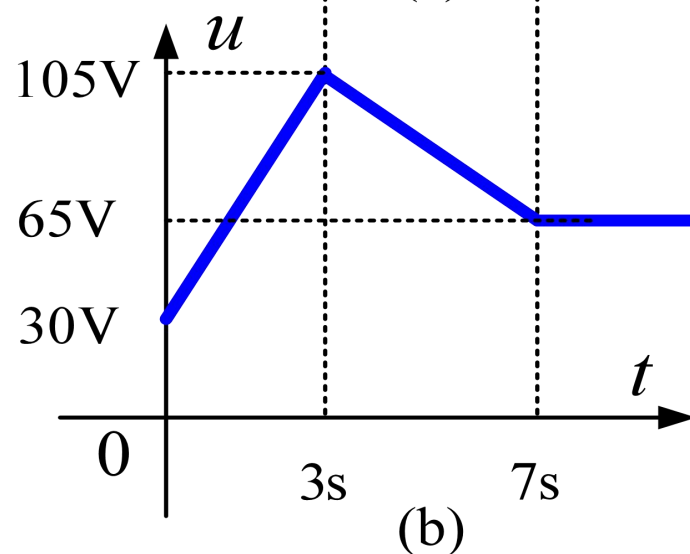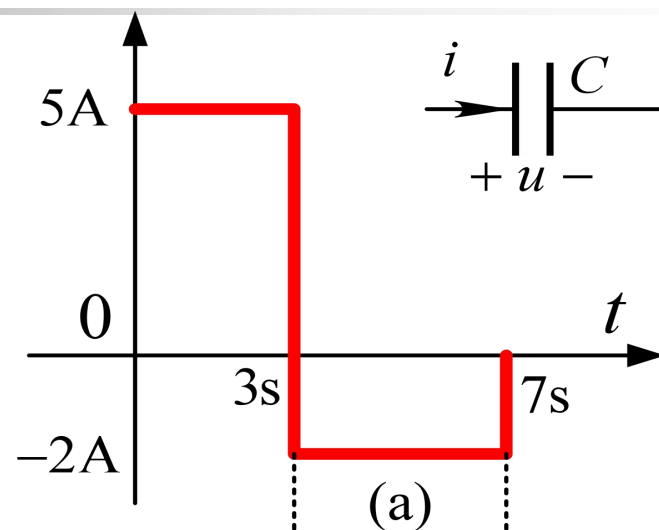

5-2 Inductor and Inductance

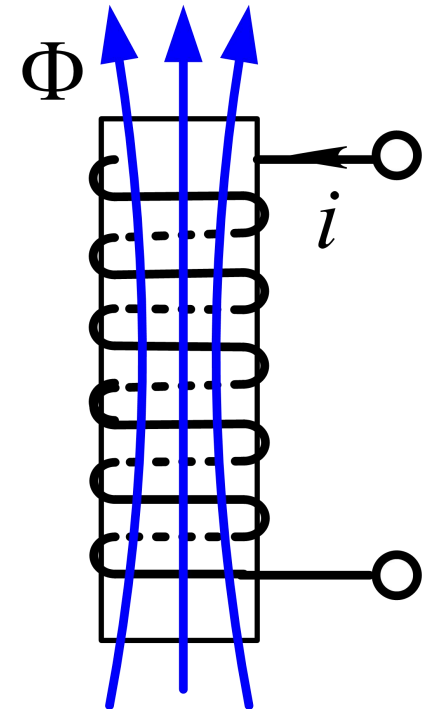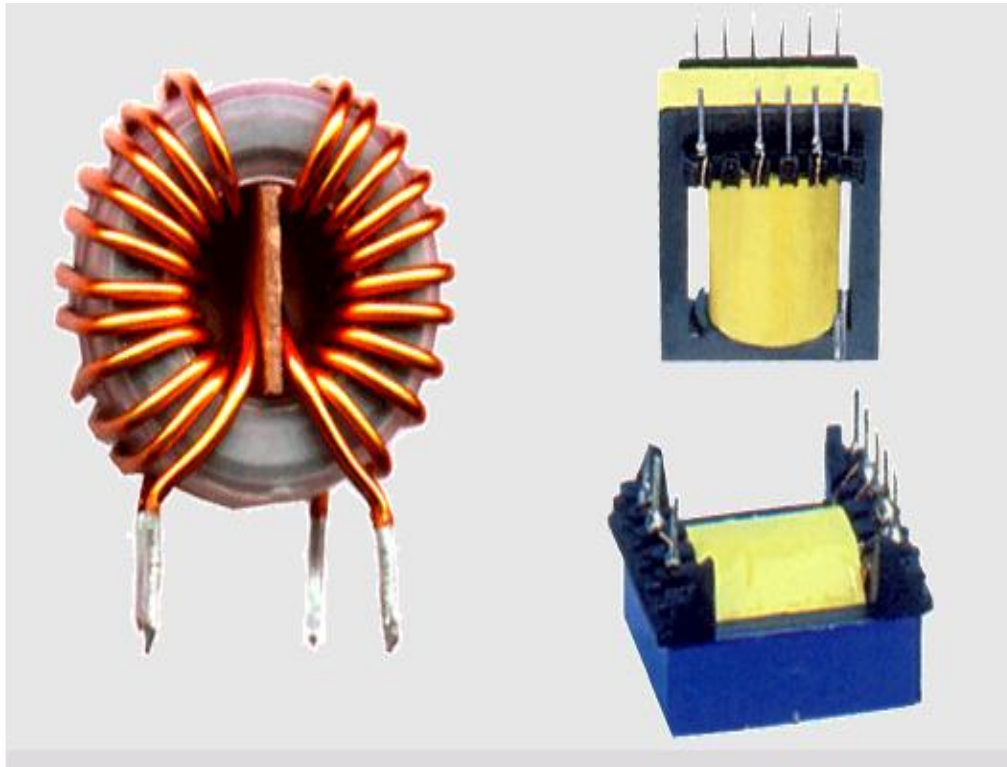


Examples of Real Inductors

Inductor and Inductance

- Inductor is a energy storing device;
- WCR of ideal Inductor:


$$\Psi(t) = Li(t)$$

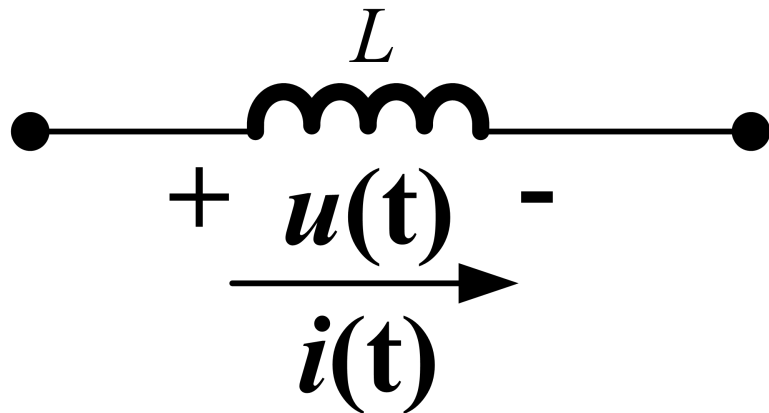


- Reference voltage and current defined with passive sign convention

VCR of Inductors (1)

$$\Psi(t) = Li(t)$$

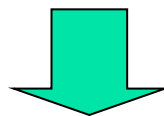
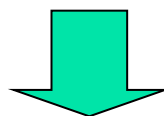
$$u(t) = \frac{d\Psi(t)}{dt} = \frac{dLi(t)}{dt} = L \frac{di(t)}{dt}$$



$$u(t) = L \frac{di(t)}{dt}$$

VCR of Inductors (2)

$u(t)$ is measured
in volts

$i(t)$ in amperes


$$u(t) = L \frac{di(t)}{dt}$$

L in henrys


t in seconds

VCR of Inductors (3)

$$u(t) = L \frac{di(t)}{dt}$$

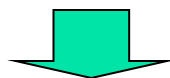

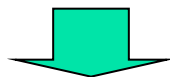
$$\begin{aligned} i(t) &= \frac{1}{L} \int_{-\infty}^t u(\tau) d\tau = \frac{1}{L} \int_{-\infty}^{t_0} u(\tau) d\tau + \frac{1}{L} \int_{t_0}^t u(\tau) d\tau \\ &= i(t_0) + \frac{1}{L} \int_{t_0}^t u(\tau) d\tau \end{aligned}$$



$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t u(\tau) d\tau \quad (t \geq t_0)$$

VCR of Inductors (4)

$$u(t) = L \frac{di(t)}{dt}$$

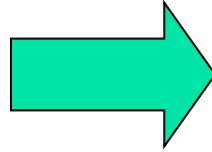


- $i(t)$ is continuous if $u(t)$ is limited;
- For DC, $u(t) = 0$, i.e., inductor is short.

The current through an inductor can not change abruptly in condition that *voltage* is limited.

VCR of Inductors (5)
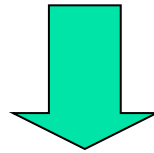
$$i(t) = \frac{1}{L} \int_{-\infty}^t u(\xi) d\xi$$



- $i(t)$ is related to all “historical” voltage;
- Inductor is a “Memorial” element;
- Dynamical element



Power and Energy

■ **Power:** $p(t) = u(t)i(t) = Li(t)\frac{di(t)}{dt}$


■ **Energy:**

$$\begin{aligned}w(t) &= \int_{-\infty}^t p(\lambda) d\lambda = \int_{-\infty}^t Li(\lambda) \frac{di(\lambda)}{d\lambda} d\lambda \\&= \int_{-\infty}^t Li(\lambda) di(\lambda) = \frac{1}{2} Li^2(t) - \frac{1}{2} Li^2(-\infty) \\&= \frac{1}{2} Li^2(t) \geq 0\end{aligned}$$






Power and Energy

$$w(t) = \frac{1}{2} L i^2(t) \geq 0$$

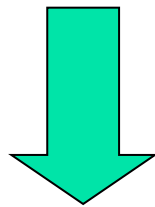


- Inductor is a passive element.

Inductors in Series

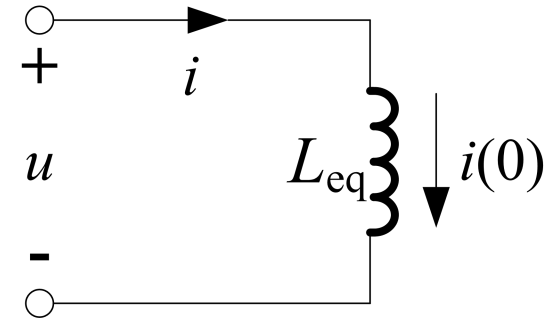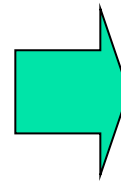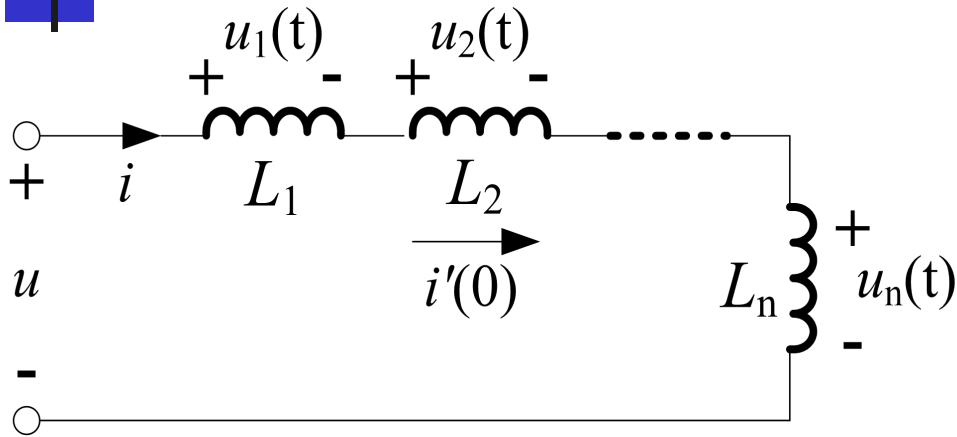

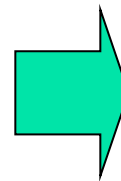
$$\begin{aligned}
 u(t) &= \sum_{k=1}^n u_k(t) \\
 &= \left(\sum_{k=1}^n L_k \right) \frac{di(t)}{dt} \\
 &= L_{eq} \frac{di(t)}{dt}
 \end{aligned}$$



$$\begin{cases} L_{eq} = \sum_{k=1}^n L_k \\ i(0) = i'(0) \end{cases}$$

Inductors in Parallel

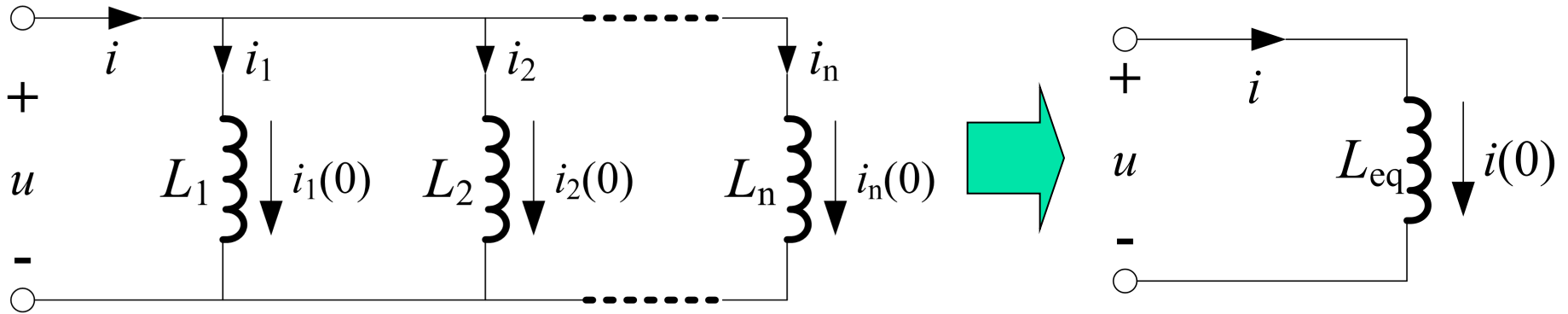

$$i(t) = \sum_{k=1}^n i_k(t)$$



$$= \sum_{k=1}^n i_k(0) + \int_0^t \left(\sum_{k=1}^n \frac{1}{L_k} \right) u(\xi) d\xi$$

$$= i(0) + \int_0^t \frac{1}{L_{eq}} u(\xi) d\xi$$

$$\Rightarrow \begin{cases} \frac{1}{L_{eq}} = \sum_{k=1}^n \left(\frac{1}{L_k} \right) \\ i(0) = \sum_{k=1}^n i_k(0) \end{cases}$$

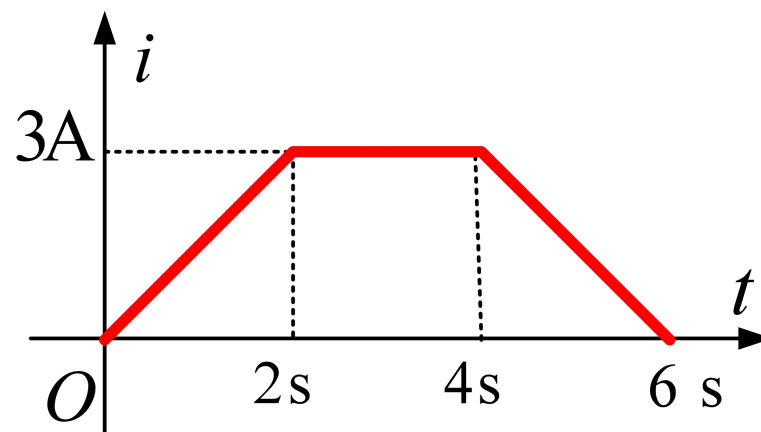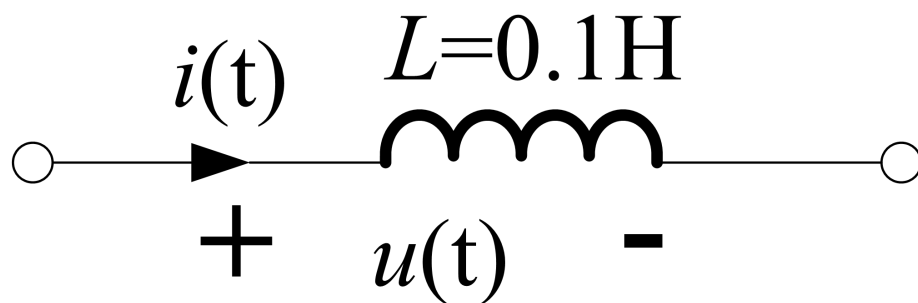Example

An inductor current has a waveform as shown.
Find the voltage, power, and energy for the inductor.






Solution:

(1) $0 < t < 2\text{s}: i = 1.5t \text{ A}$

$$u = L \frac{di}{dt} = (0.1 \times 1.5) \text{ V} = 0.15 \text{ V}$$

$$p = ui = 0.225t \text{ W}$$
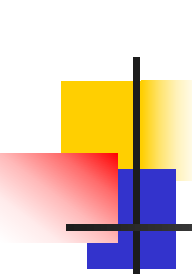
$$w_m = \frac{1}{2} Li^2 = 0.1125t^2 \text{ J}$$



(2) $2\text{s} < t < 4\text{s} : i = 3 \text{ A}$

$$u = L \frac{di}{dt} = 0$$

$$p = ui = 0$$

$$w_{\text{m}} = \frac{1}{2} Li^2 = 0.45 \text{ J}$$



(3) $4\text{s} < t < 6\text{s} : i = -1.5t + 9 \text{ A}$

$$u = L \frac{di}{dt} = -0.1 \times 1.5 \text{ V} = -0.15 \text{ V}$$

$$p = ui = (0.225t - 1.35) \text{ W}$$

$$w_m = \frac{1}{2} Li^2 = (0.1125t^2 - 1.35t + 4.05) \text{ J}$$




(3) $t > 6\text{s} : i = 0\text{ A}$

$$u = L \frac{di}{dt} = 0$$

$$p = ui = 0$$

$$w_m = \frac{1}{2} Li^2 = 0$$

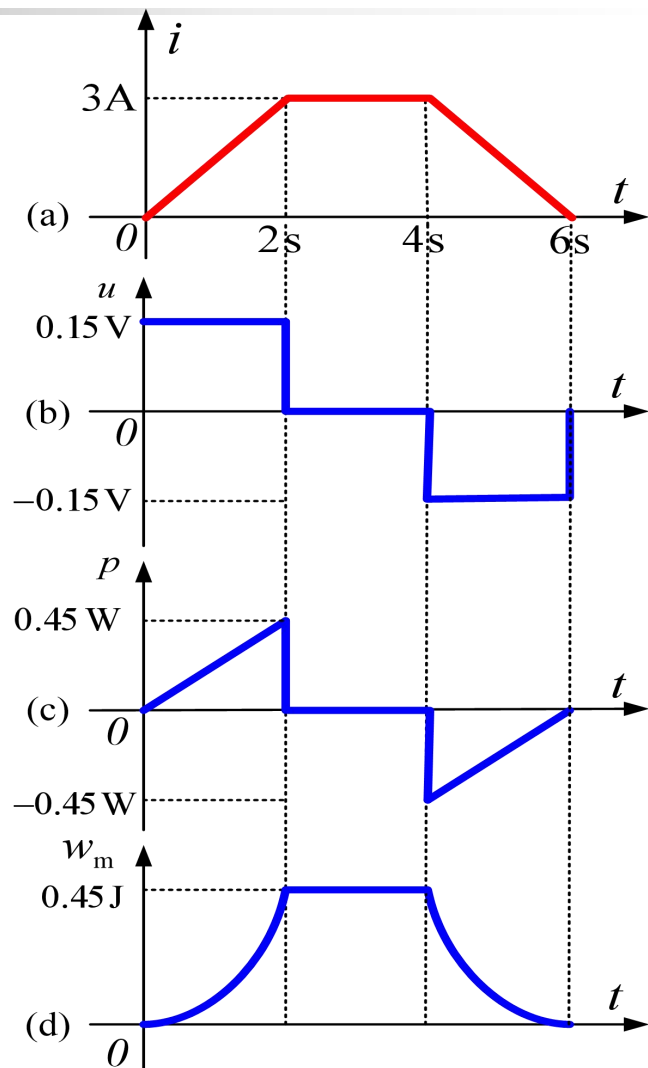

Summary of VCR for Passive Elements

Resistor: $u(t) = Ri(t)$

Capacitor:
$$\begin{cases} i(t) = C \frac{du(t)}{dt} \\ u(t) = u(t_0) + \frac{1}{C} \int_{t_0}^t i(\xi) d\xi \end{cases}$$

Memorize!!

Inductor:
$$\begin{cases} u(t) = L \frac{di(t)}{dt} \\ i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t u(\xi) d\xi \end{cases}$$

Summary of Equations for Series

Resistor: $R_{eq} = \sum_{k=1}^N R_k$

Capacitor:
$$\begin{cases} \frac{1}{C_{eq}} = \sum_{k=1}^n \left(\frac{1}{C_k} \right) \\ u(0) = \sum_{k=1}^n u_k(0) \end{cases}$$

Inductor:
$$\begin{cases} L_{eq} = \sum_{k=1}^n L_k \\ i(0) = i'(0) \end{cases}$$

Memorize!!

Summary of Equations for Parallel

Resistor: $\frac{1}{R_{eq}} = \sum_{k=1}^N \frac{1}{R_k}$

Capacitor: $\begin{cases} C_{eq} = \sum_{k=1}^n C_k \\ u(0) = u'(0) \end{cases}$

Inductor: $\begin{cases} \frac{1}{L_{eq}} = \sum_{k=1}^n \left(\frac{1}{L_k} \right) \\ i(0) = \sum_{k=1}^n i_k(0) \end{cases}$

Memorize!!



5-3 Dynamic Element and Circuit

- **Dynamic element**
- **Dynamic circuit**



Dynamic Element

■ Resistor:

- VCR of terminals is a linear algebraic equation;
- VCR is “instantaneous” or “memoryless”;
- Static element.



Dynamic Element

■ Capacitor and Inductor:

- VCR is a differential or integral equation;
- VCR is “historical” or “memorial”;
- Dynamic elements.



Dynamic Circuit

■ Dynamic circuits:

- contain at least one dynamic element;
- are described by differential equations;
- are “historical” or “memorial”.



Summary of Chapter 5

- **VCR of capacitor**
- **VCR of inductor**
- **Power/energy for capacitors/inductors**
- **Capacitors/inductors in series and parallel**
- **Conception of dynamic element and circuit**