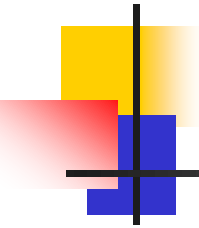




Introduction to Electronic Systems

Zheng Feng



Part 3

Sinusoidal Steady-State Analysis

(AC+Dynamic/Resistive Element+Topology)



Part 3: Sinusoidal Steady-State Analysis

8. Sinusoidal Steady-State Analysis

9. Sinusoidal Steady-State Power Calculations

10. Frequency Selective Circuits *



Chapter 8 (1)

- **Complex Number Review**
- **Sinusoidal Source**
- **Sinusoidal Response**
- **The Phasor**
- **VCR of Passive Elements in
Frequency Domain**



Chapter 8 (2)

- **KCL and KVL in Frequency Domain**
- **Mesh-Current Method**
- **Node-Voltage Method**
- **Source Transformation**
- **Superposition Theorem**
- **Thévenin and Norton Equivalents**



8-1 Complex Number Review

- **Mathematic Representations of Complex Number**
- **Basic Operations of Complex Number**



Mathematic Representations

- **Algebraic Representation**
- **Geometric Representation**
- **Trigonometric Form**
- **Exponential Form**
- **Polar Form**



Algebraic Representation

$$z = a + jb$$


$$z^* = a - jb$$

$$a = \operatorname{Re}[z] : \text{Real part} \quad b = \operatorname{Im}[z] : \text{Imaginary part}$$

$$r = |z| = \sqrt{a^2 + b^2} : \text{Modulus} \quad \varphi = \arctan \frac{b}{a} : \text{Phase}$$

$$j = \sqrt{-1} : \text{Imaginary unit}$$


Geometric Representation

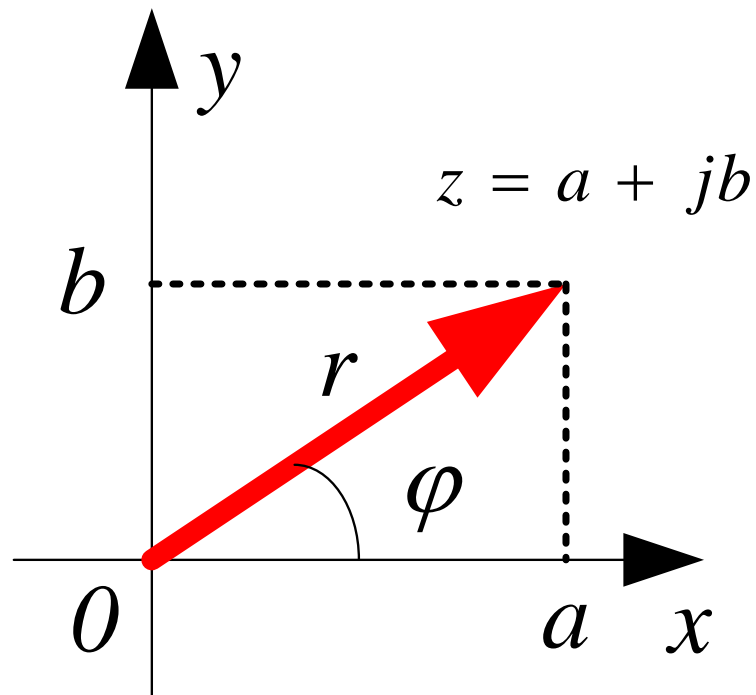


**Representation of complex
number on the complex plane**

Trigonometric Representation

$$z = a + jb$$

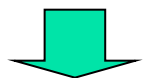
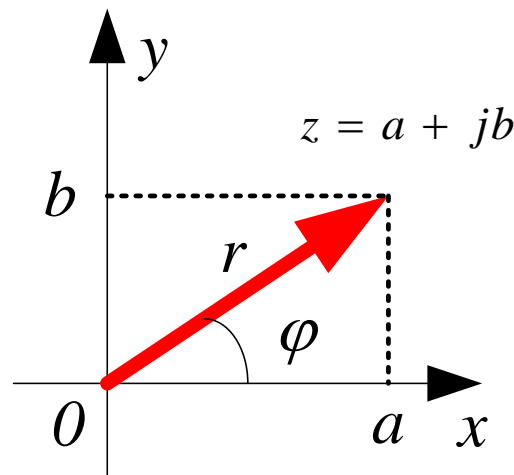
$$\begin{cases} a = r \cos \varphi \\ b = r \sin \varphi \end{cases}$$



$$z = a + jb$$

$$= r \cos \varphi + jr \sin \varphi$$

$$= r (\cos \varphi + j \sin \varphi)$$

$$\begin{cases} r = |z| = \sqrt{a^2 + b^2} \\ \varphi = \arctan \frac{b}{a} \end{cases}$$



Exponential Form

■ **Euler's formula**
$$\begin{cases} e^{j\varphi} = \cos \varphi + j \sin \varphi \\ e^{-j\varphi} = \cos \varphi - j \sin \varphi \end{cases}$$

$$z = r(\cos \varphi + j \sin \varphi)$$

$$= re^{j\varphi}$$

**Exponential Form**




Polar Form

$$z = r(\cos \varphi + j \sin \varphi)$$

$$= re^{j\varphi}$$

$$= r \angle \varphi$$

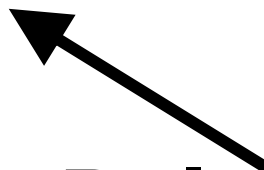

Polar Form



Basic Operations of Complex Number

- **Addition and Subtraction**
- **Multiplication**
- **Division**



Addition and Subtraction Operation

If $z_1 = a_1 + jb_1$ $z_2 = a_2 + jb_2$

Then $z_1 \pm z_2 = (a_1 + jb_1) \pm (a_2 + jb_2)$
 $= (a_1 \pm a_2) + j(b_1 \pm b_2)$

$$z_1 = z_2 \longleftrightarrow \begin{cases} a_1 = a_2 \\ b_1 = b_2 \end{cases}$$



Multiplication Operation

If $z_1 = a_1 + jb_1$ $z_2 = a_2 + jb_2$

$$\begin{aligned} z_1 \cdot z_2 &= (a_1 + jb_1) \cdot (a_2 + jb_2) = a_1a_2 + jb_1a_2 + ja_1b_2 + j^2b_1b_2 \\ &= (a_1a_2 - b_1b_2) + j(b_1a_2 + a_1b_2) \end{aligned}$$

$$\begin{aligned} z_1 \cdot z_2 &= r_1 (\cos \varphi_1 + j \sin \varphi_1) \cdot r_2 (\cos \varphi_2 + j \sin \varphi_2) \\ &= r_1 r_2 [\cos(\varphi_1 + \varphi_2) + j \sin(\varphi_1 + \varphi_2)] \end{aligned}$$

Specially,

$$j^2 = -1, \quad j^3 = -j, \quad j^4 = 1, \quad j^5 = j, \quad \dots$$



If $z_1 = r_1 e^{j\varphi_1}$ $z_2 = r_2 e^{j\varphi_2}$

Then $z_1 \cdot z_2 = r_1 e^{j\varphi_1} \cdot r_2 e^{j\varphi_2} = r_1 r_2 e^{j(\varphi_1 + \varphi_2)}$

If $z_1 = r_1 \angle \varphi_1$ $z_2 = r_2 \angle \varphi_2$

Then $z_1 \cdot z_2 = r_1 \angle \varphi_1 \cdot r_2 \angle \varphi_2 = r_1 r_2 \angle \varphi_1 + \varphi_2$


$$z \cdot z^* = (a + jb) \cdot (a - jb) = a^2 + b^2 = r^2$$



Division of Complex Number

If $z_1 = a_1 + jb_1$ $z_2 = a_2 + jb_2$

Then
$$\frac{z_1}{z_2} = \frac{a_1 + jb_1}{a_2 + jb_2} = \frac{(a_1 + jb_1) \cdot (a_2 - jb_2)}{(a_2 + jb_2) \cdot (a_2 - jb_2)}$$
$$= \frac{a_1a_2 + b_1b_2}{a_2^2 + b_2^2} + j \frac{b_1a_2 - a_1b_2}{a_2^2 + b_2^2}$$



If $z_1 = r_1 e^{j\varphi_1}$ $z_2 = r_2 e^{j\varphi_2}$


Then $\frac{z_1}{z_2} = \frac{r_1 e^{j\varphi_1}}{r_2 e^{j\varphi_2}} = \frac{r_1}{r_2} e^{j(\varphi_1 - \varphi_2)}$

If $z_1 = r_1 \angle \varphi_1$ $z_2 = r_2 \angle \varphi_2$

Then $\frac{z_1}{z_2} = \frac{r_1 \angle \varphi_1}{r_2 \angle \varphi_2} = \frac{r_1}{r_2} \angle \varphi_1 - \varphi_2$

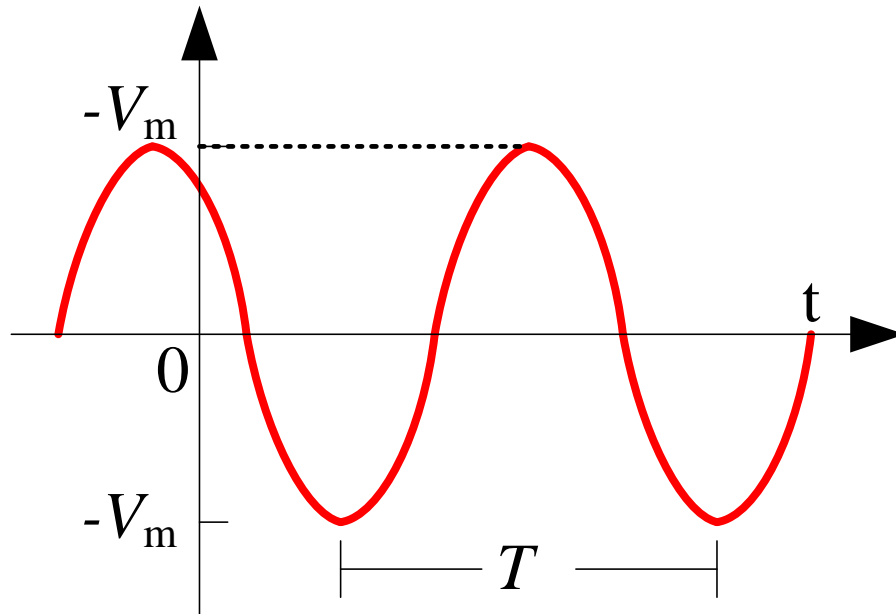8-2 Sinusoidal Source

- **Sinusoidal Voltage/Current Source:**
Voltage/Current varies sinusoidally with time.



**Alternative
Current (AC)**



Parameters of Sinusoidal Function

$$v(t) = V_m \cos(\omega t + \phi)$$




ϕ : Initial phase angle determines the value at $t = 0$.

ω : Angular frequency determines the rate
varying with time.

V_m : Amplitude determines the maximum value.

Phase Angle

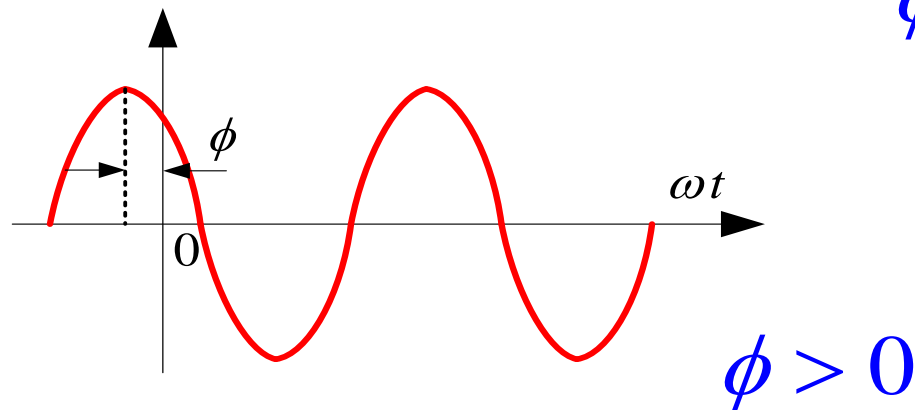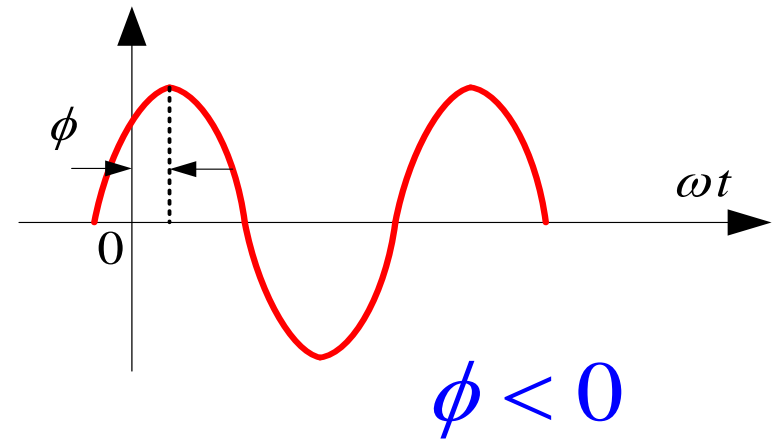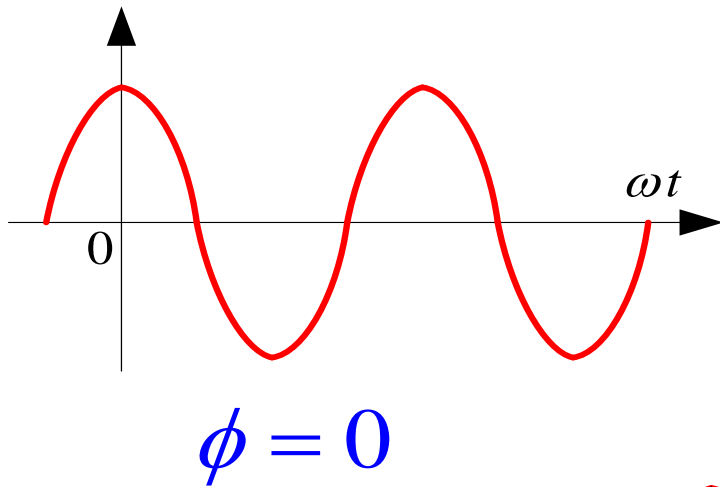ϕ : Initial phase angle determines the value at $t=0$.






Angular Frequency

$$\omega = 2\pi f = \frac{2\pi}{T} \quad : \text{measured in radians/second}$$

$$f = \frac{1}{T} \quad : \text{measured in hertz (Hz)}$$

$$T \quad : \text{measured in seconds}$$

8-3 Sinusoidal Response

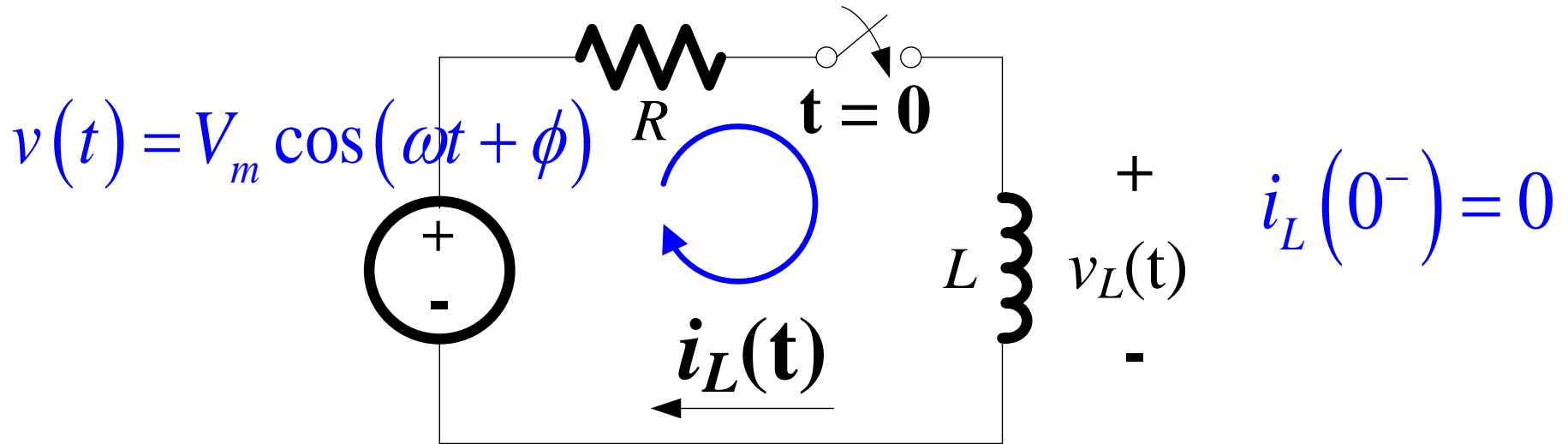

- The initial current of the inductor is zero.
- The switch is closed at $t = 0$;
- Find the inductive current.



Solution:

■ By KVL for the loop: $L \frac{di_L}{dt} + Ri_L = V_m \cos(\omega t + \phi)$

$$i_L(t) = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-(R/L)t} \\ + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

in which, $\theta = \arctan(\omega L/R)$



Sinusoidal Response

$$i_L(t) = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-(R/L)t} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$



**Transient
Response**



**Steady State
Response**

- The transient response becomes infinitesimal as time elapses;
- The steady state response exists as long as the source continues to supply the voltage.



Sinusoidal Response

- The transient response becomes infinitesimal as time elapses;
- The steady state response exists as long as the source continues to supply the voltage;
- Because the transient response vanishes as time elapses, the steady state response must also satisfy the differential equation.



Steady State Response

- In a linear circuit driven by sinusoidal sources, the steady state response is also a sinusoidal function;
- The frequency of the steady state response is identical to the frequency of the sinusoidal source;
- The amplitude and phase angle differ from those of the sinusoidal source.



Steady State Response

- We focus on the steady state response in this chapter;
- Is there any method for calculating the steady state response without solving the differential equation?
- If yes, what is it?



8-4 Phasors

■ Euler's formula: $e^{j\varphi} = \cos \varphi + j \sin \varphi$

$$\cos \varphi = \operatorname{Re} \left[e^{j\varphi} \right]$$



$$\begin{aligned} V_m \cos(\omega t + \phi) &= \operatorname{Re} \left[V_m e^{j(\omega t + \phi)} \right] \\ &= \operatorname{Re} \left[\color{blue}{V_m} e^{j\phi} e^{j\omega t} \right] \end{aligned}$$



Phasor

$$V_m \cos(\omega t + \phi) = \operatorname{Re} \left[V_m e^{j\phi} e^{j\omega t} \right]$$

$$V_m \cos(\omega t + \phi) \xrightarrow{\quad} \hat{V} = V_m e^{j\phi}$$

 **Sinusoidal Voltage**  **Phasor**

$$\hat{V} = V_m e^{j\phi} = V_m \angle \phi = V_m (\cos \phi + j \sin \phi)$$

(Inverse) Phasor Transform

■ Phasor Transform

$$V_m \cos(\omega t + \phi) \longrightarrow \hat{V} = V_m e^{j\phi}$$

$$P[V_m \cos(\omega t + \phi)] = V_m e^{j\phi} = \hat{V}$$


■ Inverse Phasor Transform

$$V_m \cos(\omega t + \phi) \longleftarrow \hat{V} = V_m e^{j\phi}$$

$$P^{-1}[\hat{V} = V_m e^{j\phi}] = V_m \cos(\omega t + \phi)$$

Phasor Diagram
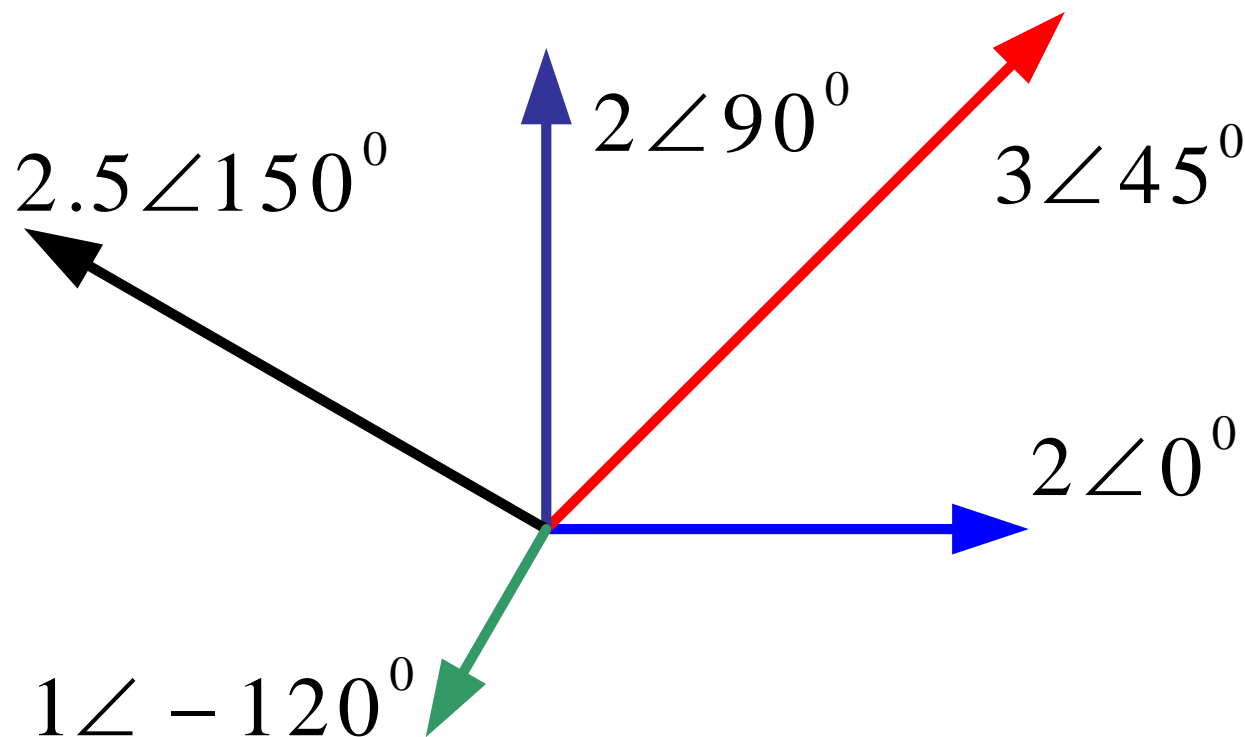
$$\hat{V} = V_m e^{j\phi} = V_m \angle \phi = V_m \cos \phi + jV_m \sin \phi$$





Phasor Transform

- A phasor is a complex number;
- A phasor represents a sinusoidal function, and shows up as the coefficient of $e^{j\omega t}$;
- A phasor has two elements: Amplitude and Phase angle;
- Phasor transform transfers the sinusoidal function from time domain to phasor domain, which is also called **frequency domain**.



Example

$$v(t) = 5 \cos(100\pi t + 30^\circ)$$

$$\hat{V} = P\left[5 \cos(100\pi t + 30^\circ)\right] = P\left[\operatorname{Re}\left(5e^{j30^\circ} e^{j100\pi t}\right)\right]$$

$$= 5e^{j30^\circ} = 5\angle 30^\circ$$

$$= 5\left(\cos 30^\circ + j \sin 30^\circ\right) = \frac{5\sqrt{3}}{2} + j\frac{5}{2}$$



Example

$$v(t) = 5 \cos(500\pi t + 30^\circ)$$

$$\hat{V} = P\left[5 \cos(500\pi t + 30^\circ)\right] = P\left[\operatorname{Re}\left(5e^{j30^\circ} e^{j500\pi t}\right)\right]$$

$$= 5e^{j30^\circ} = 5\angle 30^\circ$$

$$= 5\left(\cos 30^\circ + j \sin 30^\circ\right) = \frac{5\sqrt{3}}{2} + j \frac{5}{2}$$



Example

$$i(t) = -7 \sin(100\pi t + 30^\circ)$$

$$\hat{I} = P[-7 \sin(100\pi t + 30^\circ)] = P[7 \cos(100\pi t + 30^\circ + 90^\circ)]$$

$$= P[7 \cos(100\pi t + 120^\circ)] = P[\operatorname{Re}(7e^{j120^\circ} e^{j100\pi t})]$$

$$= 7e^{j120^\circ} = 7 \angle 120^\circ$$

$$= 7(\cos 120^\circ + j \sin 120^\circ) = -\frac{7}{2} + j \frac{7\sqrt{3}}{2}$$



Inverse Phasor Transform

- Phasor is **NOT** equal to sinusoidal function.
- A sinusoidal voltage/current can **NOT** be completely determined by a phasor;
- Sinusoidal voltage/current is determined by both a phasor and corresponding radian angular frequency.

$$\hat{V} = V_m e^{j\phi} \longleftrightarrow v(t) = \operatorname{Re} \left[V_m e^{j\phi} e^{j\omega t} \right] = V_m \cos(\omega t + \phi)$$



Example

$$f = 50\text{Hz}, \quad \hat{V} = 50\angle -30^\circ \text{V}$$

$$\omega = 2\pi f = 2\pi \times 50\text{Hz} = 100\pi \text{ (rad/s)}$$

$$\begin{aligned} v(t) &= P^{-1} \left[50\angle -30^\circ \right] = \text{Re} \left[50e^{j\phi} e^{j\omega t} \right] \\ &= \text{Re} \left[50e^{j(-30^\circ)} e^{j100\pi t} \right] = 50 \cos(100\pi t - 30^\circ) \text{V} \end{aligned}$$



Example

$$f = 100\text{Hz}, \quad \hat{V} = 50\angle -30^\circ \text{V}$$

$$\omega = 2\pi f = 2\pi \times 100\text{Hz} = 200\pi \text{ (rad/s)}$$

$$\begin{aligned} v(t) &= P^{-1} \left[50\angle -30^\circ \right] = \text{Re} \left[50e^{j(-30^\circ)} e^{j200\pi t} \right] \\ &= 50 \cos(200\pi t - 30^\circ) \text{V} \end{aligned}$$



Basic Operation of Phasors

- **Addition and Subtraction Operation**
- **Differential Operation**
- **Integral Operation**



Addition and Subtraction

If $v_n(t) = V_{mn} \cos(\omega t + \phi_n)$

Then
$$P\left[\sum_{n=1}^N v_n(t)\right] = \sum_{n=1}^N P[v_n(t)]$$



Proof:

$$\begin{aligned}\sum_{n=1}^N v_n(t) &= \sum_{n=1}^N V_{mn} \cos(\omega t + \phi_n) \\&= \sum_{n=1}^N \operatorname{Re} \left[\mathbf{V}_{mn} e^{j\phi_n} e^{j\omega t} \right] = \operatorname{Re} \left\{ \sum_{n=1}^N \left[V_{mn} e^{j\phi_n} e^{j\omega t} \right] \right\} \\&= \operatorname{Re} \left\{ \left[\sum_{n=1}^N V_{mn} e^{j\phi_n} \right] e^{j\omega t} \right\} = \operatorname{Re} \left\{ \sum_{n=1}^N P \left[\mathbf{v}_n(t) \right] e^{j\omega t} \right\}\end{aligned}$$



Differential Operation

If $v(t) = V_m \cos(\omega t + \phi)$

Then $P\left[\frac{dv(t)}{dt}\right] = j\omega P[v(t)]$



Proof:

$$\begin{aligned}\frac{dv(t)}{dt} &= \frac{d[V_m \cos(\omega t + \phi)]}{dt} = \frac{d\left\{\operatorname{Re}\left[V_m e^{j\phi} e^{j\omega t}\right]\right\}}{dt} \\&= \operatorname{Re}\left[\frac{d(V_m e^{j\phi} e^{j\omega t})}{dt}\right] = \operatorname{Re}\left[V_m e^{j\phi} \frac{d(e^{j\omega t})}{dt}\right] \\&= \operatorname{Re}\left[V_m e^{j\phi} (j\omega e^{j\omega t})\right] = \operatorname{Re}\left[j\omega V_m e^{j\phi} e^{j\omega t}\right] \\&= \operatorname{Re}\left[j\omega \hat{V} e^{j\omega t}\right]\end{aligned}$$



Integral Operation

If $v(t) = V_m \cos(\omega t + \phi)$

Then $P\left[\int v(t) dt\right] = \frac{1}{j\omega} P[v(t)]$



Proof:

$$\begin{aligned}\int v(t) dt &= \int V_m \cos(\omega t + \phi) dt = \int \operatorname{Re} \left[V_m e^{j\phi} e^{j\omega t} \right] dt \\&= \operatorname{Re} \left[\int V_m e^{j\phi} e^{j\omega t} dt \right] = \operatorname{Re} \left[V_m e^{j\phi} \int e^{j\omega t} dt \right] \\&= \operatorname{Re} \left[V_m e^{j\phi} \cdot \frac{1}{j\omega} e^{j\omega t} \right] = \operatorname{Re} \left[\frac{1}{j\omega} V_m e^{j\phi} e^{j\omega t} \right] \\&= \operatorname{Re} \left[\frac{1}{j\omega} \hat{V} e^{j\omega t} \right]\end{aligned}$$



8-5 VCR of Passive Elements

- **VCR of Resistor in Phasors**
- **VCR of Capacitor in Phasors**
- **VCR of Inductor in Phasors**

VCR of Resistor in Phasors


$$i(t) = I_m \cos(\omega t + \phi) \quad \bullet \xrightarrow{i(t)} \text{---} \underset{+ \quad v(t) \quad -}{\text{---} R \text{---}} \bullet$$

$$v(t) = RI_m \cos(\omega t + \phi)$$

$$= R \cdot \text{Re} \left[I_m e^{j\phi} e^{j\omega t} \right] = \text{Re} \left[R \cdot \hat{I} e^{j\omega t} \right]$$

$$\hat{V} = R \cdot \hat{I}$$


VCR of Resistor in Phasors

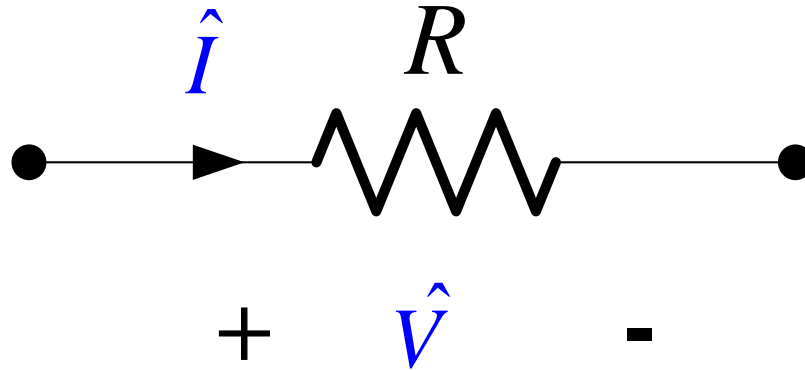

$$\hat{V} = R \cdot \hat{I}$$

VCR of Resistors in Phasor

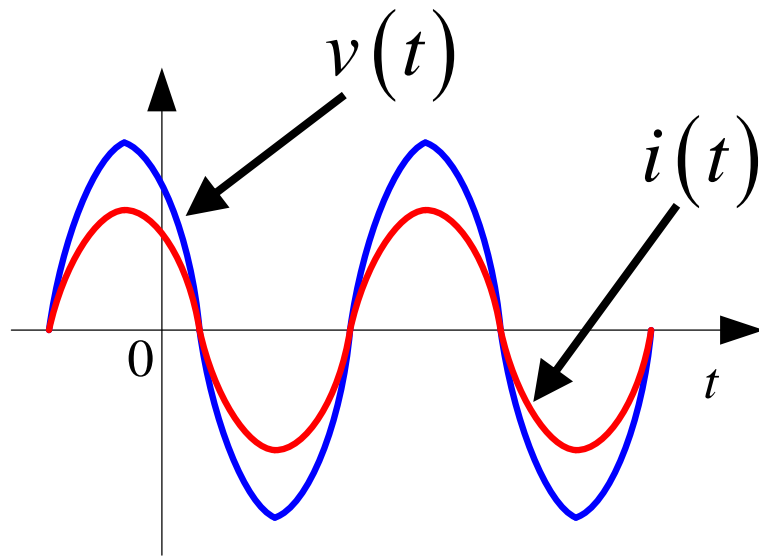
$$\begin{aligned} v(t) &= \operatorname{Re} \left[R \cdot \hat{I} e^{j\omega t} \right] \\ &= \operatorname{Re} \left[R \cdot I_m e^{j\phi} e^{j\omega t} \right] = \operatorname{Re} \left[V_m e^{j\phi} e^{j\omega t} \right] \end{aligned}$$



■ For resistor, $v(t)$ and $i(t)$ are **in phase**.

VCR of Capacitors in Phasor

$$v(t) = V_m \cos(\omega t + \phi)$$

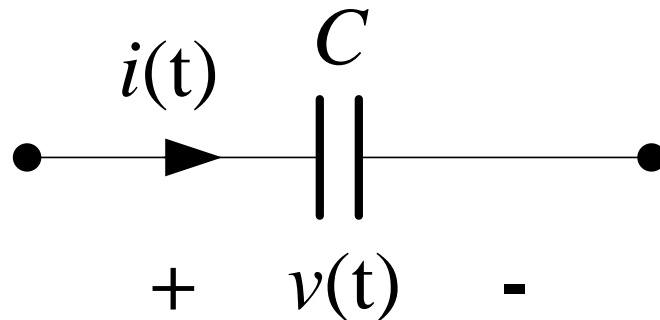


$$i(t) = C \frac{dv}{dt} = \omega C V_m \cos(\omega t + \phi + 90^\circ)$$

$$= \text{Re} \left[\omega C V_m e^{j(\phi + 90^\circ)} e^{j\omega t} \right] = \text{Re} \left[\omega C V_m e^{j\phi} e^{j90^\circ} e^{j\omega t} \right]$$

$$= \text{Re} \left[j\omega C V_m e^{j\phi} e^{j\omega t} \right] = \text{Re} \left[j\omega C \hat{V} e^{j\omega t} \right]$$

$$= \text{Re} \left[\hat{I} e^{j\omega t} \right]$$

VCR of Capacitors in Phasor

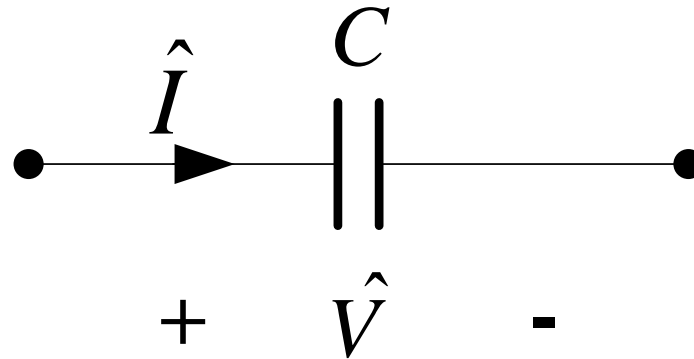


$$\hat{V} = \frac{1}{j\omega C} \hat{I}$$

VCR of Capacitors in

Phasor

$$i(t) = \text{Re} \left[\hat{I} e^{j\omega t} \right] = \text{Re} \left[j\omega C \hat{V} e^{j\omega t} \right] = \text{Re} \left[\omega C V_m e^{j(\phi+90^\circ)} e^{j\omega t} \right]$$

$$v(t) = V_m \cos(\omega t + \phi)$$

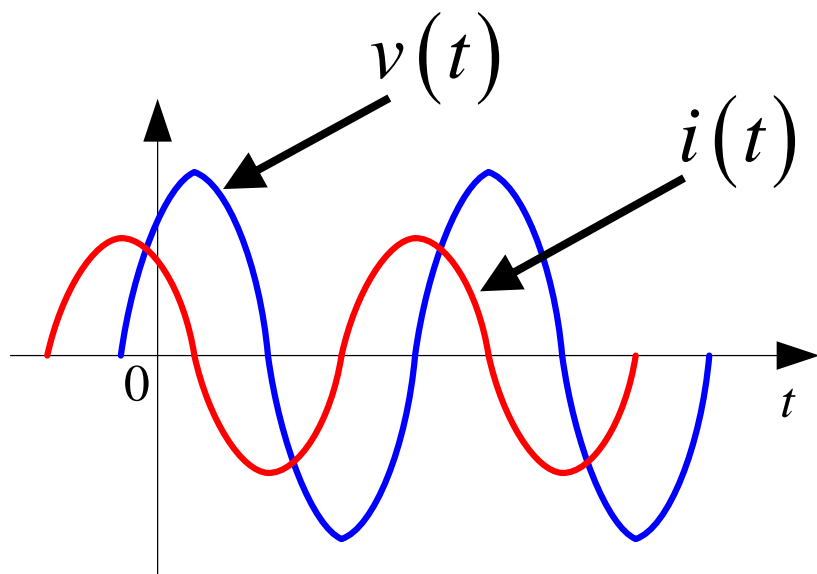

■ **For capacitor,**
 $v(t)$ lags $i(t)$
by 90° .

VCR of Inductors in Phasor

$$i(t) = I_m \cos(\omega t + \phi) \quad \bullet \xrightarrow{i(t)} \text{---} \overset{L}{\text{---}} \text{---} \bullet$$

$+ \quad v(t) \quad -$


$$v(t) = L \frac{di}{dt} = \omega L I_m \cos(\omega t + \phi + 90^\circ)$$

$$= \text{Re} \left[\omega L I_m e^{j(\phi + 90^\circ)} e^{j\omega t} \right]$$

$$= \text{Re} \left[\omega L I_m e^{j\phi} e^{j90^\circ} e^{j\omega t} \right] = \text{Re} \left[j\omega L I_m e^{j\phi} e^{j\omega t} \right]$$

$$= \text{Re} \left[j\omega L \hat{I} e^{j\omega t} \right] = \text{Re} \left[\hat{V} e^{j\omega t} \right]$$

VCR of Inductors in Phasor

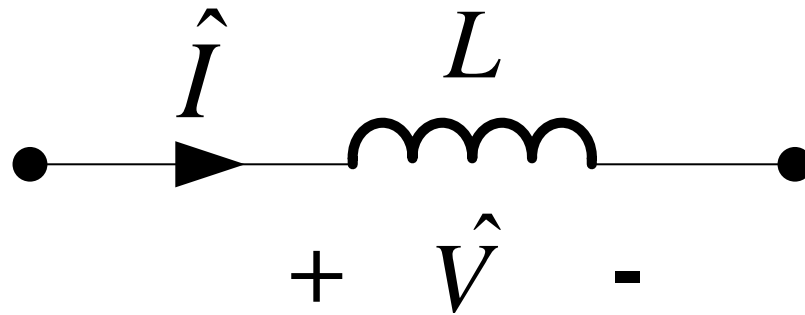


$$\hat{V} = j\omega L \hat{I}$$

VCR of Inductors in Phasor

$$v(t) = \operatorname{Re} \left[\hat{V} e^{j\omega t} \right] = \operatorname{Re} \left[j\omega L I_m e^{j\phi} e^{j\omega t} \right] = \operatorname{Re} \left[\omega L I_m e^{j(\phi+90^\circ)} e^{j\omega t} \right]$$

$$i(t) = I_m \cos(\omega t + \phi)$$

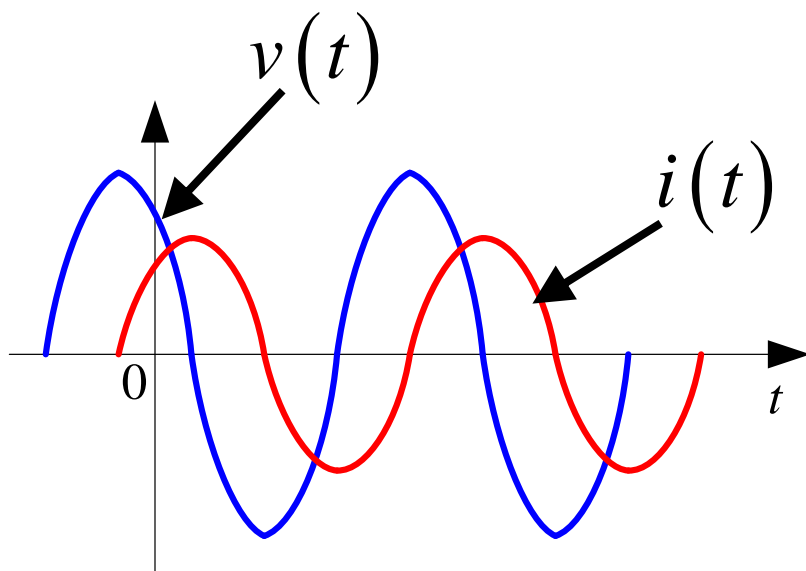


■ For inductor,
 $v(t)$ leads $i(t)$
by 90° .

Summary


Resistor:

$$\hat{V} = R \cdot \hat{I}$$

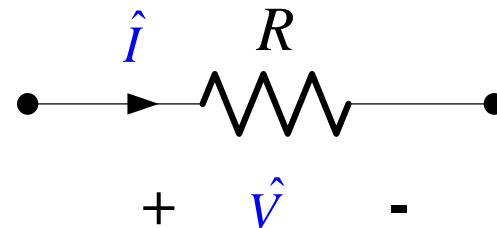


Capacitor:
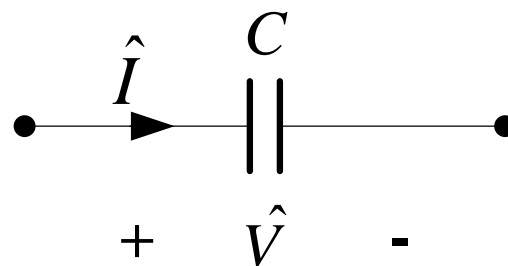
$$\hat{V} = \frac{1}{j\omega C} \hat{I}$$



Inductor:

$$\hat{V} = j\omega L \hat{I}$$

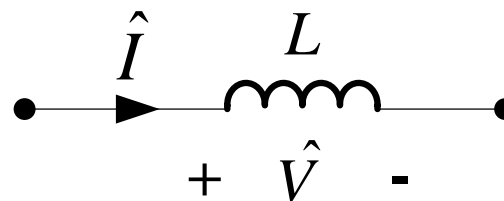



Impedance and Admittance

■ Impedance:

defined as the ratio of a circuit element's **voltage phasor** to its **current phasor**.

$$Z = \frac{\hat{V}}{\hat{I}} \quad \text{:measured in } \Omega$$

■ Admittance:

defined as the reciprocal of impedance.

$$Y = \frac{1}{Z} = \frac{\hat{I}}{\hat{V}} \quad \text{:measured in S}$$



VCR

Impedance

Admittance

R:

$$\hat{V} = R \cdot \hat{I}$$

$$Z = R$$

$$Y = 1/R = G$$

C:

$$\hat{V} = \frac{1}{j\omega C} \hat{I}$$

$$Z = \frac{1}{j\omega C}$$

$$Y = j\omega C$$

L:

$$\hat{V} = j\omega L \hat{I}$$

$$Z = j\omega L$$

$$Y = 1/j\omega L$$



Ohm's Law in Frequency Domain

$$\hat{V} = Z\hat{I}$$

$$Z = R$$

$$Z = \frac{1}{j\omega C}$$

$$Z = j\omega L$$

$$\hat{I} = Y\hat{V}$$

$$Y = 1/R = G$$

$$Y = j\omega C$$

$$Y = 1/j\omega L$$



Reactance and Susceptance

■ Reactance:

defined as the imaginary part of the impedance.

$$Z = R + jX$$


■ Susceptance:

defined as the imaginary of the admittance.


$$Y = G + jB$$

Example


$$\omega = 1000 \text{ rad / s}$$

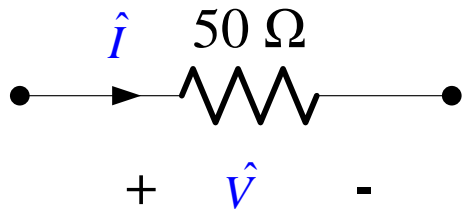

$$Z = R = 50 \Omega$$

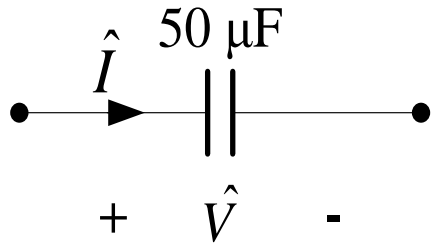

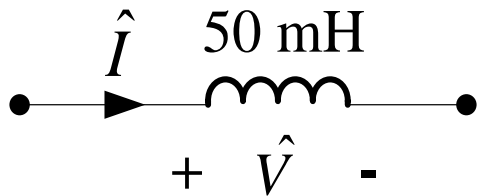
$$Z = \frac{1}{j\omega C} = -j \frac{1}{1000 \times 50 \times 10^{-6}} = -j20 \Omega$$



$$Z = j\omega L = j1000 \times 50 \times 10^{-3} = j50 \Omega$$

Example

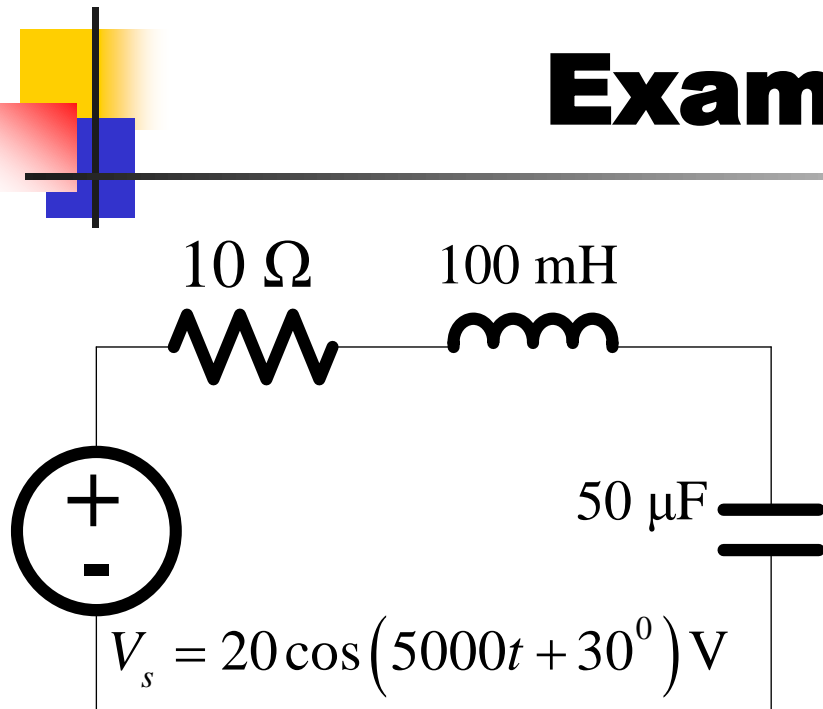

$$\omega = 5000 \text{ rad / s}$$


$$\begin{aligned}\hat{V}_s &= P \left[20 \cos(5000t + 30^\circ) \right] \\ &= 20 \angle 30^\circ \text{ V}\end{aligned}$$

$$Z_R = 10 \Omega$$



$$Z_L = j\omega L = j \times 5000 \times 100 \times 10^{-3} = j500 \Omega$$

$$Z_C = -j \frac{1}{\omega C} = -j \frac{1}{5000 \times 50 \times 10^{-6}} = -j4 \Omega$$

Circuits in Frequency Domain

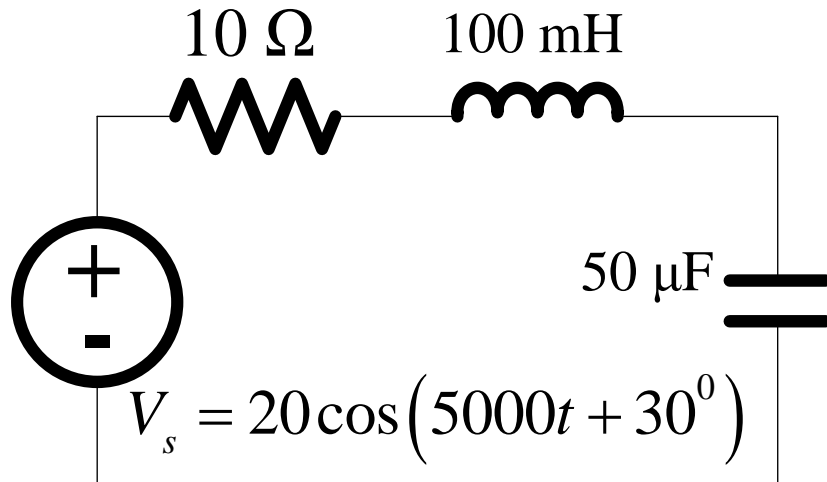

$$\omega = 5000 \text{ rad / s}$$

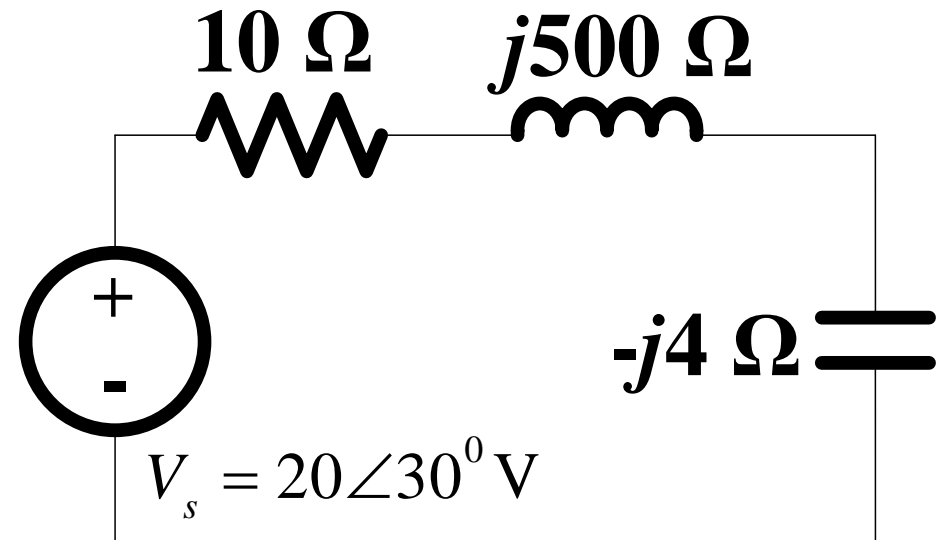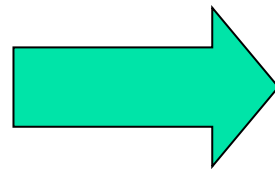



8-6 KCL and KVL in Phasors

- KCL in frequency domain
- KVL in frequency domain



KCL in Frequency Domain


- **The algebraic sum of all the phasor currents entering any node in a circuit is ZERO.**

$$\sum_{n=1}^N \hat{I}_n = 0$$




Proof:

$$\begin{aligned}\sum_{n=1}^N i_n(t) &= \sum_{n=1}^N \operatorname{Re} \left[I_{mn} e^{j\theta_n} e^{j\omega t} \right] = \operatorname{Re} \left[e^{j\omega t} \cdot \sum_{n=1}^N I_{mn} e^{j\theta_n} \right] \\ &= \operatorname{Re} \left[e^{j\omega t} \cdot \sum_{n=1}^N \hat{I}_n \right] = 0\end{aligned}$$


$$\sum_{n=1}^N \hat{I}_n = 0$$

KCL in Frequency Domain

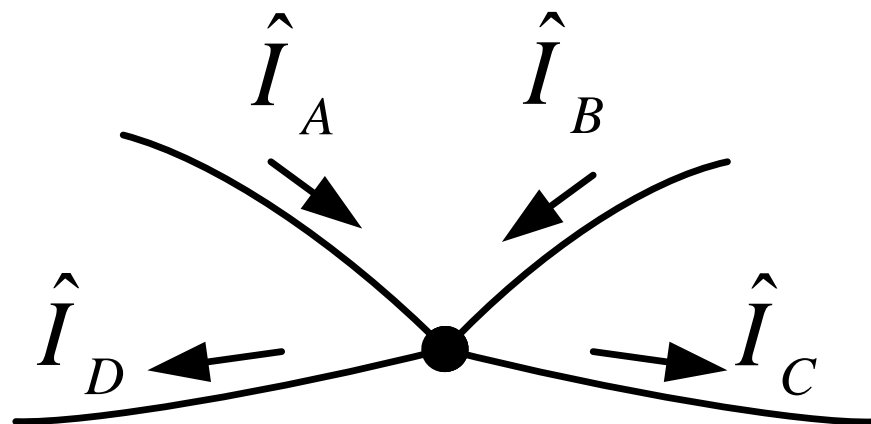

$$\hat{I}_A + \hat{I}_B = \hat{I}_C + \hat{I}_D$$

$$\hat{I}_A + \hat{I}_B + (-\hat{I}_C) + (-\hat{I}_D) = 0$$

$$(-\hat{I}_A) + (-\hat{I}_B) + \hat{I}_C + \hat{I}_D = 0$$



KVL in Frequency Domain


- **The algebraic sum of all the phasor voltages around any loop in a circuit is ZERO.**

$$\sum_{n=1}^N \hat{V}_n = 0$$




Proof:

$$\begin{aligned}\sum_{n=1}^N v_n(t) &= \sum_{n=1}^N \operatorname{Re} \left[V_{mn} e^{j\theta_n} e^{j\omega t} \right] = \operatorname{Re} \left[\sum_{n=1}^N V_{mn} e^{j\theta_n} e^{j\omega t} \right] \\ &= \operatorname{Re} \left[e^{j\omega t} \cdot \sum_{n=1}^N \hat{V}_n \right] = 0\end{aligned}$$

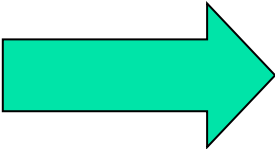
$$\sum_{n=1}^N \hat{V}_n = 0$$

KVL in Frequency Domain

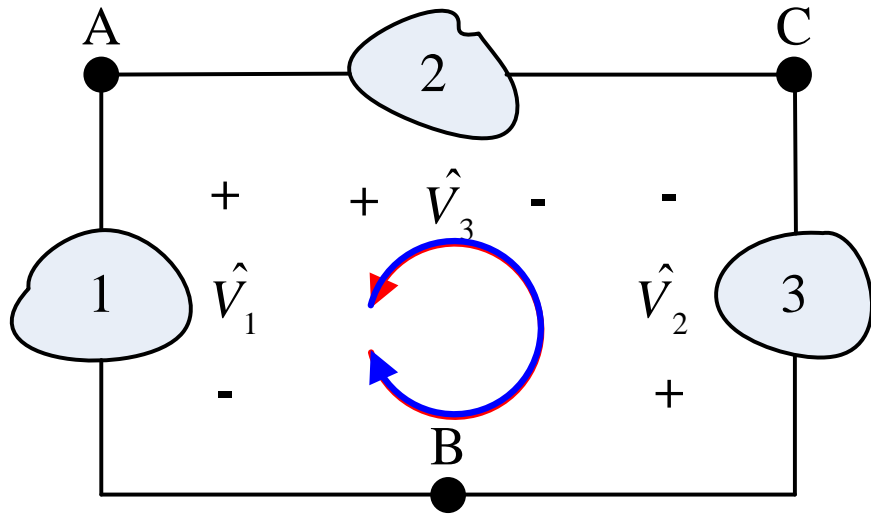


$$\hat{V}_1 = \hat{V}_3 - \hat{V}_2$$

$$\hat{V}_1 + \hat{V}_2 - \hat{V}_3 = 0$$

$$-\hat{V}_1 + \hat{V}_3 - \hat{V}_2 = 0$$

Impedances in Series and Parallel

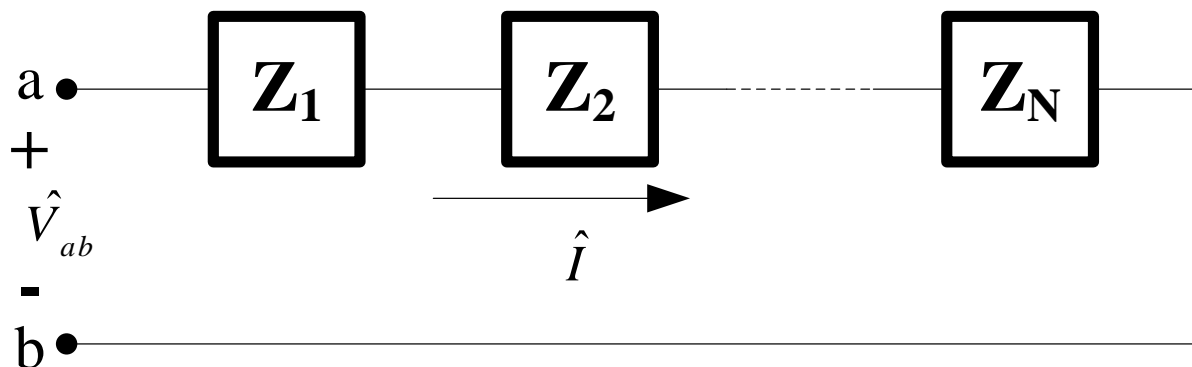


By KVL in phasor:

$$\hat{V}_{ab} = \hat{V}_1 + \hat{V}_2 + \cdots + \hat{V}_N = \sum_{n=1}^N \hat{V}_n$$

$$= \sum_{n=1}^N (Z_n \hat{I}) = \hat{I} \sum_{n=1}^N Z_n \quad \Rightarrow \quad Z_{ab} = \frac{\hat{V}_{ab}}{\hat{I}_{ab}} = \sum_{n=1}^N Z_n$$

Impedances in Series and Parallel

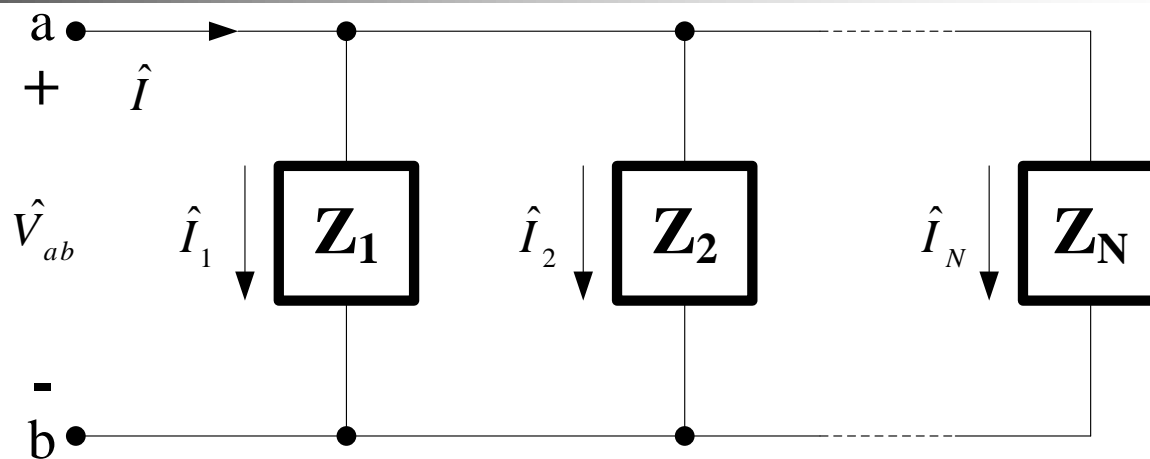


By KCL in phasor:


$$\hat{I} = \hat{I}_1 + \hat{I}_2 + \dots + \hat{I}_N = \sum_{n=1}^N \hat{I}_n$$

$$= \sum_{n=1}^N \left(\frac{\hat{V}_{ab}}{Z_n} \right) = \hat{V}_{ab} \sum_{n=1}^N \left(\frac{1}{Z_n} \right) \quad \longrightarrow \quad \frac{1}{Z_{ab}} = \frac{\hat{I}}{\hat{V}_{ab}} = \sum_{n=1}^N \frac{1}{Z_n}$$

Voltage/Current Division

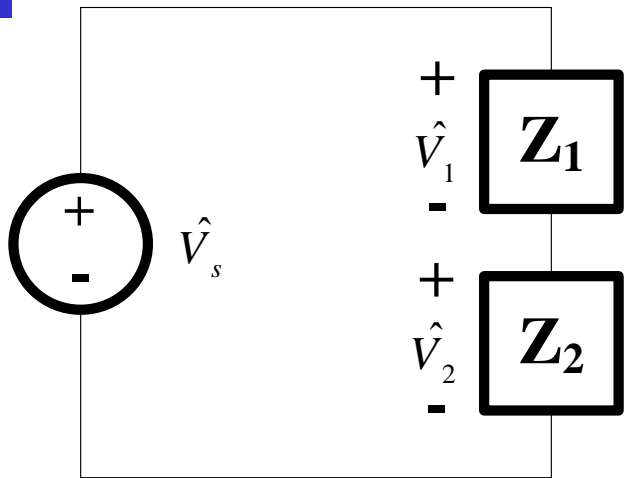

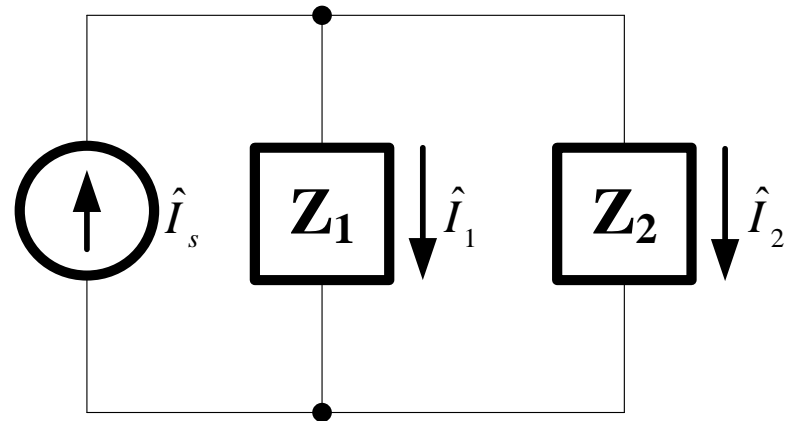
$$\begin{cases} \hat{V}_1 = \frac{Z_1}{Z_1 + Z_2} \hat{V}_s \\ \hat{V}_2 = \frac{Z_2}{Z_1 + Z_2} \hat{V}_s \end{cases}$$



$$\begin{cases} \hat{I}_1 = \frac{Z_2}{Z_1 + Z_2} \hat{I}_s \\ \hat{I}_2 = \frac{Z_1}{Z_1 + Z_2} \hat{I}_s \end{cases}$$

Example

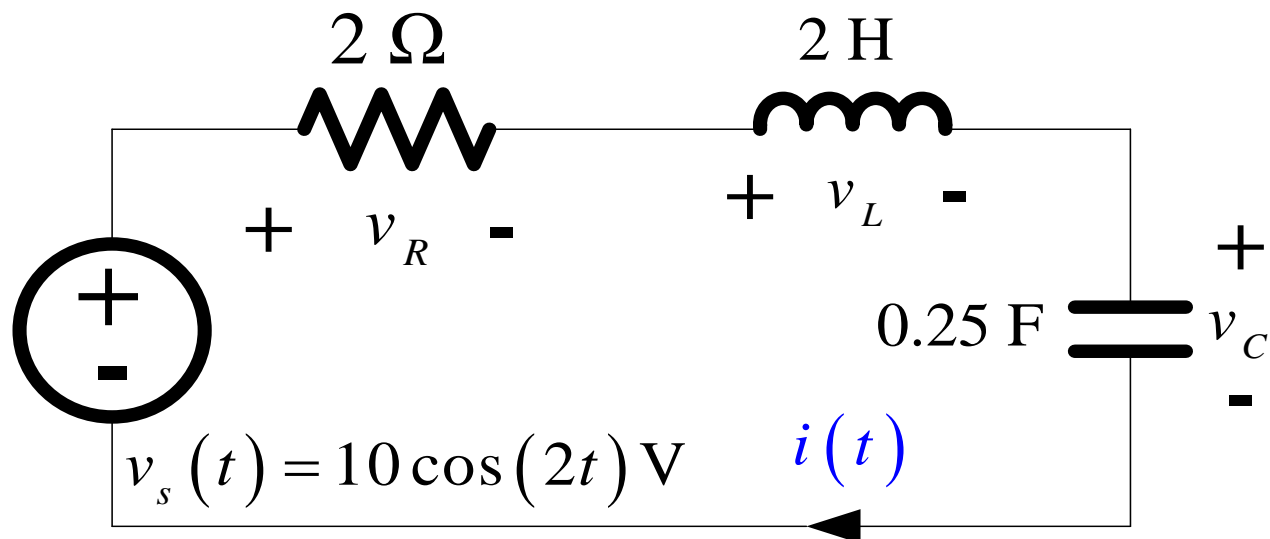


Find the steady-state current $i(t)$ and voltages across all passive elements.

Solution:

$$\omega = 2 \text{ rad} / \text{s} \quad \hat{V}_s = 10 \angle 0^\circ \text{ V}, \quad Z_R = R = 2 \Omega$$
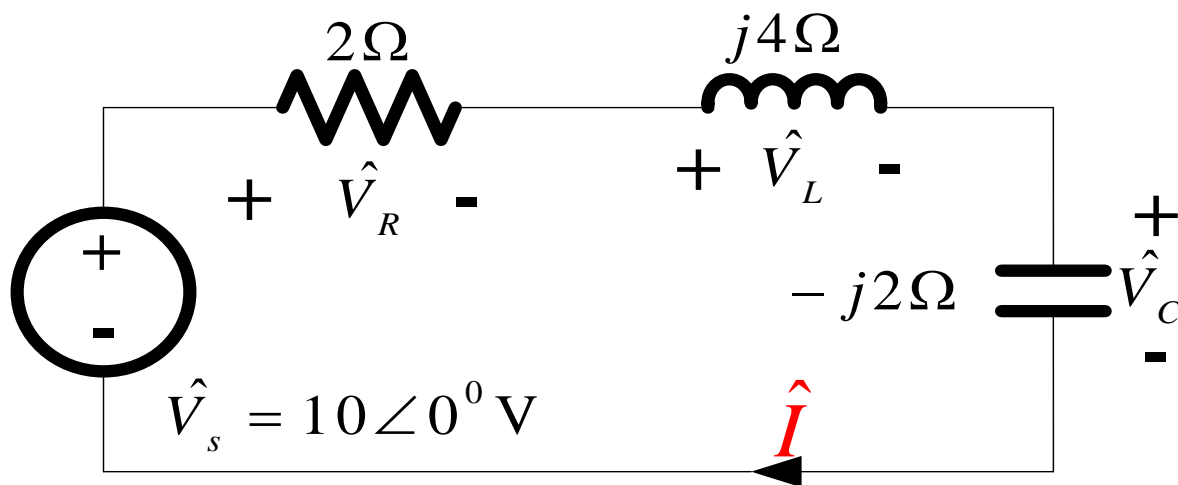
$$Z_L = j\omega L = j4 \Omega, \quad Z_C = \frac{1}{j\omega C} = -j2 \Omega$$






Apply KVL to the loop: $\hat{V}_s = (Z_R + Z_L + Z_C) \hat{I}$

$$\begin{aligned}\hat{I} &= \frac{\hat{V}}{Z_R + Z_L + Z_C} = \frac{10\angle 0^\circ}{2 + j4 - j2} = \frac{10\angle 0^\circ}{2 + j2} \\ &= \frac{10\angle 0^\circ}{2\sqrt{2}\angle 45^\circ} = \frac{5}{\sqrt{2}} \angle -45^\circ \text{ A}\end{aligned}$$


$$i(t) = \text{Re}[\hat{I}e^{j\omega t}] = \text{Re}\left[\frac{5}{\sqrt{2}}e^{j(-45^\circ)}e^{j\omega t}\right] = \frac{5}{\sqrt{2}}\cos(2t - 45^\circ) \text{ A}$$



$$\begin{cases} \hat{V}_R = Z_R \hat{I} = \frac{10}{\sqrt{2}} \angle -45^\circ \text{ V} \\ \hat{V}_L = Z_L \hat{I} = j4 \times \frac{5}{\sqrt{2}} \angle -45^\circ = \frac{20}{\sqrt{2}} \angle 45^\circ \text{ V} \\ \hat{V}_C = Z_C \hat{I} = -j2 \times \frac{5}{\sqrt{2}} \angle -45^\circ = \frac{10}{\sqrt{2}} \angle -135^\circ \text{ V} \end{cases}$$

$$\begin{cases} v_R = \frac{10}{\sqrt{2}} \cos(2t - 45^\circ) \text{ V} \\ v_L = \frac{20}{\sqrt{2}} \cos(2t + 45^\circ) \text{ V} \\ v_C = \frac{10}{\sqrt{2}} \cos(2t - 135^\circ) \text{ V} \end{cases}$$


$$\omega = 2 \text{ rad / s}$$

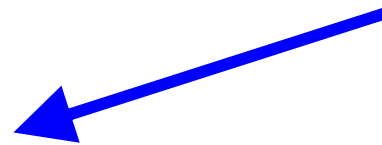




Steps of Sinusoidal Steady State Analysis:

- 1. Represent all voltage/current source
by phasors;**
- 2. Find the phasor model of the given
circuit by phasor transform;**

- 
-
- 3. Find the **sinusoidal steady-state response** in frequency domain by using KCL/KVL, or mesh-current/node-voltage method, or circuit theorems;**
 - 4. Find the corresponding response in time domain by **inverse phasor transform** if necessary.**

Example

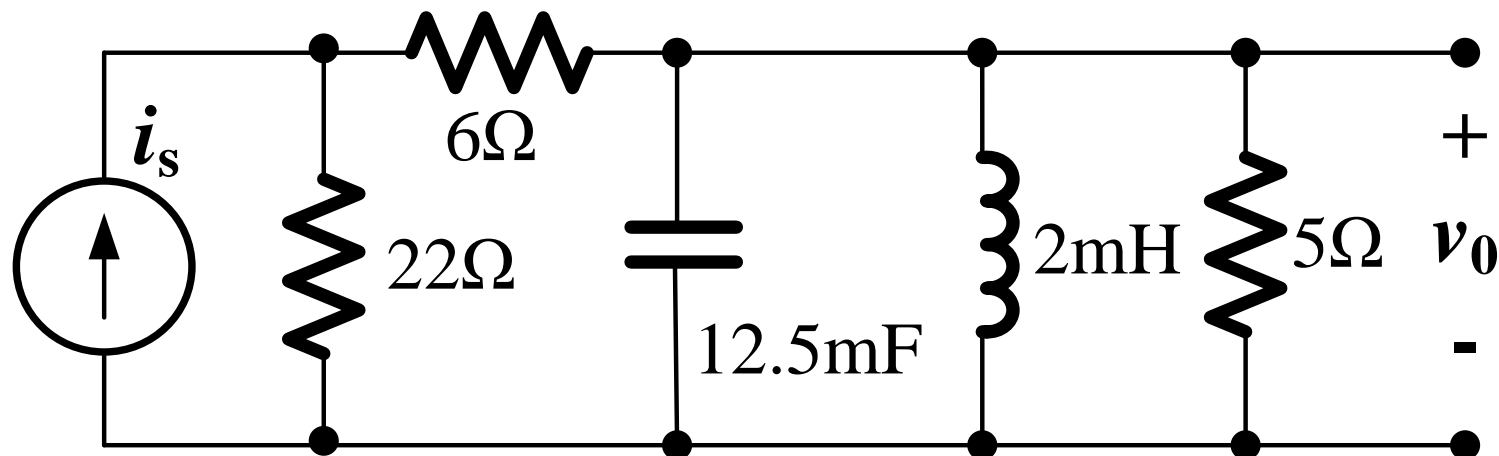

The circuit shown above is operating in the sinusoidal steady state. Find the voltage v_0 if $i_s = 3\cos(200t)\text{mA}$.

$$v_0 = 10\cos(200t)\text{mV}$$

Solution


$$\omega = 200 \text{ rad/s}, R = 5 \Omega$$

$$Z_c = \frac{1}{j\omega C} = \frac{1}{j \times 200 \times 12.5 \times 10^{-3}} = -0.4j \Omega$$

$$Z_L = j\omega L = j \times 200 \times 2 \times 10^{-3} = 0.4j \Omega$$

$$\frac{1}{Z} = \frac{1}{Z_c} + \frac{1}{Z_L} + \frac{1}{Z_R}, \text{ 则 } Z = Z_R, \text{ 那么并联电阻 } Z = 5 \Omega$$

电路可以等效为
右图的电路：

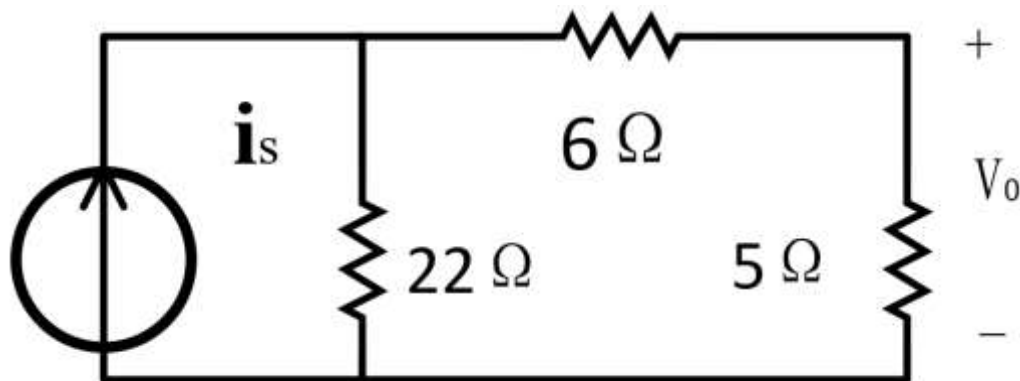




Solution

电路为 22Ω 电阻与 11Ω 电阻并联电路

则流过 v_0 的电流为

$$i_{v_0} = \frac{22}{22 + 6 + 5} i_s = \frac{2}{3} i_s = 2\cos(200t)\text{mA}$$


$$v_0 = Ri_{v_0} = 10\cos(200t)\text{mV}$$



8-7 Mesh-Current and Node-Voltage Method

- **Mesh-Current Method in
Frequency Domain**
- **Node-Voltage Method in
Frequency Domain**

Example

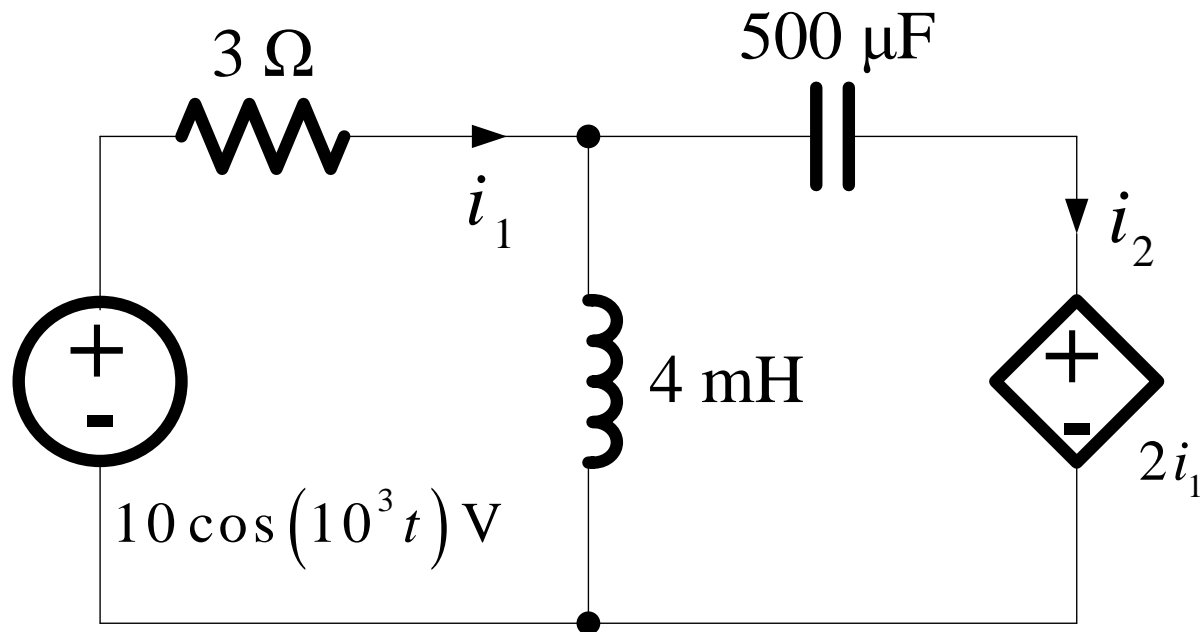

Find the current of $i_1(t)$ and $i_2(t)$ for the circuit shown above by mesh-current method.



Solution:

$$\omega = 10^3 \text{ rad} / \text{s}$$


$$\hat{V}_s = 10 \angle 0^\circ$$

$$Z_R = R = 2\Omega$$

$$Z_L = j\omega L = j10^3 \times 4 \times 10^{-3} = j4\Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j10^3 \times 500 \times 10^{-6}} = -j2\Omega$$

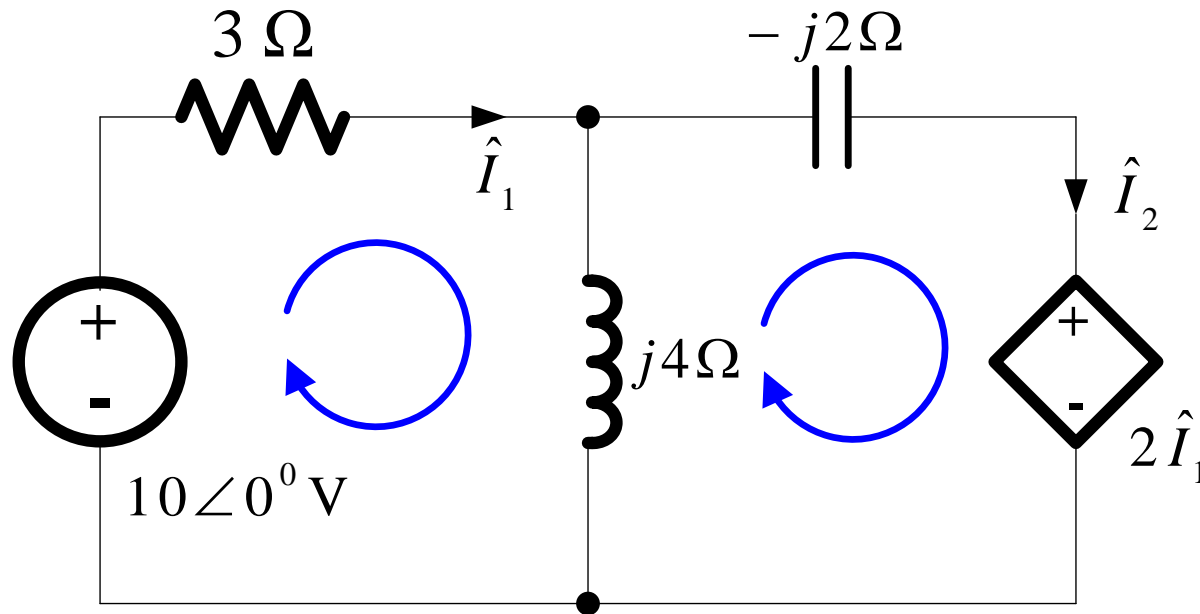
The frequency domain equivalent circuit represented by phasors is:






By mesh current method:

$$\begin{cases} 3\hat{I}_1 + j4(\hat{I}_1 - \hat{I}_2) = 10\angle 0^\circ \\ j4(\hat{I}_2 - \hat{I}_1) - j2\hat{I}_2 = -2\hat{I}_1 \end{cases}$$

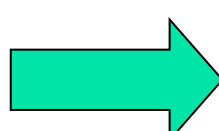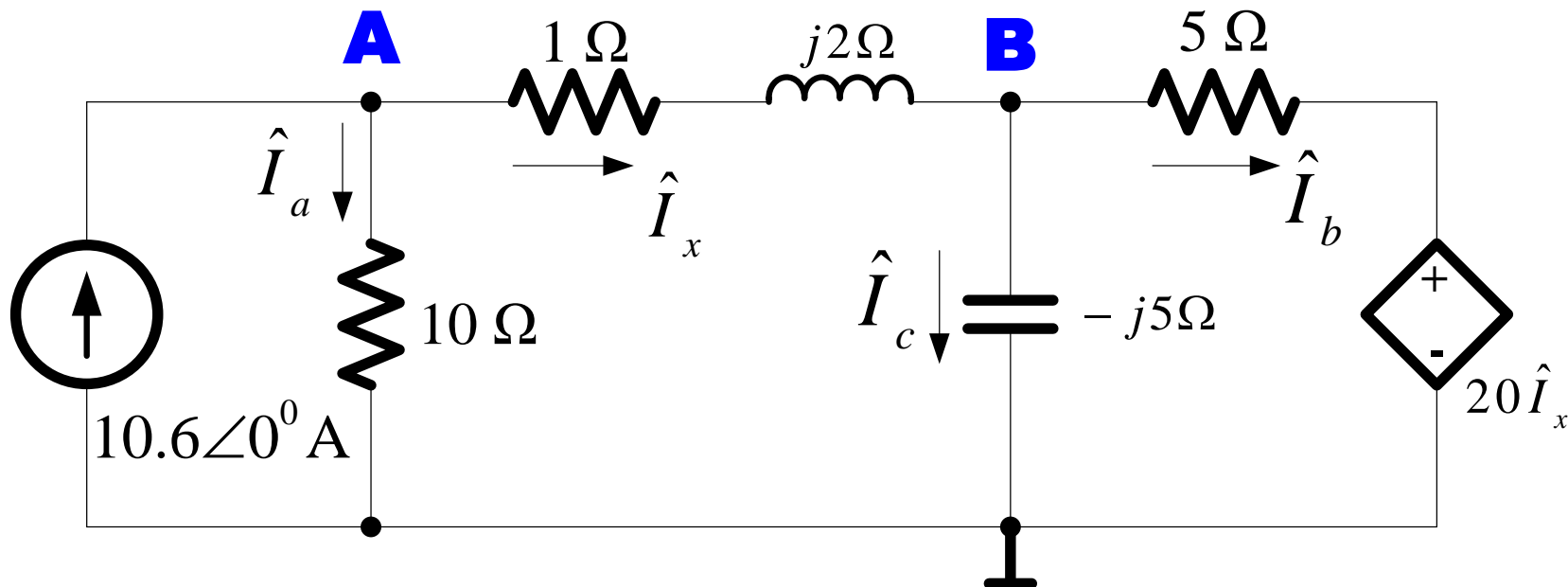

$$\begin{cases} \hat{I}_1 = \frac{10}{7 - j4} = 1.24\angle 29.7^\circ \text{ A} \\ \hat{I}_2 = \frac{20 + j30}{13} = 2.77\angle 56.3^\circ \text{ A} \end{cases}$$


$$\omega = 10^3 \text{ rad} / \text{s}$$

The required currents of $i_1(t)$ and $i_2(t)$ are:

$$\begin{cases} i_1 = 1.24 \cos(10^3 t + 29.7^\circ) \text{ A} \\ i_2 = 2.77 \cos(10^3 t + 56.3^\circ) \text{ A} \end{cases}$$

Example



Find the current of \hat{I}_a , \hat{I}_b , and \hat{I}_c for the circuit shown above by node-voltage method.



Solution:

Apply KCL for node A and node B:



$$\begin{cases} \frac{\hat{V}_1}{10} + \frac{\hat{V}_1 - \hat{V}_2}{1 + j2} - 10.6 = 0 \\ \frac{\hat{V}_2 - \hat{V}_1}{1 + j2} + \frac{\hat{V}_2}{-j5} + \frac{\hat{V}_2 - 20\hat{I}_x}{5} = 0 \\ \hat{I}_x = \frac{\hat{V}_1 - \hat{V}_2}{1 + j2} \end{cases} \quad \rightarrow \quad \begin{cases} \hat{V}_1 = 68.4 - j16.8\text{V} \\ \hat{V}_2 = 68 - j26\text{V} \end{cases}$$




**Hence the
required
currents are:**

$$\left\{ \begin{array}{l} \hat{I}_a = \frac{\hat{V}_1}{10} = 6.84 - j1.68\text{A} \\ \hat{I}_x = \frac{\hat{V}_1 - \hat{V}_2}{1 + j2} = 3.76 + j1.68\text{A} \\ \hat{I}_b = \frac{\hat{V}_2 - 20\hat{I}_x}{5} = -1.44 - j11.92\text{A} \\ \hat{I}_c = \frac{\hat{V}_2}{-j5} = 5.2 + j13.6\text{A} \end{array} \right.$$

8-8 Source Transformation

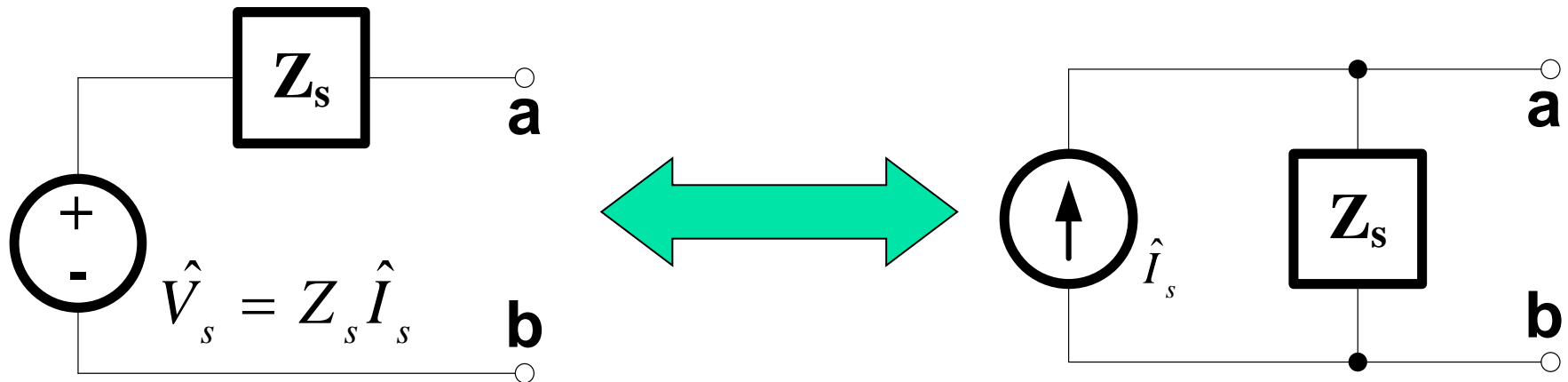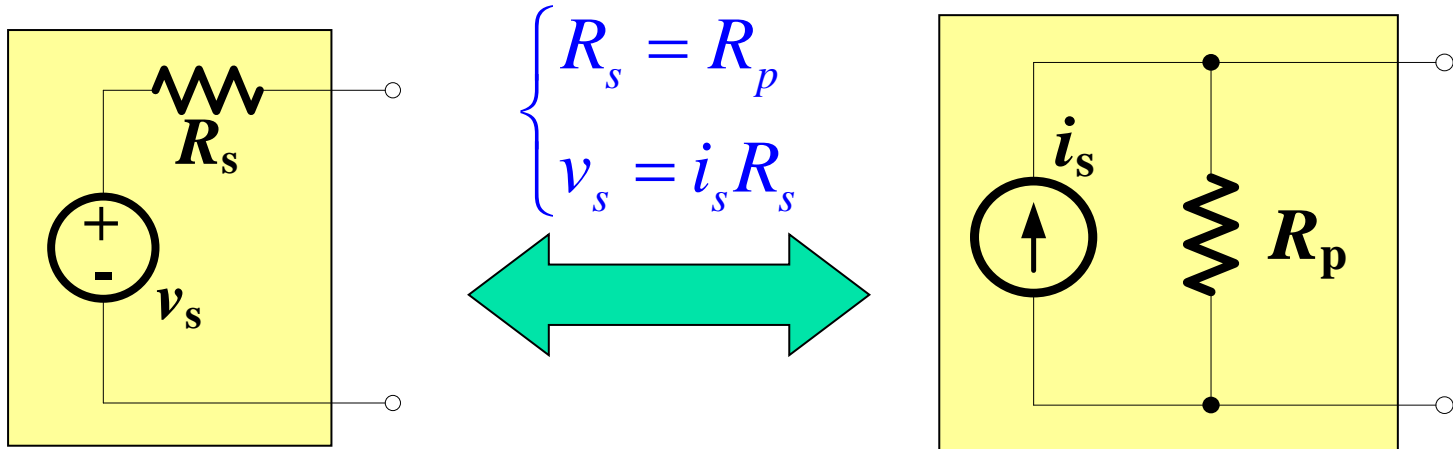

Example

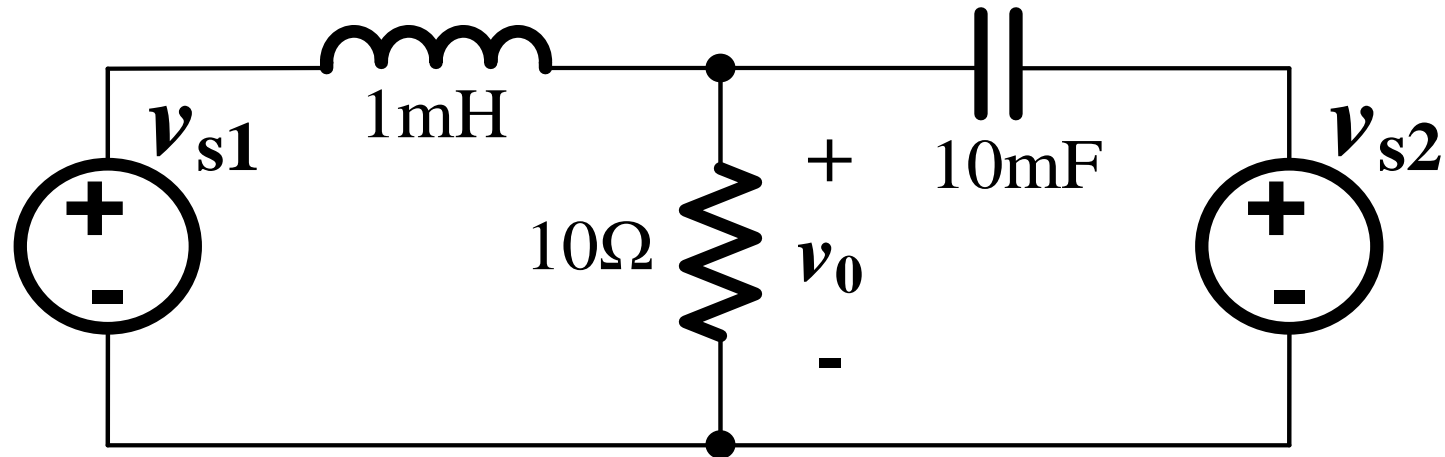

Use source transformation to find the steady state expression v_0 if $v_{s1}=20\cos(200t)\text{V}$ and $v_{s2}=50\cos(200t)\text{V}$.

$$v_0 = 0$$


Solution


$$\omega = 200 \text{ rad/s}$$

$$Z_L = j\omega l = j \times 200 \times 1 \times 10^{-3} = 0.2j\Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 200 \times 10 \times 10^{-3}} = -0.5j\Omega$$

经过电源变换后的电路图如下：

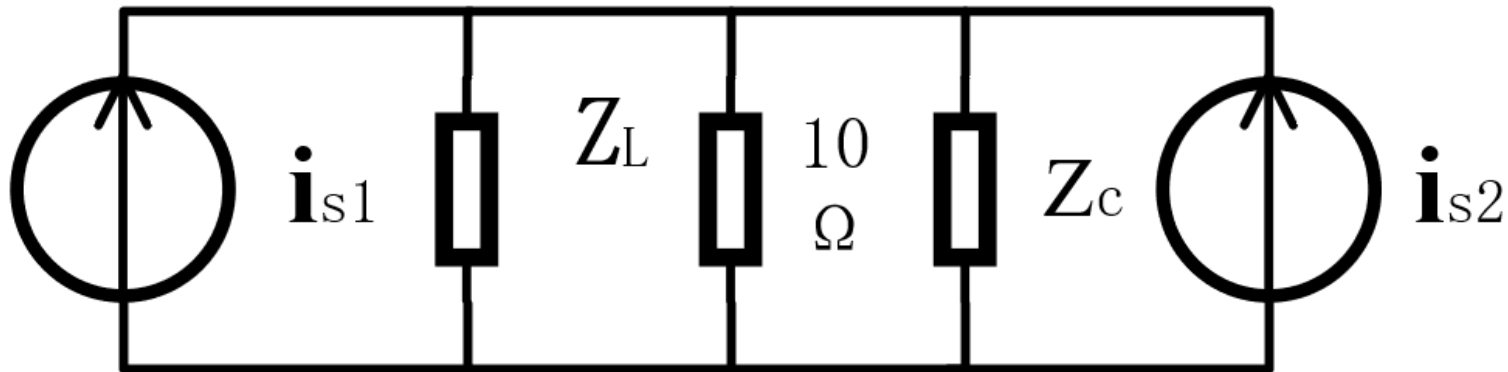




其中 $i_{s1} = \frac{v_{s1}}{Z_L} = \frac{20\cos(200t)}{0.2j} = -j100\cos(200t)A$

$$i_{s2} = \frac{v_{s2}}{Z_c} = \frac{50\cos(200t)}{-0.5j} = j100\cos(200t)A$$

电流源合并则经过 v_0 的电流为 $i = 0A$

所以 $v_0 = iR = 0V$

Superposition Theorem

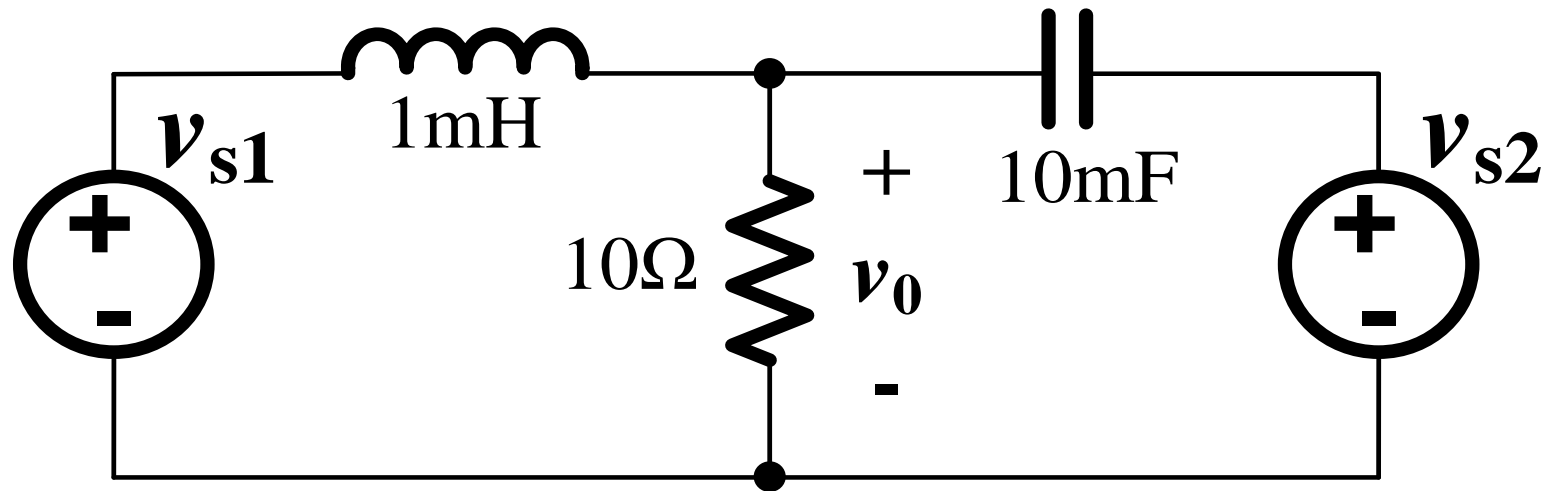

You can try it by **Superposition Theorem**.



Solution

叠加定理是各个电源单独作用时对电路的影响，
当电源单独作用时其他电压源看作短路，其他
电流源看作断路。


电容与电感的电阻为：

$$\omega = 200 \text{ rad/s}$$


$$Z_L = j\omega l = j \times 200 \times 1 \times 10^{-3} = 0.2j\Omega$$


$$Z_C = \frac{1}{j\omega c} = \frac{1}{j \times 200 \times 10 \times 10^{-3}} = -0.5j\Omega$$

当 v_{s1} 单独作用时:

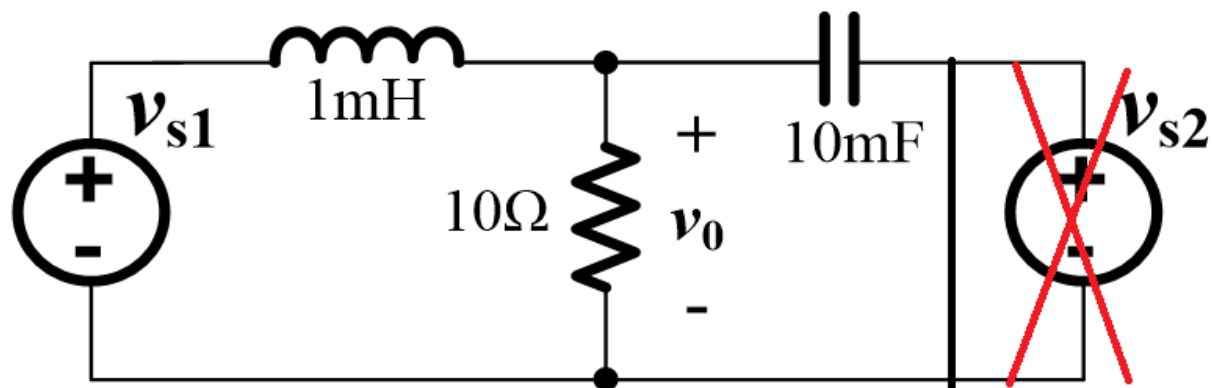

当 v_{s2} 单独作用时:

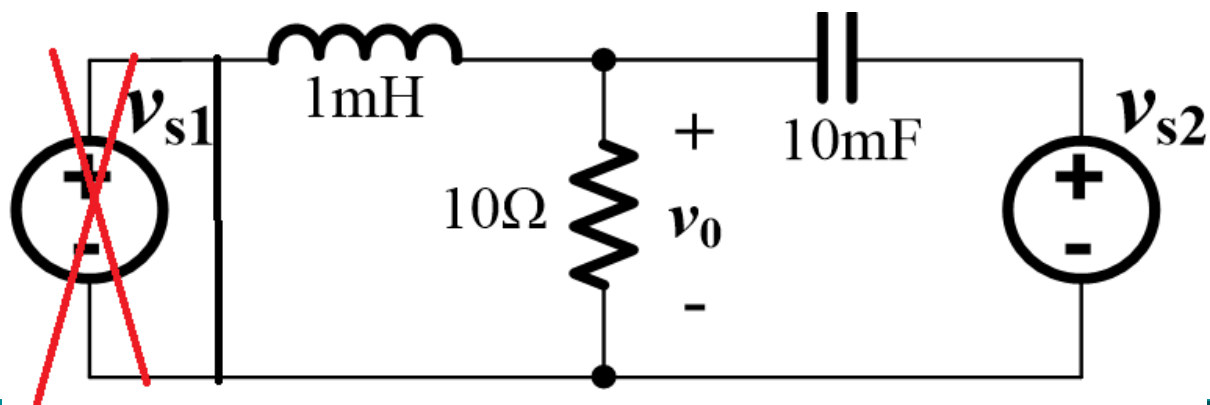



当 v_{s1} 单独作用时 v_0 等于电阻与电容的并联电压

电阻与电容的并联电阻为: $Z_1 = \frac{Z_R Z_C}{Z_R + Z_C}$,


当 v_{s1} 作用时 $v_0 = \frac{Z_1}{Z_1 + Z_L} v_{s1} = \frac{250 \cos(200t)}{3j - 0.1} \text{ V}$

当 v_{s2} 单独作用时 v_0 等于电阻与电感的并联电压

电阻与电感的并联电阻为: $Z_2 = \frac{Z_R Z_L}{Z_R + Z_L}$,

当 v_{s2} 作用时 $v_0 = \frac{Z_2}{Z_2 + Z_C} v_{s1} = \frac{250 \cos(200t)}{0.1 - 3j} \text{ V}$


所以 v_0 在 v_{s1} 和 v_{s2} 同时作用时为0V



8-9 Thévenin Equivalents and Norton Equivalents

- **Thévenin Equivalents in Frequency Domain**
- **Norton Equivalents in Frequency Domain**


Example

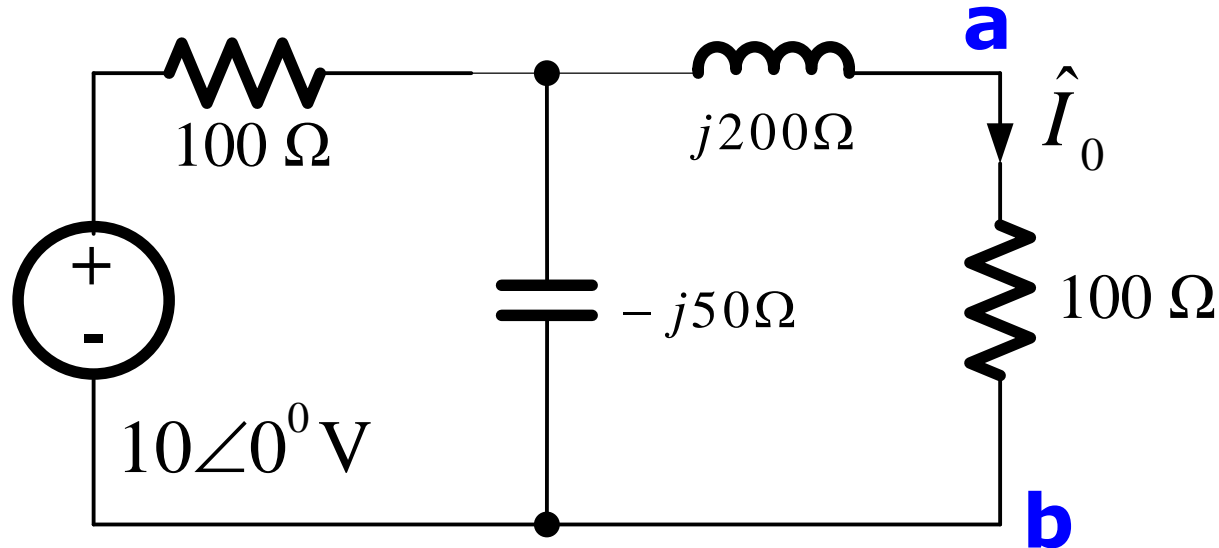

Find the current of \hat{I}_0 for the circuit shown above by Thévenin equivalent.


Solution:

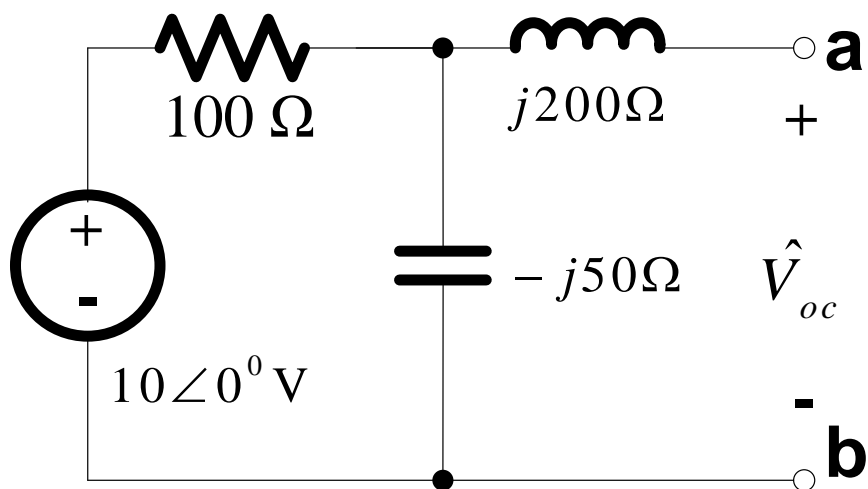1. Find the open circuit voltage between terminal a and b:



$$\begin{aligned}\hat{V}_{oc} &= \frac{-j50}{-j50 + 100} \times 10\angle 0^\circ \\ &= \frac{-j}{-j + 2} \times 10\angle 0^\circ \\ &= \frac{\angle -90^\circ}{\sqrt{5}\angle -26.6^\circ} \times 10\angle 0^\circ \\ &= 2\sqrt{5}\angle -63.4^\circ \text{ V}\end{aligned}$$

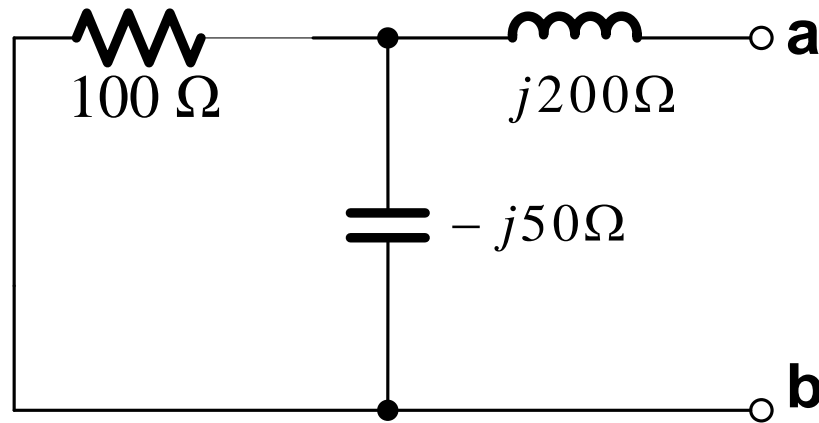
2. Find the Thévenin equivalent **impedance** between terminal a and b:



$$Z_{Th} = j200 + \frac{100(-j50)}{100 - j50} = (20 + j160)\ \Omega$$




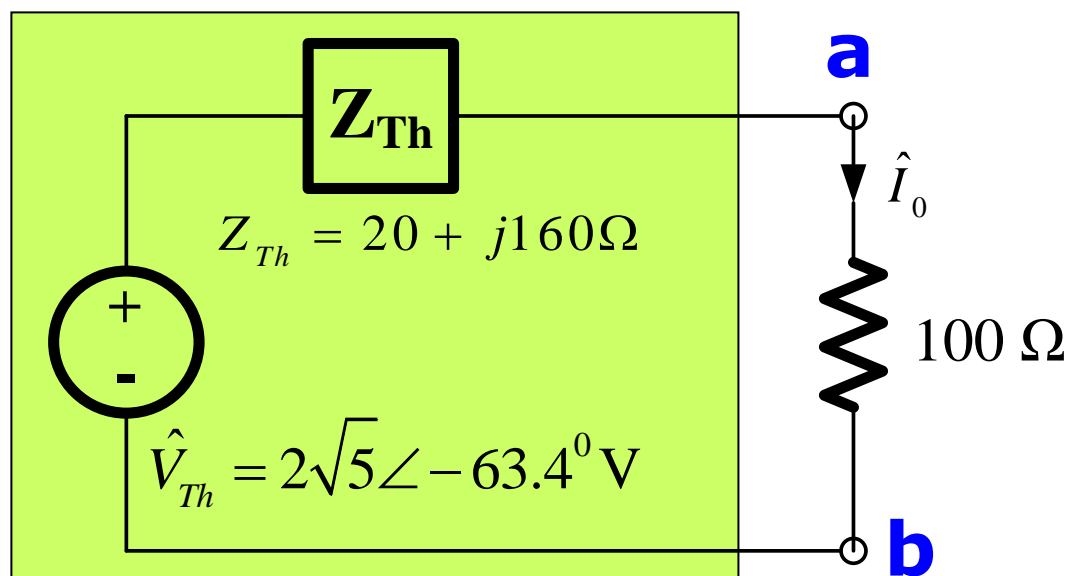Hence, the Thévenin equivalent between terminal a and b is:



$$\hat{I}_0 = \frac{\hat{V}_{Th}}{Z_{Th} + 100\Omega} = \frac{2\sqrt{5}\angle -63.4^\circ}{20 + j160 + 100} = 0.0224\angle -116.53^\circ \text{ A}$$


Example

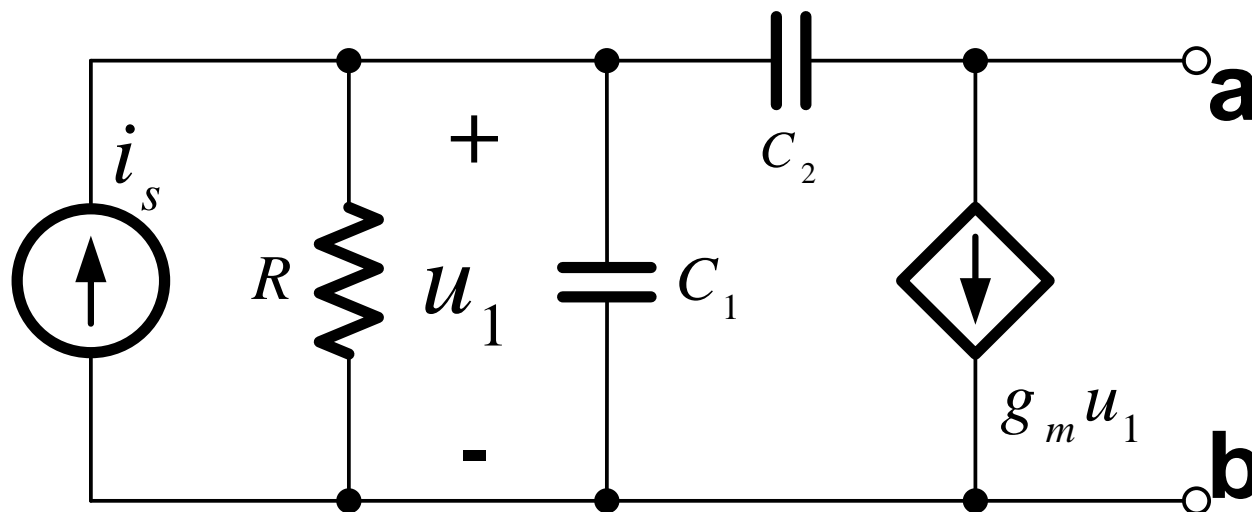

Find the Thévenin equivalent for the two terminals of a and b in the circuit shown above.

Solution:

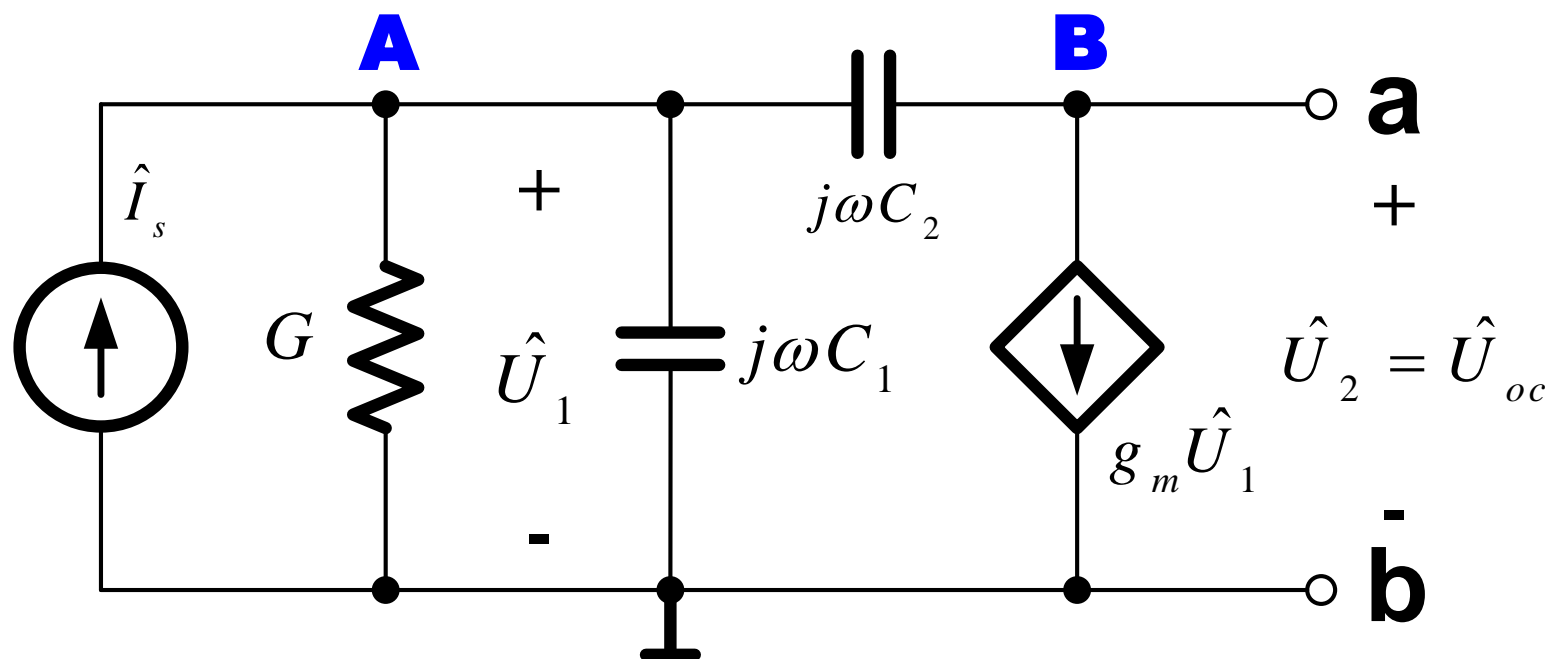The frequency domain equivalent circuit represented by phasors is:





1. Find the open circuit voltage between the terminal a and b:


Apply node voltage method:

$$\begin{cases} G\hat{U}_1 + j\omega C_1\hat{U}_1 + j\omega C_2(\hat{U}_1 - \hat{U}_2) = \hat{I}_s \\ j\omega C_2(\hat{U}_2 - \hat{U}_1) + g_m\hat{U}_2 = 0 \end{cases}$$

$$\text{Then, } \hat{U}_{oc} = \hat{U}_2 = \frac{(j\omega C_2 - g_m)\hat{I}_s}{-\omega^2 C_1 C_2 + j\omega C_2(g_m + G)}$$



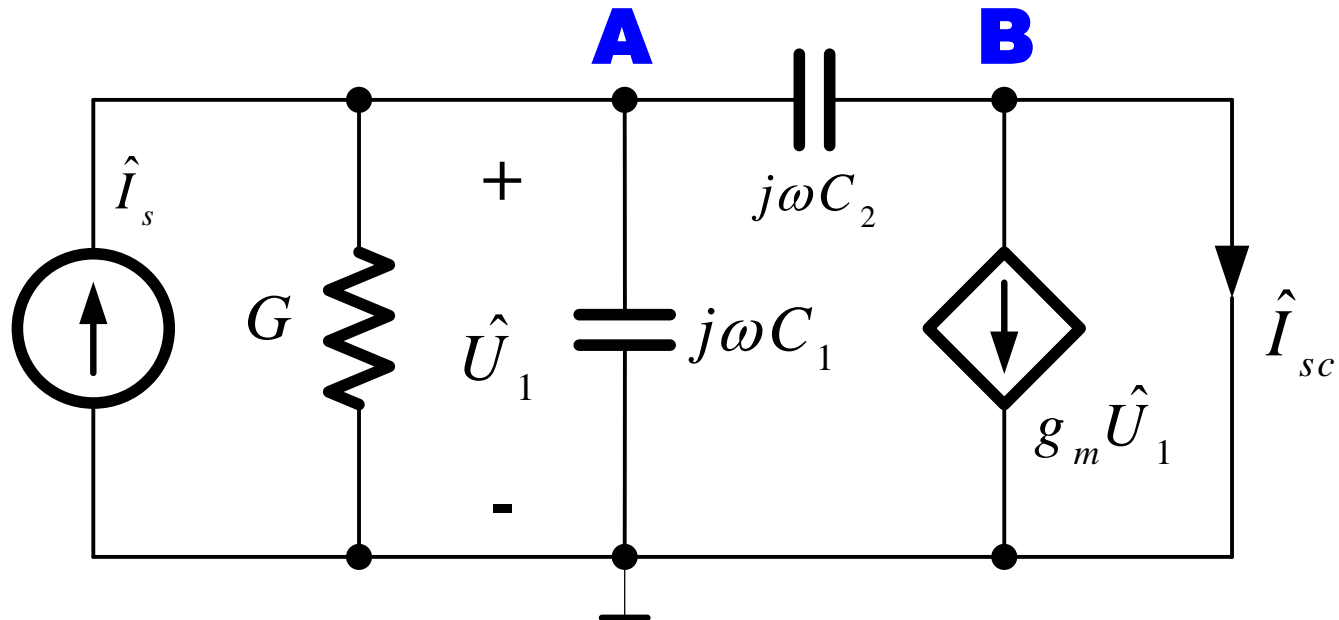2. Find the short circuit current between the terminal a and b:





Apply node-voltage method for the circuit:

$$\begin{cases} \hat{I}_{sc} = j\omega C_2 \hat{U}_1 - g_m \hat{U}_1 \\ \hat{I}_s = G \hat{U}_1 + j\omega C_1 \hat{U}_1 + j\omega C_2 \hat{U}_1 \end{cases}$$

$$\Rightarrow \hat{I}_{sc} = \frac{(j\omega C_2 - g_m) \hat{I}_s}{G + j\omega(C_1 + C_2)}$$




3. Find the Thévenin Equivalent Impedance:


$$\hat{U}_{Th} = \hat{U}_{oc} = \frac{(j\omega C_2 - g_m) \hat{I}_s}{-\omega^2 C_1 C_2 + j\omega C_2 (g_m + G)}$$

$$Z_{Th} = \frac{\hat{U}_{oc}}{\hat{I}_{sc}} = \frac{G + j\omega(C_1 + C_2)}{-\omega^2 C_1 C_2 + j\omega C_2 (g_m + G)}$$

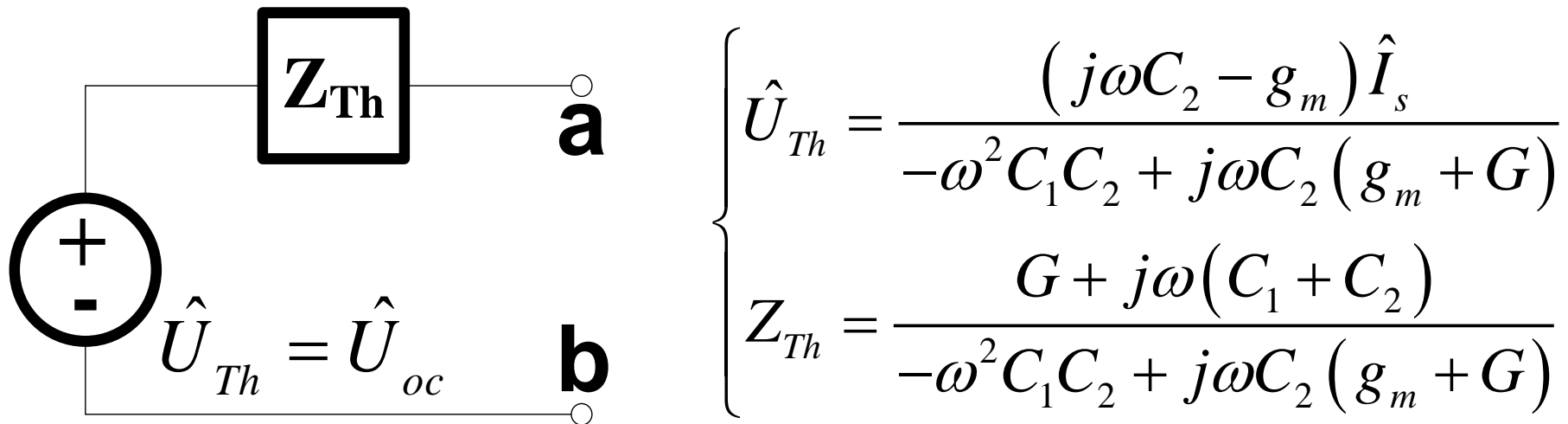Hence, the Thévenin equivalent for the two terminals of a and b is:



Norton Equivalents

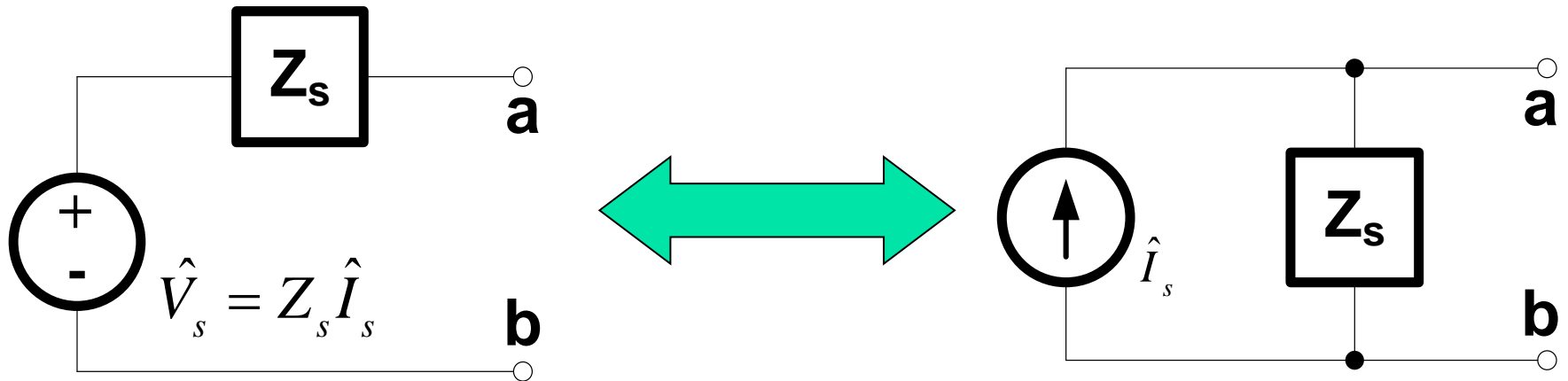

Norton equivalent can be derived from Thévenin equivalent by source transformation; and vice versa.



Summary of Chapter 8

- Conception of phasor;
- Phasor transform and inverse phasor transform
- Circuit in frequency domain by phasors
- KCL and KVL in frequency domain
- Node-voltage and mesh-current method, Source transformation, Superposition, Thévenin and Norton Equivalents in frequency domain