



# **Introduction to Electronic Systems**

---


**Zheng Feng**



# Part 1: Resistive Circuit Analysis

---

1. Circuit Variables and Circuit Elements
- 2. Simple Resistive Circuit Analysis**
3. Techniques of Circuit Analysis
4. Operational Amplifier



# **Chapter 2: Simple Resistive Circuit Analysis**

---

- **Kirchhoff's Laws**
- **Analysis of Simple Circuit Containing  
Controlled Sources**
- **Resistors in Series and in Parallel**



## 2-1 Kirchhoff's Laws

---

- **Definitions for Circuit Topology**
- **Kirchhoff's Current Law (KCL)**
- **Kirchhoff's Voltage Law (KVL)**




# Some Definitions

---


- **Node**
- **Path**
- **Loop**
- **Branch**
- **Mesh**

# Planar circuit

## A non-planar circuit

 


## A planar circuit

 

# Node (1)

- A point which two or more elements have connected to is called a node.


This is all one  
NODE.

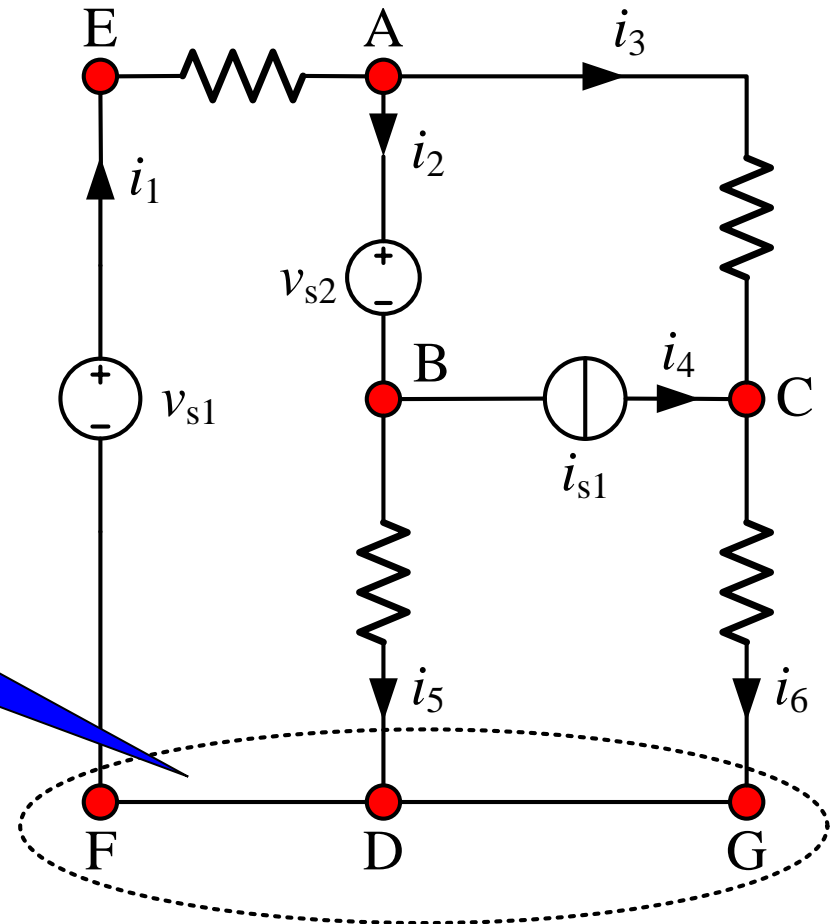

# Node (2)
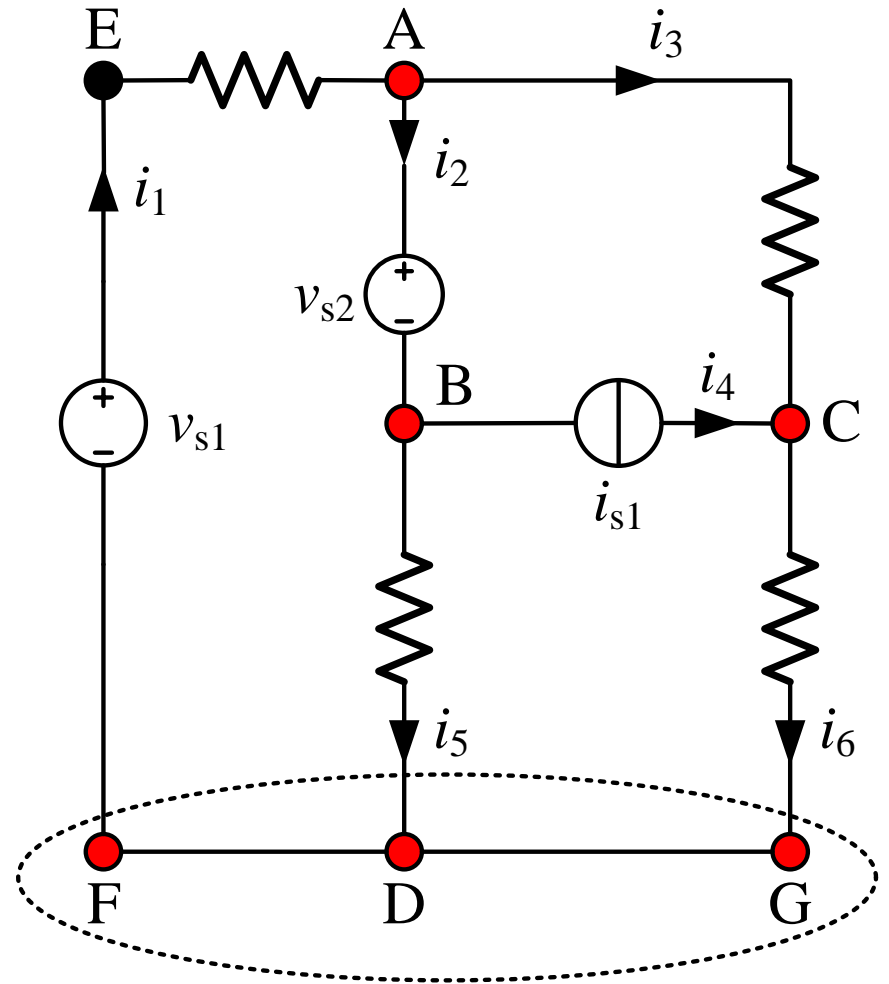
## ■ Essential **NODE**:

A node where three or more elements join.







# Node (3)


---

## Notes:

- A NODE is a point where two or more circuit elements meet;
- Consider all of the perfect conducting wires as part of a NODE;
- Every element has a NODE at each of its terminals.

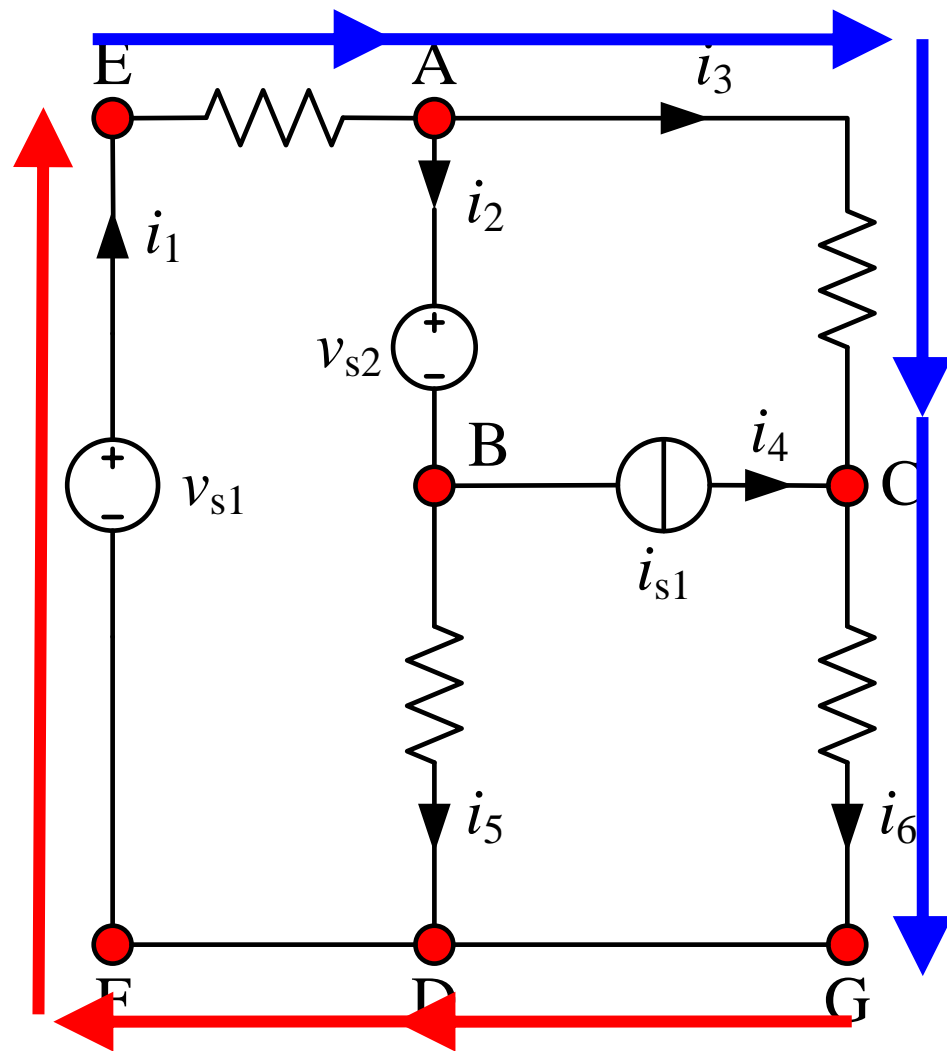
# Path

■ A **PATH** is a trace of adjoining basic elements with no intermediate nodes included more than once.



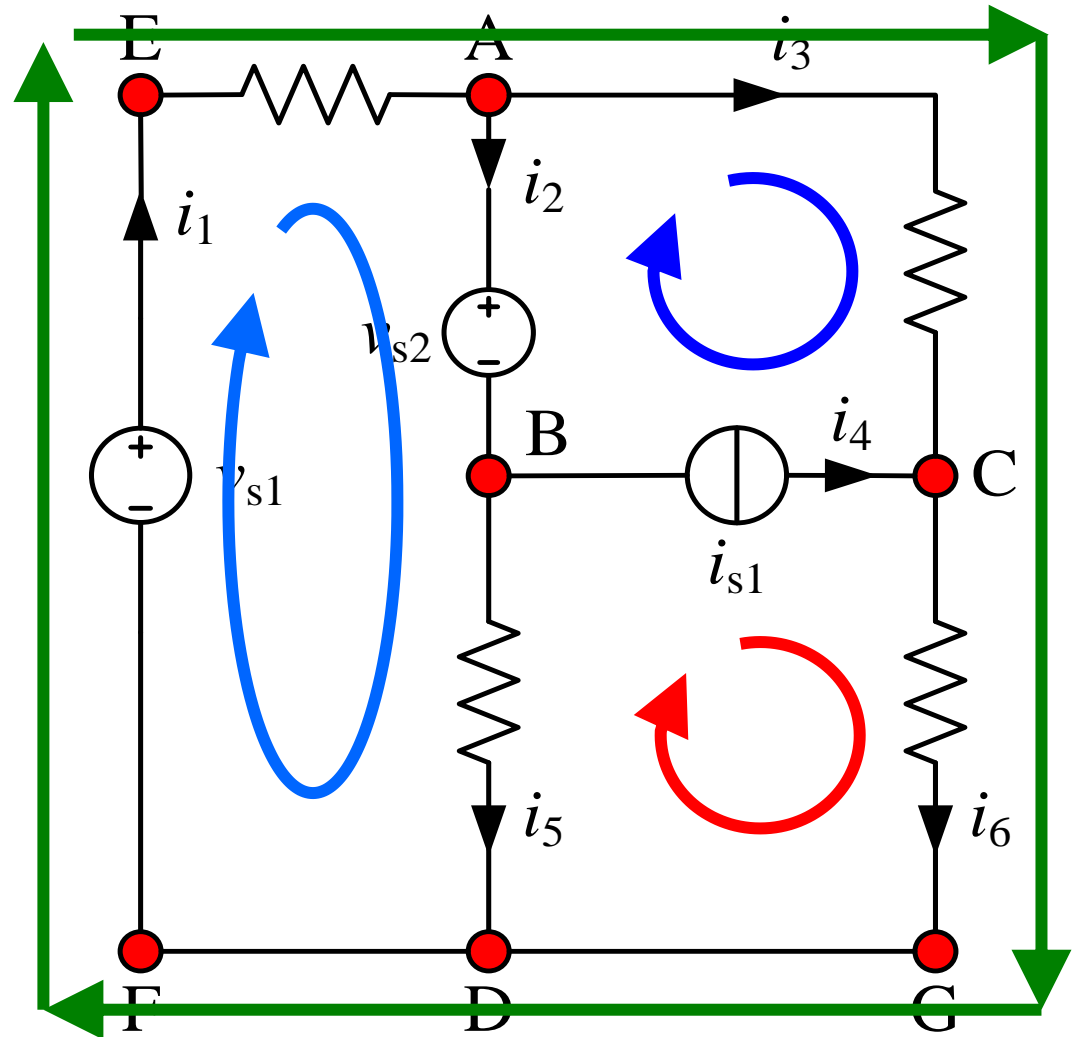
# Loop

■ A **LOOP** is a path whose last node is the same as the starting node, or a closed path.


 
# Branch (1)


■ A **BRANCH** is defined as a path that connects two adjoining nodes.



# Branch (2)

 
## ■ Essential branch

- Connects two essential nodes without passing through any essential node.



 
# Mesh (1)


- A **MESH** is:  
defined as a loop  
that does not  
contain any other  
loops within it.
- Mesh does not  
enclose any  
branches.



# How many branches, nodes, meshes?

 

# How many branches, nodes, meshes?

 

**ANS: 14 branches; 9 nodes; 6 meshes**



# Kirchhoff's Laws

**Topology  
Constraint**

+

**Element  
Constraint**

=

**Circuit  
Behavior**



**KCL, KVL**



**Ohm's Law\***  
**IVS, ICS, ...**

**\* For resistive elements**



# Kirchhoff's Current Law (KCL)

**KCL:** The **algebraic** sum of all the currents entering **any** node in a circuit is **zero**.

$$\sum_{n=1}^N i_n(t) = 0$$

# Kirchhoff's Current Law (KCL)

$$i_A + i_B + (-i_C) + (-i_D) = 0$$

*Or:*

$$(-i_A) + (-i_B) + i_C + i_D = 0$$

*Or:*

$$i_A + i_B = i_C + i_D$$

**Reference direction of current is critical for KCL.**




# Generalization of KCL

The algebraic sum of all the currents entering any **closed surface** is zero.

$$\sum_{n=1}^N i_n(t) = 0$$

# Generalization of KCL

 

Or:  $4 + (-7) + 10 = (-2) + i_2$




# Kirchhoff's Voltage Law (KVL)

**KVL:** The **algebraic** sum of all the voltages around **any** loop in a circuit is **ZERO**.

$$\sum_{n=1}^N v_n(t) = 0$$

# Kirchhoff's Voltage Law (KVL)

 

$$-v_1 + v_2 - v_3 = 0$$

Or:

$$v_1 + v_3 - v_2 = 0$$

$$\text{Or: } v_1 = v_2 - v_3$$

**Guiding direction (clockwise or anti-clockwise)  
is critical for KVL.**

# Comments on KCL

**Conservation of Charge  $\Rightarrow$  KCL**

- A node cannot store, destroy, or generate charge
- Electrical charges cannot be accumulated at a node
- Continuity of current:

$$\oint \vec{\sigma} \cdot d\vec{S} = \frac{dq_{total}}{dt} = \sum_{n=1}^N i_n(t) = 0$$




# Comments on KVL



Conservation of Energy  $\Rightarrow$  KVL


- Potential difference (The energy/work required to move a unit charge) from point A to B is independent of the path taken from A to B;
 
$$\oint \vec{E} \cdot d\vec{l} = \sum_{n=1}^N v_n(t) = 0$$




# Apply KCL to a More Complex Circuit

  

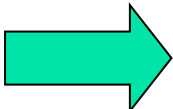**KCL**   $i_1 + (-i_2) + (-i_3) + i_4 + (-i_5) = 0$

# Apply KVL to a More Complex Circuit

 

**Loop I :**

$$v_1 + v_2 + v_6 - v_s = 0$$

**Loop II :**

$$v_3 - v_4 - v_2 = 0$$


**Loop III :**

$$v_4 + v_5 + v_7 = 0$$


**Loop IV :**

$$-v_6 + v_8 = 0$$


# Interconnections are valid?

 

(a)


 


(b)

 


(c)

# Interconnections are valid?

  


# Is the interconnection valid?

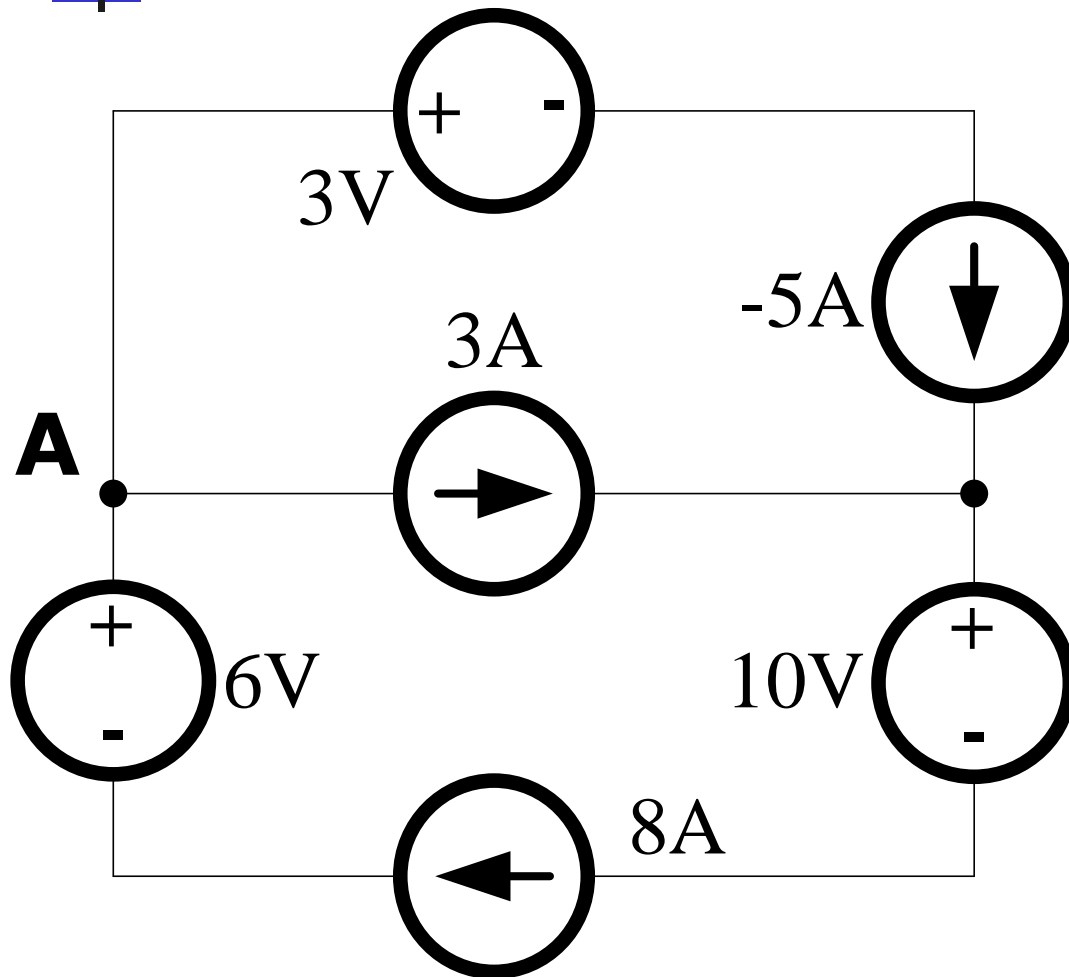


■ Apply KCL for node A:

$$8 - (-5) - 3 \neq 0$$

 


The connection is not permissible.

# Is the interconnection valid?

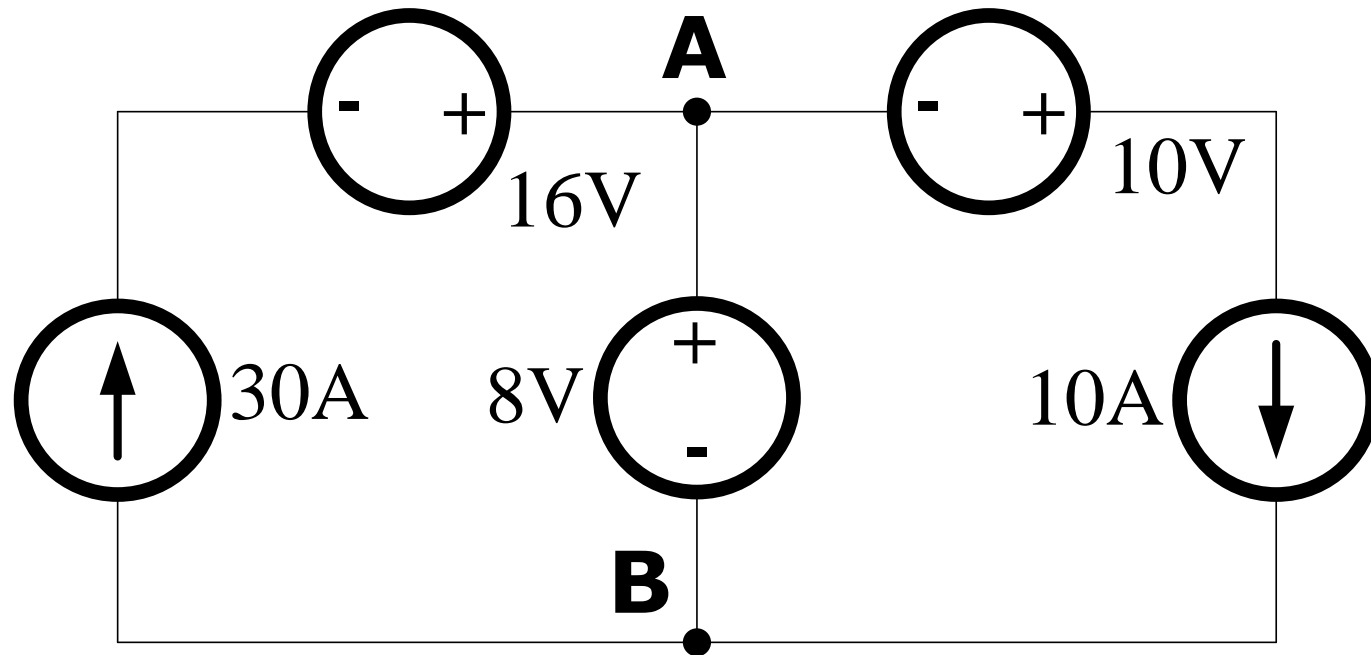


**By KCL and KVL, this connection is valid.**

# Is the interconnection valid?

 



(a)

 


(b)




# Is the interconnection valid?

  


# Interconnections are valid?

 


(e)

 

(f)

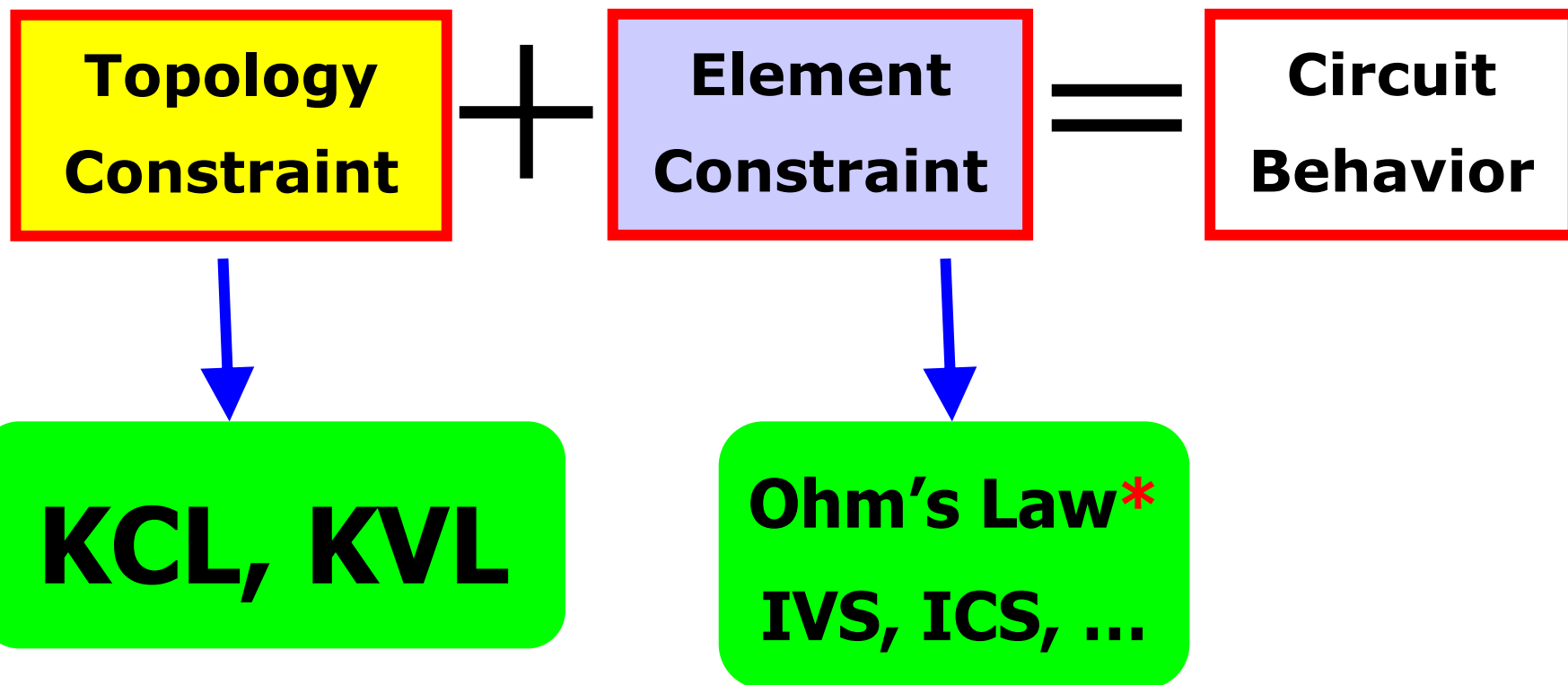


**\* For resistive elements**

 

**Behavior of resistive circuits can be determined now by using:**


- **Element constraint** --VCR for sources and resistors (Ohm's Law);
- **Topology constraint** --KCL and KVL!

# Example:

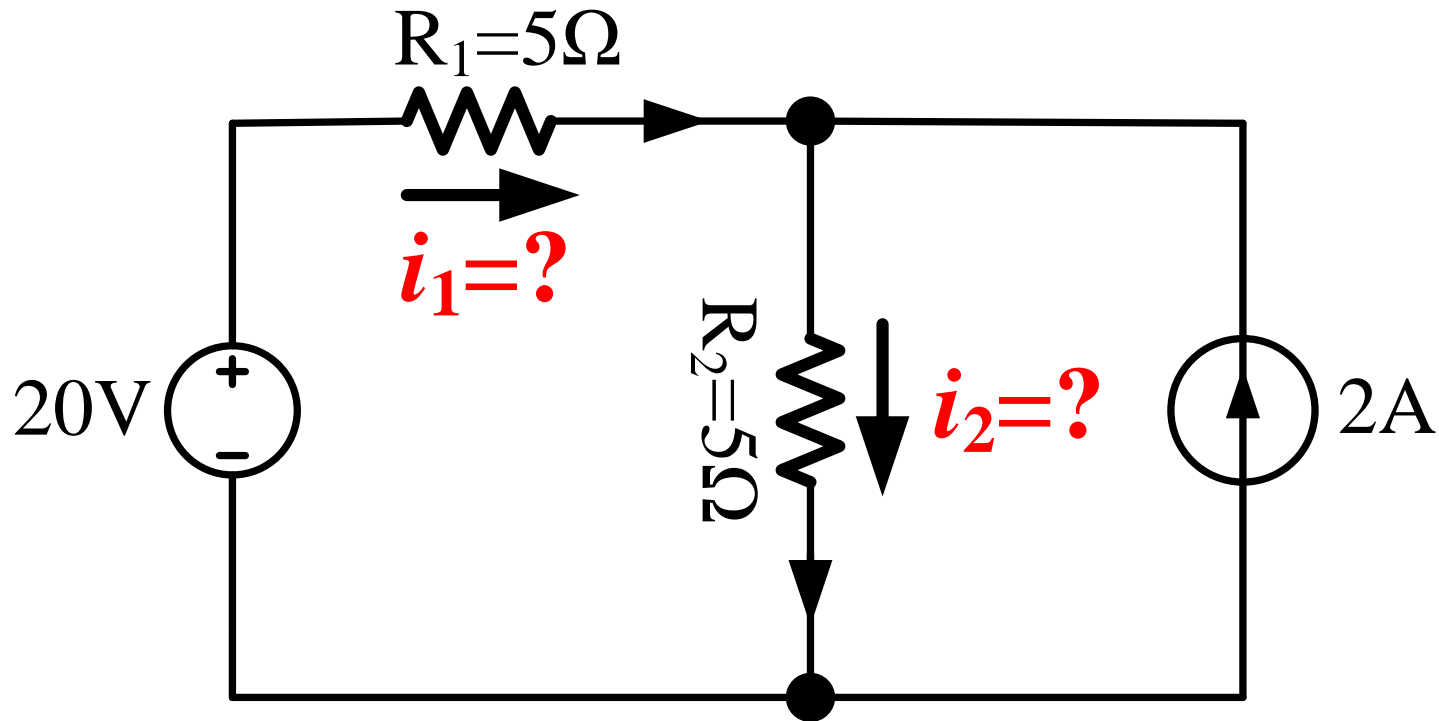


Find the value of current  $i_1$  and  $i_2$ .

# Solution:

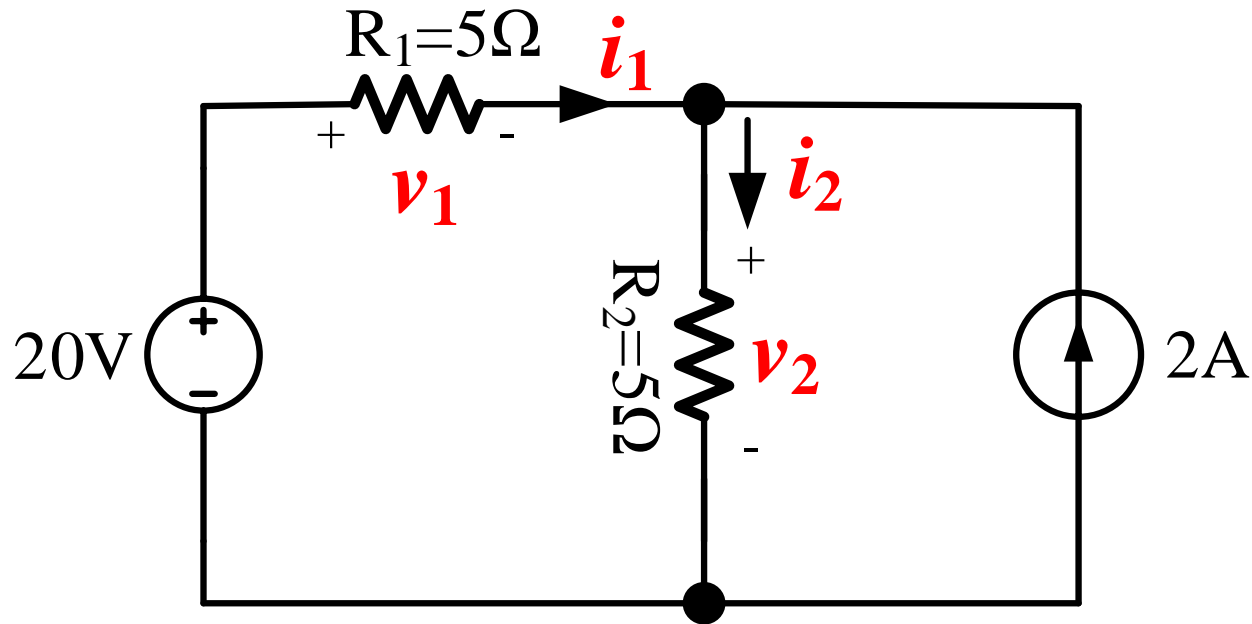

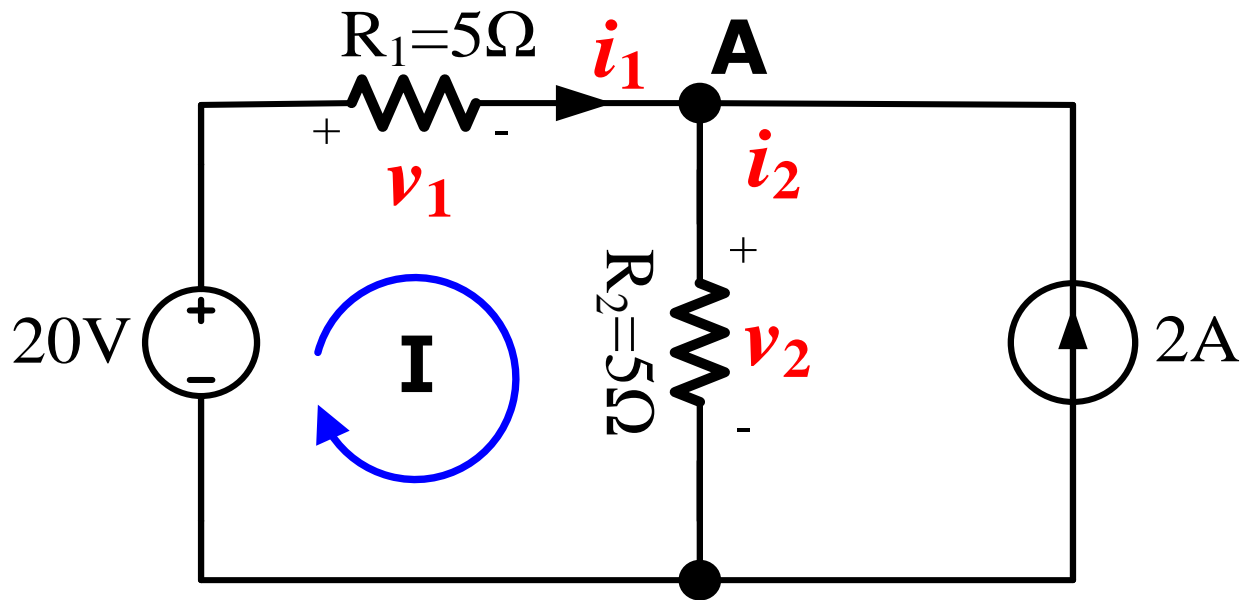By Ohm's law: 
$$\begin{cases} v_1 = 5i_1 \\ v_2 = 5i_2 \end{cases}$$



Apply KVL to loop **I**:  $v_1 + v_2 - 20 = 0$

Apply KCL to node **A**:  $i_1 - i_2 + 2 = 0$




**Then, build a set of equations:**

$$\left\{ \begin{array}{l} v_1 = 5i_1 \\ v_2 = 5i_2 \\ i_1 - i_2 + 2 = 0 \\ v_1 + v_2 - 20 = 0 \end{array} \right. \quad \rightarrow \quad \left\{ \begin{array}{l} i_1 = 1A \\ i_2 = 3A \end{array} \right.$$



# Check the answer by power balance:

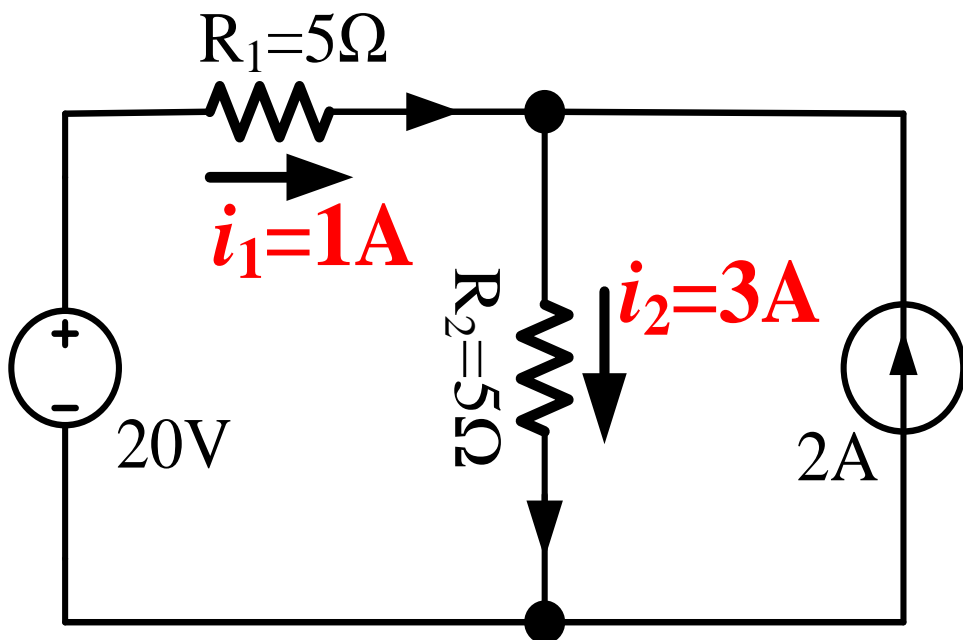

$$\left\{ \begin{array}{l} P_1 = 1^2 \times 5 = 5W \\ P_2 = 3^2 \times 5 = 45W \\ P_3 = -20 \times 1 = -20W \\ P_4 = -15 \times 2 = -30W \end{array} \right.$$



# Check the answer by power balance:


$$P_{dissipated} = P_1 + P_2 = 5 + 45 = 50\text{W}$$

$$P_{developed} = -(P_3 + P_4) = 20 + 30 = 50\text{W}$$

$$P_{dissipated} = P_{developed}$$


**Power is balanced, and the answer  
is reasonable!**

# Example:

 

Find the value of  $R$  and the power supplied by the 250V voltage source.

**ANS:  $R = 60\Omega$**

 

取顺时针为绕行方向,对四个回路列写KVL方程,对节点A, B, C列写KCL方程:

$$\begin{cases} -250 + 14I_1 + IR = 0 \\ -14I_1 + 30I_2 + 10I_4 = 0 \\ -IR - 10I_4 + 160 = 0 \\ -250 + 30I_2 + 160 = 0 \end{cases} \quad \begin{cases} I_U - I_2 - I_1 = 0 \\ I_1 + I_4 - I = 0 \\ I_2 - I_4 - 5 = 0 \end{cases}$$

解得

$$I_U = 8A; I_1 = 5A; I_2 = 3A;$$

$$I_4 = -2A; I = 3A; R = 60\Omega;$$


$$P_u = U_s \cdot I_U = 250V \times 8A = 2000W$$

注: R2, R3可以看做一个30Ω电阻; R5, R6可看做一个32Ω电阻以简化分析



## **2-2 Analysis of Simple Circuit Containing Controlled Sources**

# Example:

 

**Find the value of voltage  $v_o$  .**



# Solution:

By KVL, we have: 
$$\begin{cases} 10 = 6i_s \\ 3i_s = 2i_o + 3i_o \end{cases}$$

$$\begin{aligned} \Rightarrow \begin{cases} i_s = \frac{5}{3} \text{ A} \\ i_o = 1 \text{ A} \end{cases} & \quad \Rightarrow v_o = 3i_o = 3 \text{ V} \end{aligned}$$

**Finally, check the answer by power balance.**




**Check the answer by power balance:**

$$P_{dissipated} = P_{developed} ???$$




**Example:**

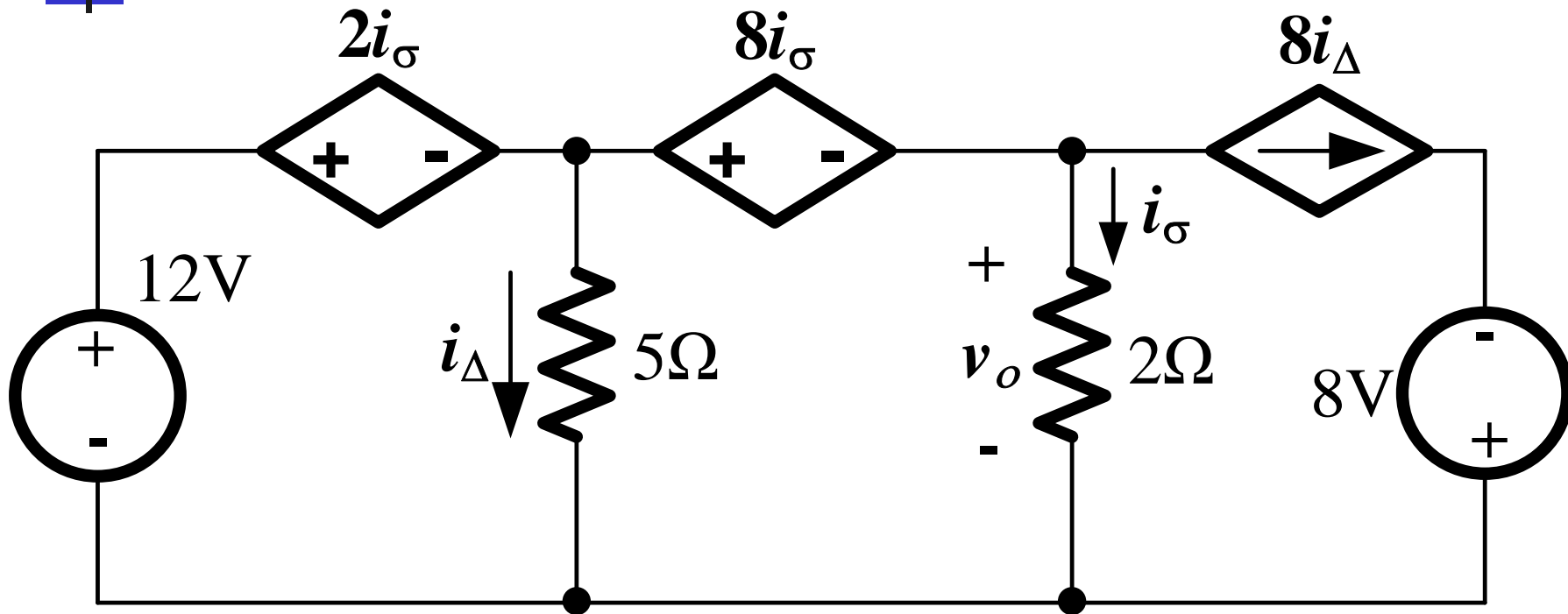**ANS:  $i_{\Delta} = 2\text{A}$ ;  $v_o = 2\text{V}$**



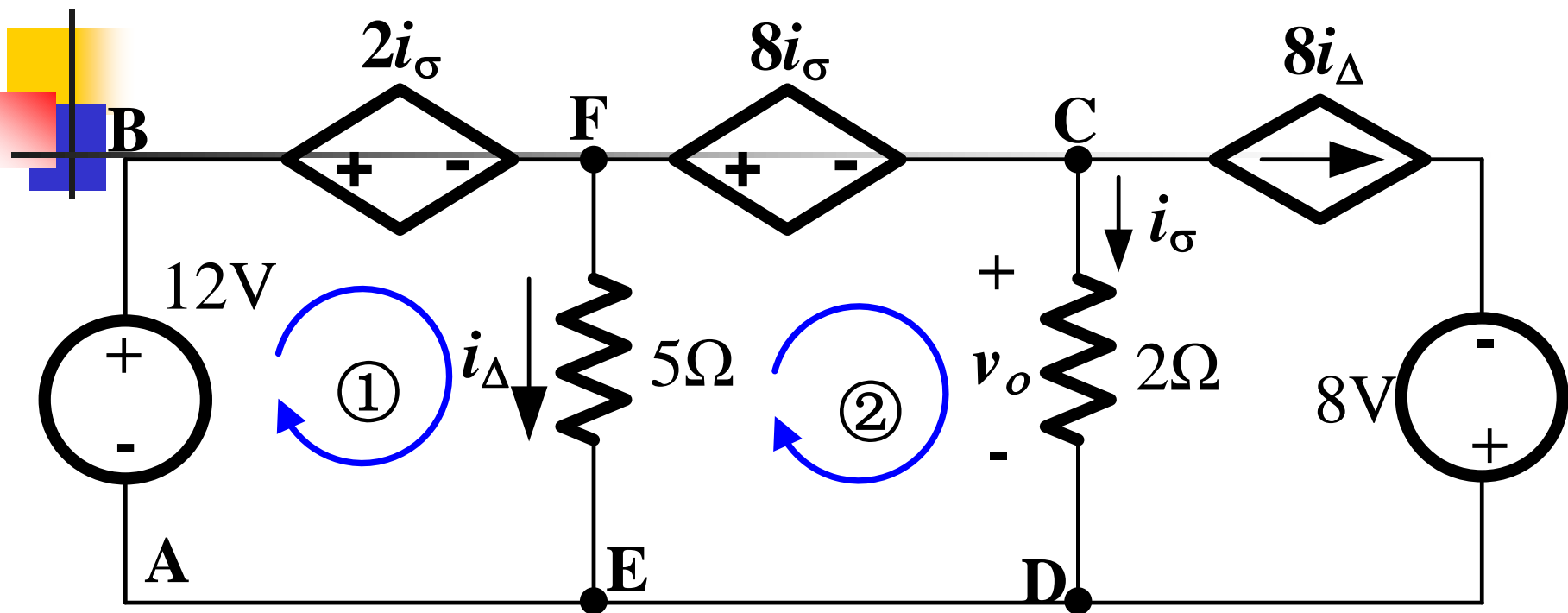**Find the current  $i_{\Delta}$  and voltage  $v_o$ ; and show that the power developed equals the power absorbed.**



对①②使用KVL方程

$$\begin{cases} 12 - 2i_{\sigma} - 5i_{\Delta} = 0 \\ 8i_{\sigma} + 2i_{\sigma} - 5i_{\Delta} = 0 \end{cases} \quad \text{解得} \begin{cases} i_{\sigma} = 1A \\ i_{\Delta} = 2A \end{cases} \quad \text{所以 } v_0 = 2i_{\sigma} = 2V$$

总电流为:  $i_{\Delta} + i_{\sigma} + 8i_{\Delta} = 19A$ , 则电压源  $p_{12V} = 19A \times 12V = 228W$ ,  
 $p_{8V} = 8i_{\Delta} \times 8V = 8 \times 2 \times 8 = 128W$ , 则电压源放出总功率  $356W$ .

其余元件吸收功率分别为:

$$2 \times 19 + 5 \times 2^2 + 8 \times (8 \times 2 + 1) + 2 \times 1 + 8 \times 2 \times (8 + 2) = 356W$$




## **2-3 Resistors in Series and Parallel**

---

- **Resistors in Series**
- **Resistors in parallel**
- **Voltage and current division**
 
# Resistors in Series

In a circuit, all elements carry the **SAME** current are said to be connected in **series**.




For node A, by KCL:

$$i_1 - i_2 = 0$$

**Not only equal!**

$$i_1 = i_2$$

# Resistors in Series

 


$$R_{eq} = \sum_{k=1}^N R_k$$

**(Prove it by using KCL and KVL)**
 
# Resistors in Parallel

In a circuit, all elements have the **SAME** voltage across them are said to be connected in **parallel**.




For Loop **I**, by KVL:

**Not only equal!**

$v_1 = v_2$

# Resistors in Parallel

 


$$\therefore \frac{1}{R_{eq}} = \sum_{k=1}^N \frac{1}{R_k}$$

**(Prove it by using KCL and KVL)**



**A special case:**

 


$$R_{eq} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$



 
# A popular mistake:

$$R_{eq} = R_1 \parallel R_2 \parallel R_3 = \frac{\cancel{R_1 R_2 R_3}}{\cancel{R_1 + R_2 + R_3}}$$



$$R_{eq} = R_1 \parallel R_2 \parallel R_3 = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$


# Voltage Division

 

Generally, for  $N$   
resistors in series:

$$v_k = \frac{R_k}{\sum_{n=1}^N R_n} v_s$$


# Example:

 

$$v_o = \frac{R_{eq}}{R_1 + R_{eq}} v_s$$

$$\left( R_{eq} = \frac{R_2 R_L}{R_2 + R_L} \right)$$

# Current Division

 

$$\begin{cases} i_1 = \frac{R_2}{R_1 + R_2} i_s = \frac{G_1}{G_1 + G_2} i_s \\ i_2 = \frac{R_1}{R_1 + R_2} i_s = \frac{G_2}{G_1 + G_2} i_s \end{cases}$$

**Generally, for  $N$   
resistors in parallel:**

$$i_k = \frac{G_k}{\sum_{n=1}^N G_n} i_s$$



# Summary of Chapter 2

---

- Ohm's Law with and w/o PSC
- Node, Loop, Mesh, .....
- **KCL and KVL**
- **Simple circuits analysis containing CS**
- Resistors in Series and in Parallel



# Primary Goals of Chapter 2

---

**In this chapter, we seek to develop our:**

- **Ability to implement Ohm's Law;**
- **Ability to use Kirchhoff's Laws (KCL & KVL);**
- **Skills in analyzing simple circuits containing dependent sources.**