



Introduction to Electronic Systems

Zheng Feng



Part 2: Dynamic Circuit Analysis

5. Capacitors and Inductors

**6. Response of First-order RC
and RL Circuits**

7. Response of Second-order RLC
Circuits*



Chapter 6

- **RC and RL Circuits**
- **Initial Values**
- **Natural Response of RC/RL Circuits**
- **Step Response of RC/RL Circuits**
- **General Solution Method**
- **Sequential Switching**
- **Integrating Amplifier**



Mathematical Fundamentals

- **First-order Differential Equation**

- **Complex Number**



6-1 RC and RL Circuits



- **What is RC and RL Circuits?**
- **What is Natural Response?**
- **What is Step Response?**



RC and RL Circuits



- Circuit that consists of sources, resistors, and **either (but not both) inductor or capacitor** is called first-order RC or RL circuit;
- RC: Resistor-Capacitor
- RL: Resistor-Inductor

Natural Response

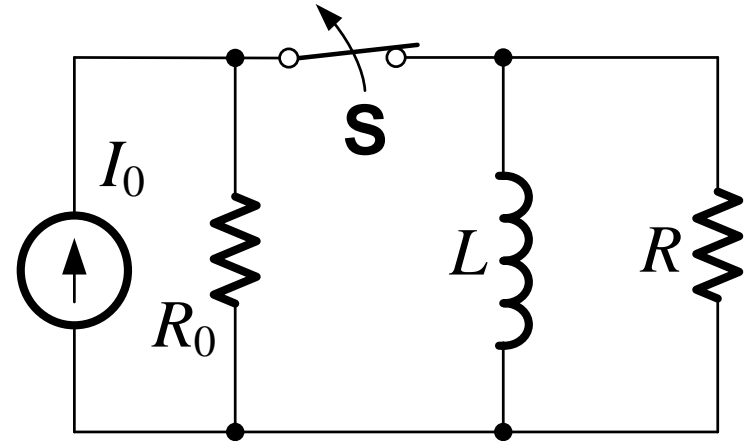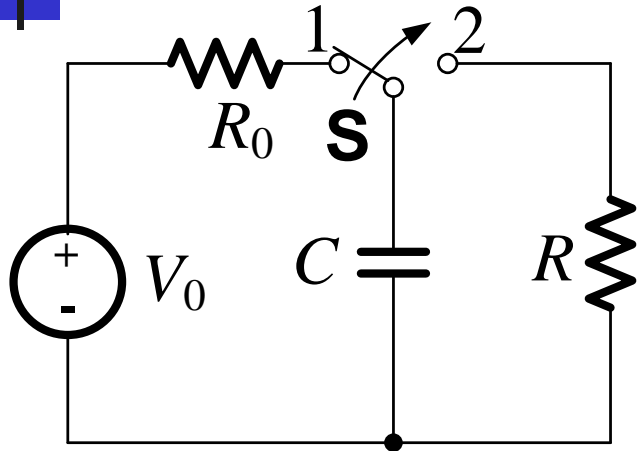



- The capacitor/inductor is abruptly disconnected from its source;
- Energy stored in the capacitor/inductor is released to a resistive network.

Natural Response

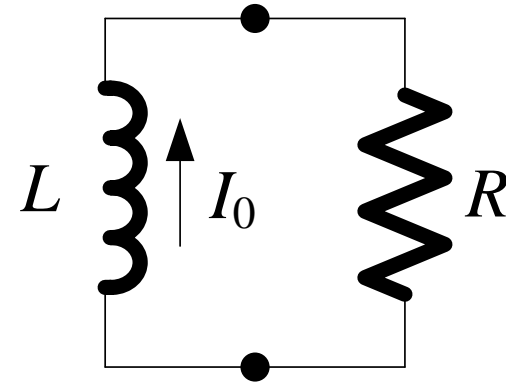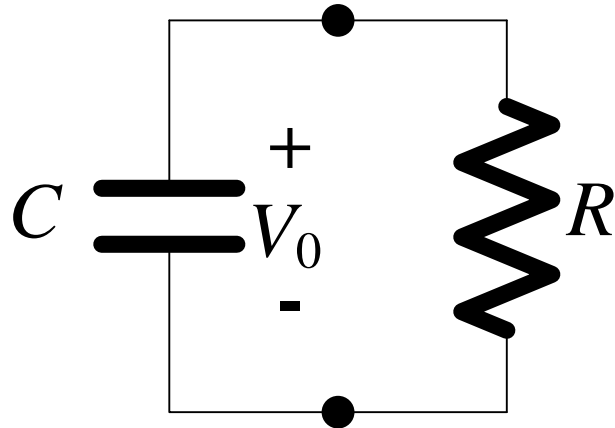



- The voltages and currents arising in the circuit are referred to as the **Natural Response**;
- The circuit behavior is determined by the **circuit itself**, but not the external source excitation.

Step Response

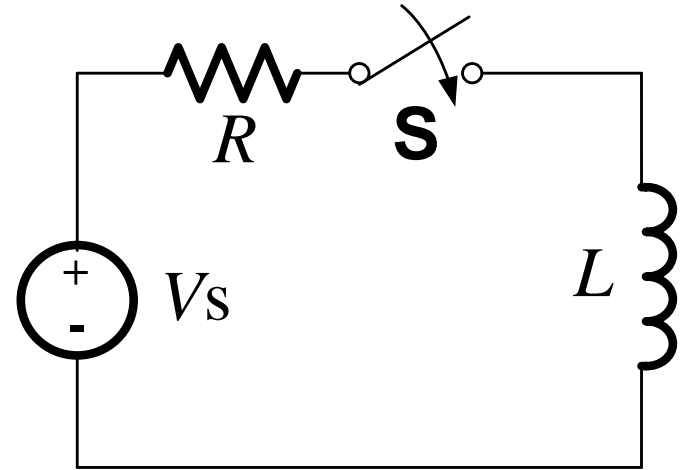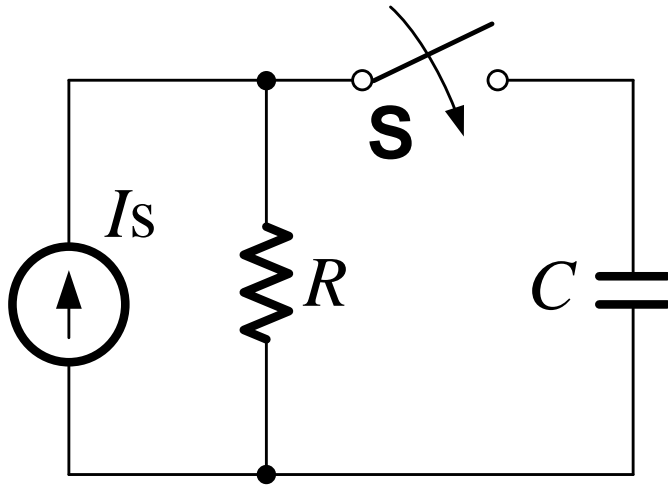





- The voltage or current source is suddenly applied to the capacitor/inductor;
- Energy is acquired by the capacitor/inductor.

Step Response

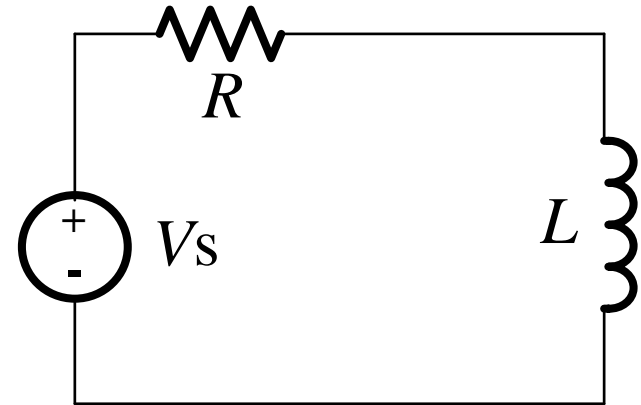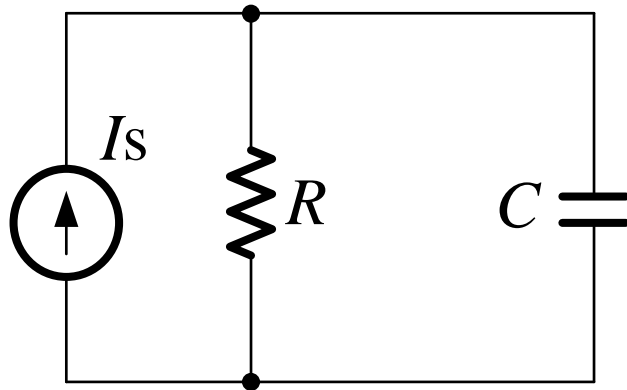

- The voltages and currents arising in the circuit are referred to as the **Step Response**;
- The circuit behavior is determined **both by the circuit itself, and the external source excitation.**

RC and RL Circuits with Source

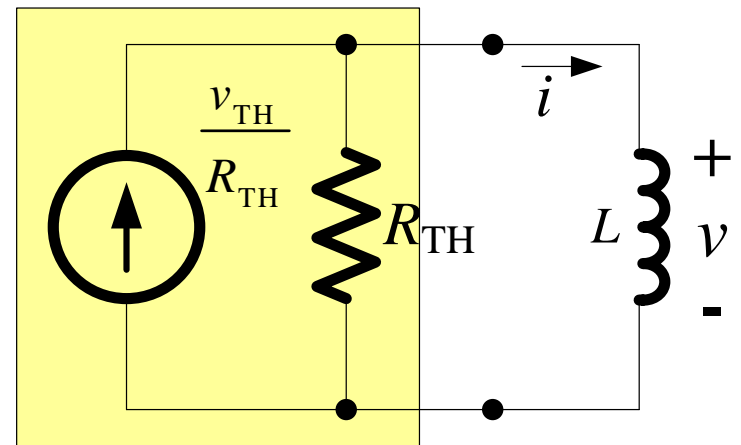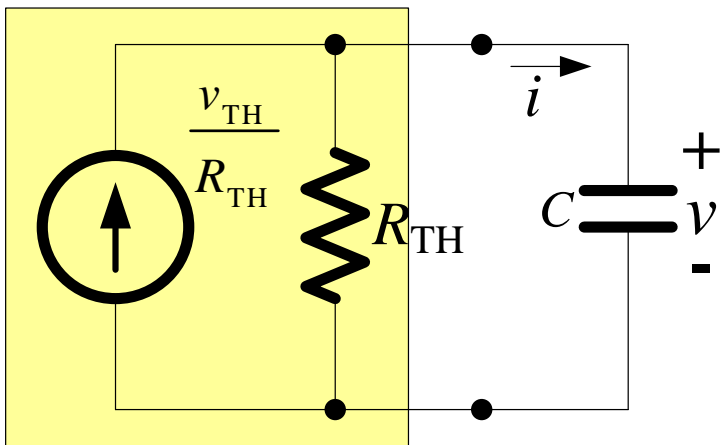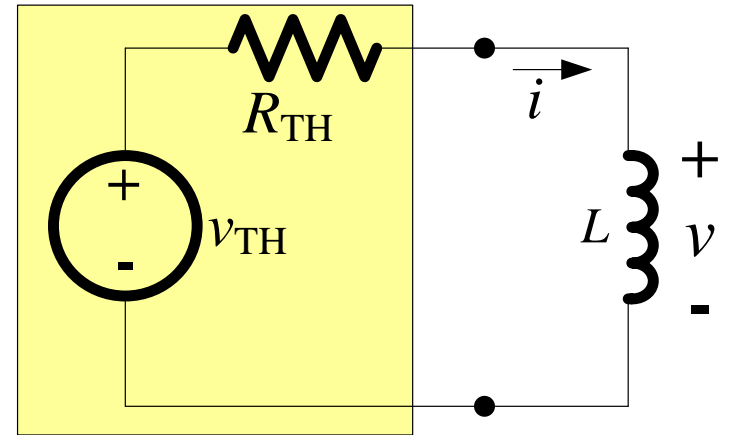
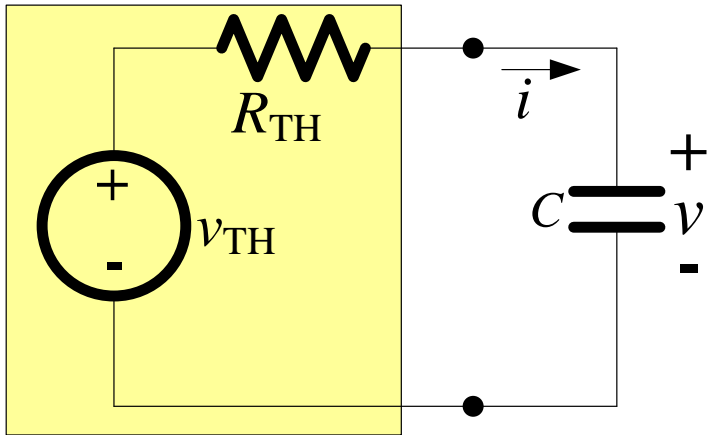




6-2 Initial Values

- **Switching Time**
- **Switching Theorem**
- **Method for Initial Values**

Switching Time

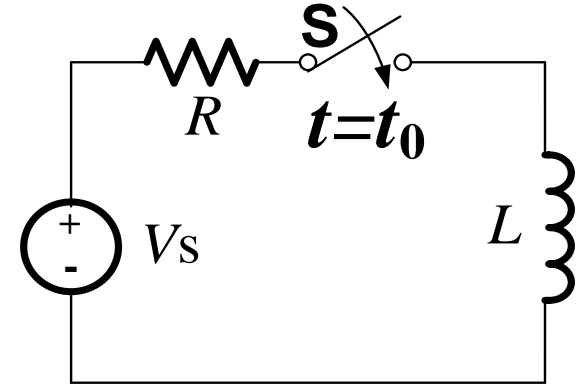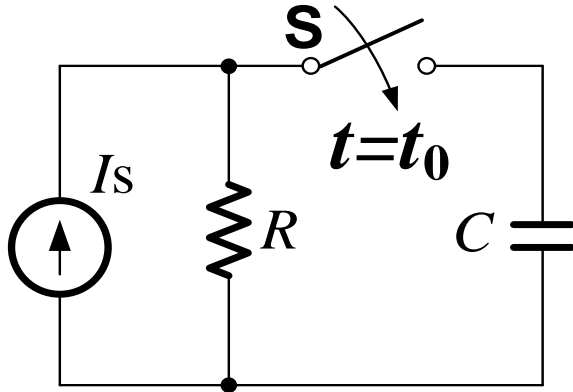

- Circuit is switched at the time of t_0 ;
- t_0^- denote the time just prior to switching;
- t_0^+ denote the time immediately following switching.



Switching Time

$$u_C(t_0^-), \quad i_C(t_0^-), \quad u_L(t_0^-), \quad i_L(t_0^-)$$

- denote the voltages and currents at the time just prior to switching (at the time t_0^-);



Switching Time

$$u_C(t_0^+), \quad i_C(t_0^+), \quad u_L(t_0^+), \quad i_L(t_0^+)$$

- denote the voltages and currents at the time immediately following switching (at the time t_0^+);
- are referred to as the initial values (initial voltage or initial current) of the circuits.



Switching Theorem

For a capacitor, $i(t) = C \frac{du(t)}{dt}$

If $i(t)$ is limited, then $u(t)$ is **continuous**.

$$u_C(t_0^-) = u_C(t_0^+)$$

■ Specially, if $t_0=0$, $u_C(0^+) = u_C(0^-)$



Switching Theorem

For an inductor, $u(t) = L \frac{di(t)}{dt}$

If $u(t)$ is limited, then $i(t)$ is **continuous**.

$$i_L(t_0^-) = i_L(t_0^+)$$

■ Specially, if $t_0=0$, $i_L(0^+) = i_L(0^-)$



Method for Initial Values

■ Initial values:

● Independent initial values:

$$u_C(0^+), \quad i_L(0^+)$$

● Other dependent initial values:

$$i_C(0^+), \quad u_L(0^+) \dots\dots$$




Method for Initial Values

■ Steps for initial values:

1. Find the values of $u_C(0^-)$, $i_L(0^-)$
2. Find independent initial values by switching theorem: $u_C(0^+)$, $i_L(0^+)$
3. Redraw the circuit for $t=0^+$;
4. Find other dependent initial values by KCL and KVL.

Example

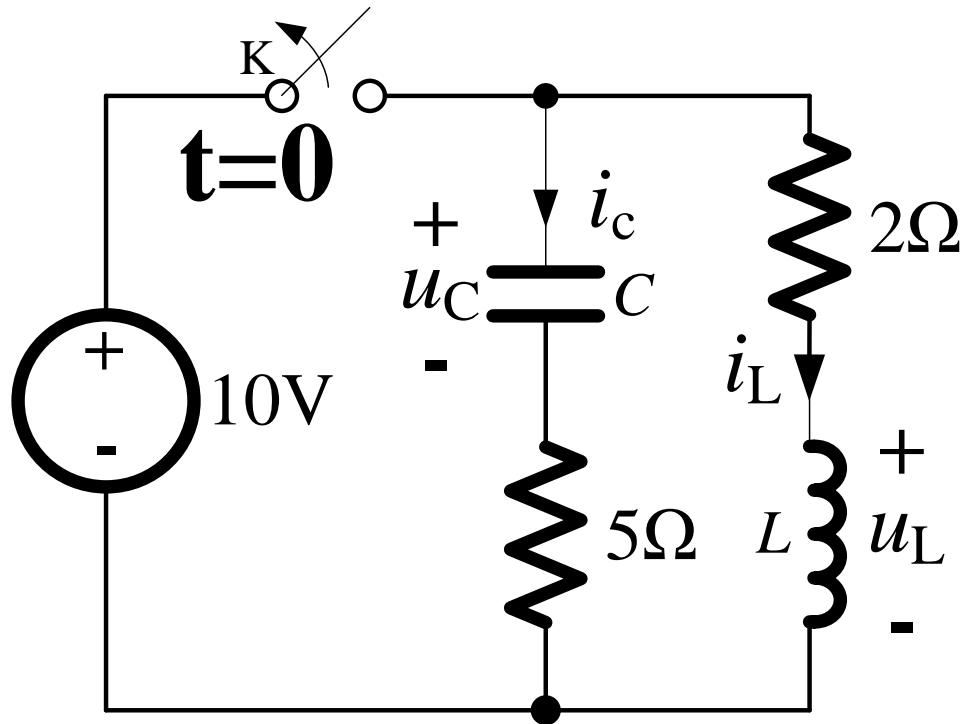

The switch has been closed **for a long time**, and is opened at $t = 0$. Find $u_C(0^+)$ and $i_L(0^+)$.




Analysis:

- $u_C(t)$ and $i_L(t)$ are continuous;
- The circuit is switched at $t=0$;
- $u_C(0^+) = u_C(0^-)$ and $i_L(0^+) = i_L(0^-)$;
- At the time of $t=0^-$, the switch has been closed for a long time;
- For DC source, capacitor is **OPEN**, and inductor is **SHORT**.

Solution:

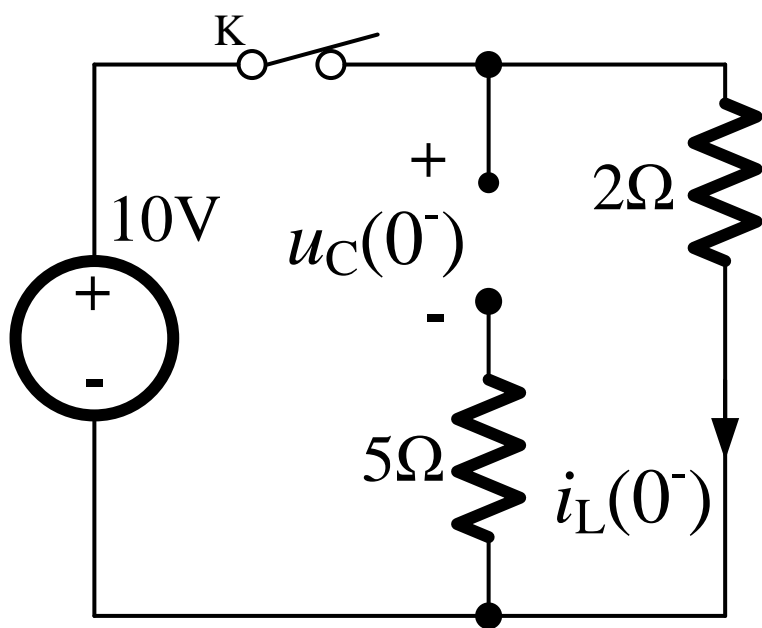
At the time of $t=0^-$, the equivalent circuit is:



$$\begin{cases} u_C(0^-) = 10V \\ i_L(0^-) = 5A \end{cases}$$

$$\begin{cases} u_C(0^+) = u_C(0^-) = 10V \\ i_L(0^+) = i_L(0^-) = 5A \end{cases}$$


Example

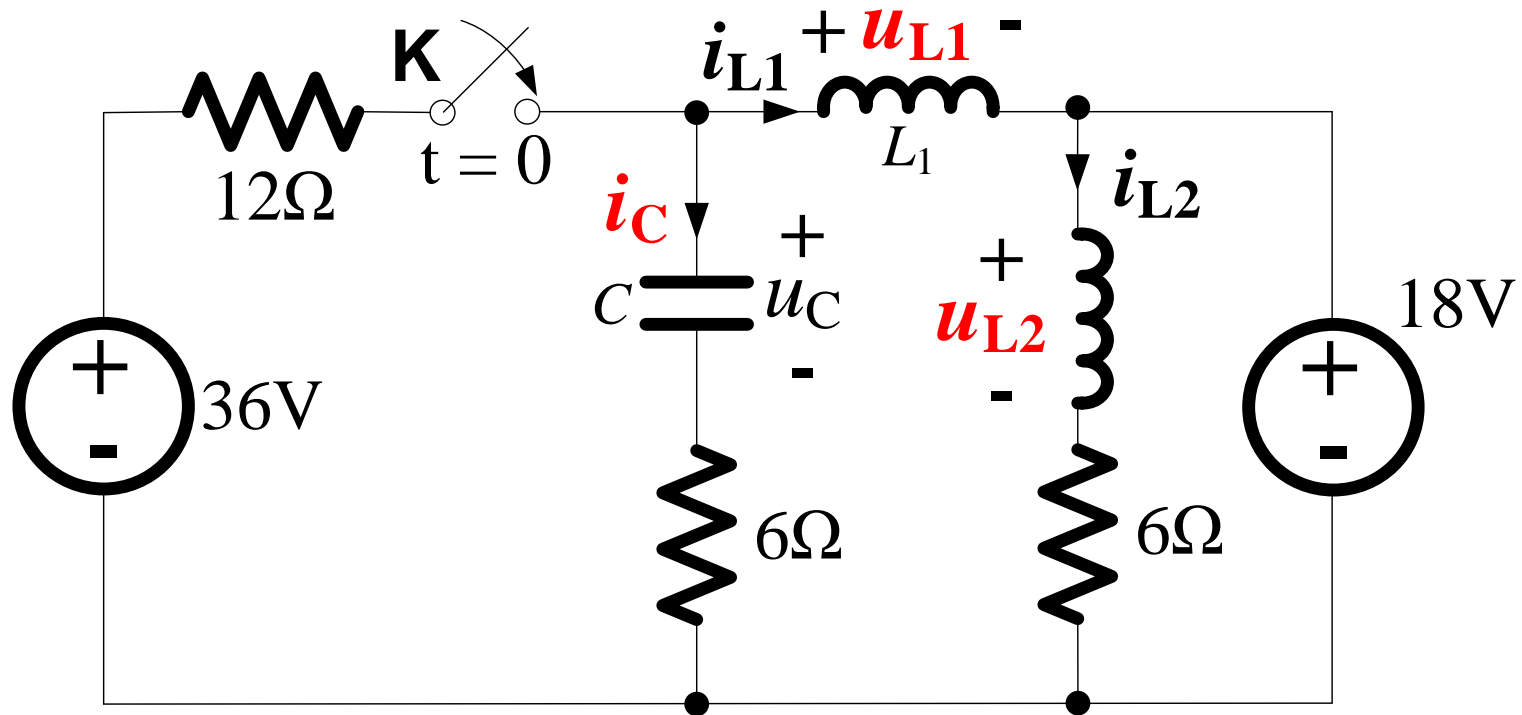

The switch K has been opened for a long time, and is closed at $t=0$. Find $i_C(0^+)$, $u_{L1}(0^+)$, and $u_{L2}(0^+)$.

Solution:

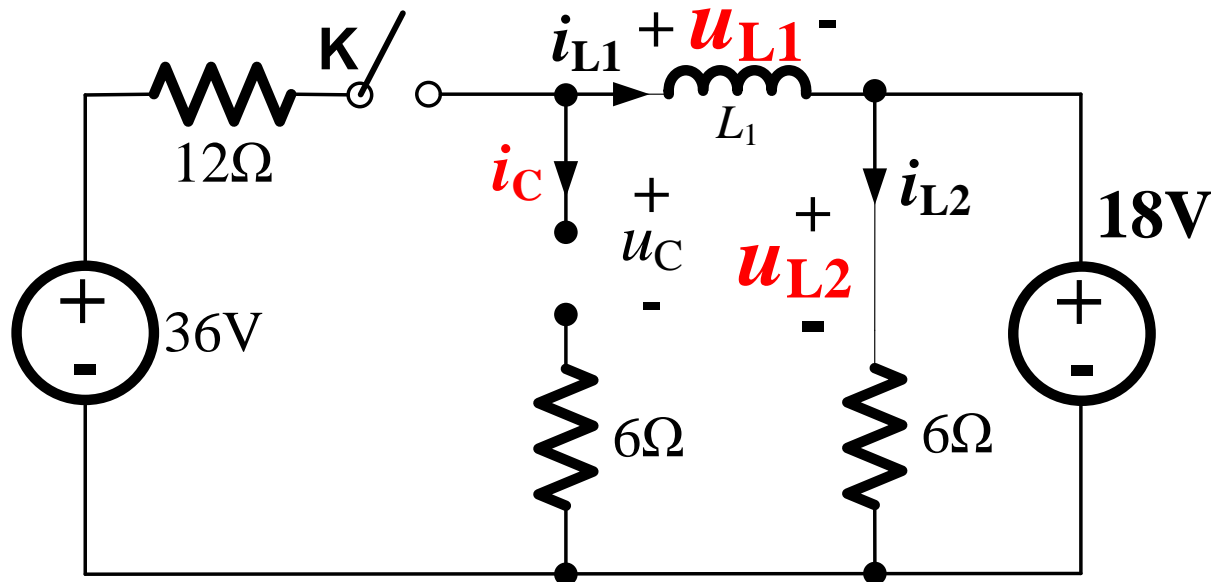At the time of $t=0^-$, the equivalent circuit is:



$$\begin{cases} i_{L1}(0^-) = 0A \\ i_{L2}(0^-) = 3A \\ u_C(0^-) = 18V \end{cases}$$





At $t=0^+$, by switching theorem, we have:

$$\begin{cases} i_{L1}(0^+) = i_{L1}(0^-) = 0A \\ i_{L2}(0^+) = i_{L2}(0^-) = 3A \\ u_C(0^+) = u_C(0^-) = 18V \end{cases}$$



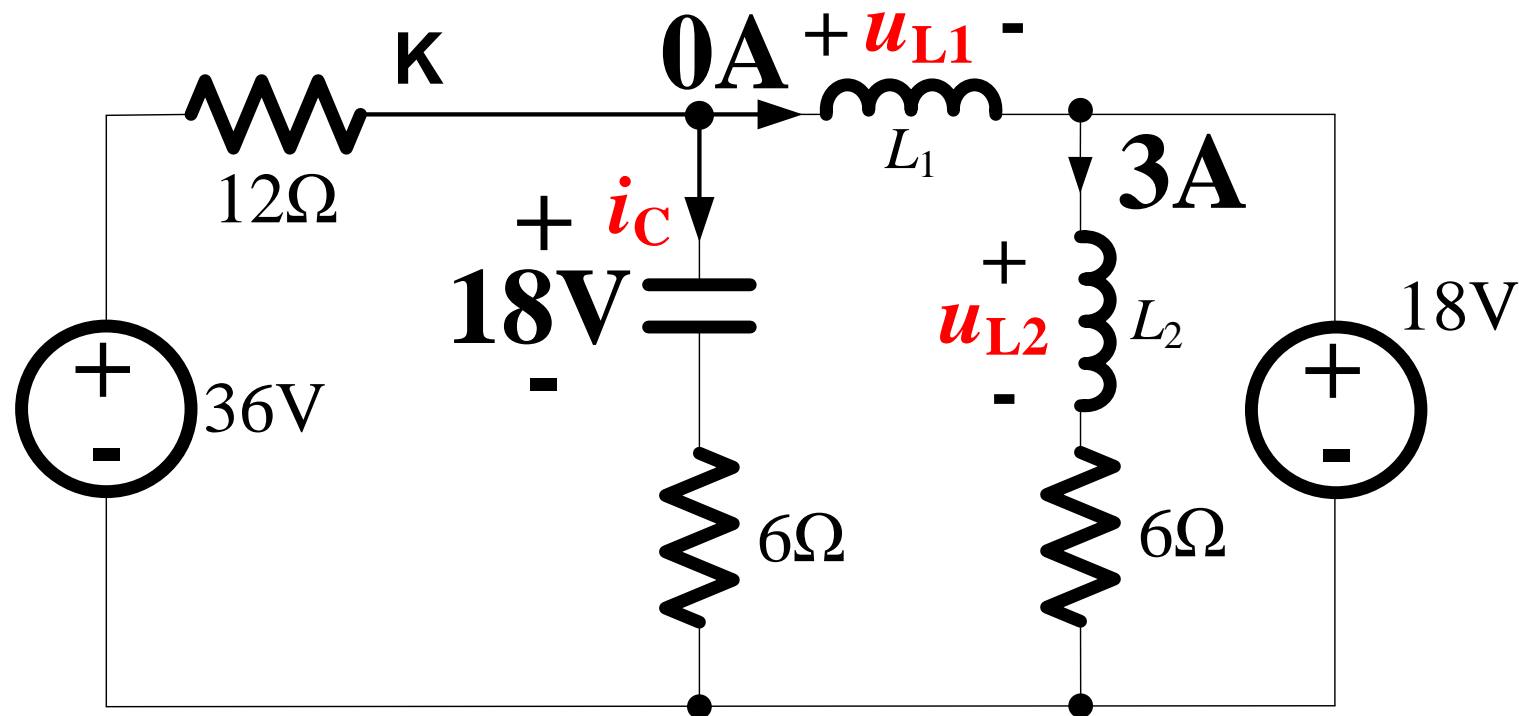
Then, the circuit can be redrawn for $t=0^+$:



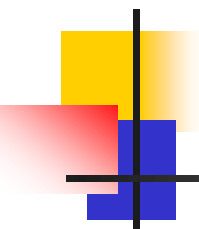


At $t=0^+$, by KVL we have:
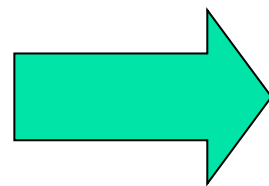
$$\begin{cases} (12 + 6)i_C(0^+) + 18 - 36 = 0 \\ 12i_C(0^+) + u_{L1}(0^+) + 18 - 36 = 0 \\ u_{L2}(0^+) + 18 = 18 \end{cases}$$



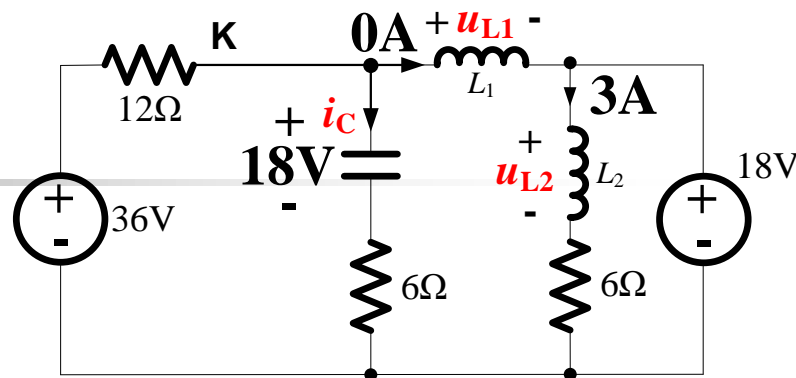
$$\begin{cases} i_C(0^+) = 1A \\ u_{L1}(0^+) = 6V \\ u_{L2}(0^+) = 0V \end{cases}$$



Exercise

ANS:

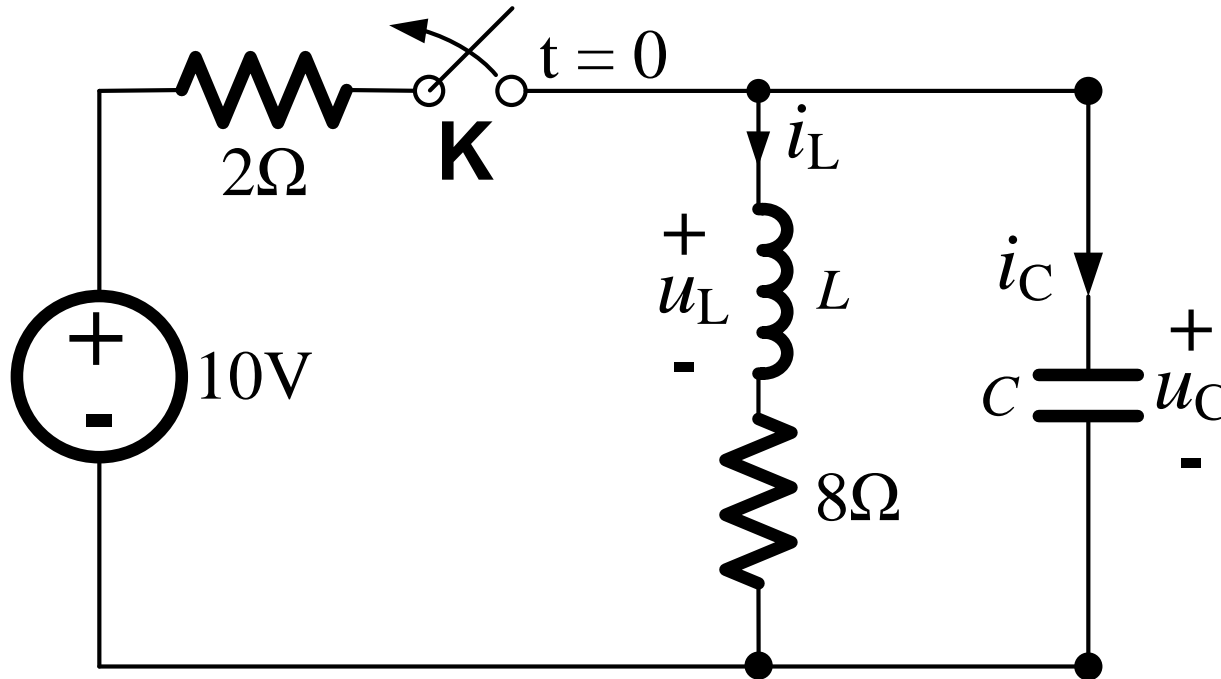

$$\left\{ \begin{array}{l} i_L(0^+) = 1\text{A} \\ u_C(0^+) = 8\text{V} \\ i_C(0^+) = -1\text{A} \\ u_L(0^+) = 0\text{V} \\ i_R(0^+) = 1\text{A} \\ u_R(0^+) = 8\text{V} \end{array} \right.$$


The switch K has been closed for a long time, and is opened at $t=0$. Find initial value for all elements.



6-3 Natural Response

- **Natural Response of RC Circuits**
- **Natural Response of RL Circuits**

Natural Response of RC Circuits

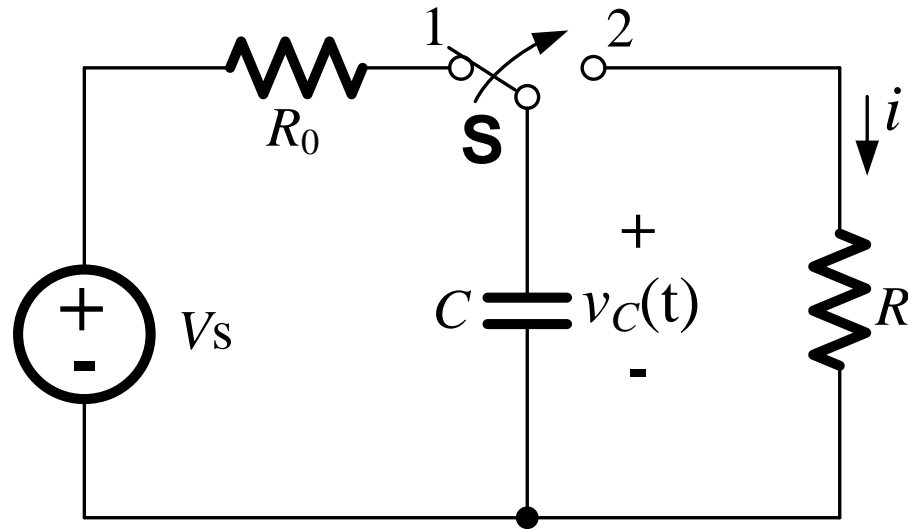


$$\begin{cases} v_C(0^-) = V_s \\ i_C(0^-) = 0 \end{cases}$$

- The switch has been in the position 1 for a long time;
- The switch is moved to 2 at $t=0$;
- Energy stored in *capacitor* is suddenly released to R .

Natural Response of RC Circuits


■ By Node-Voltage method:
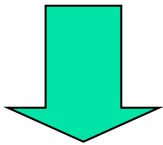
$$C \frac{dv_C}{dt} + \frac{v_C}{R} = 0$$



$$\frac{dv_C}{v_C} = -\frac{1}{RC} dt$$
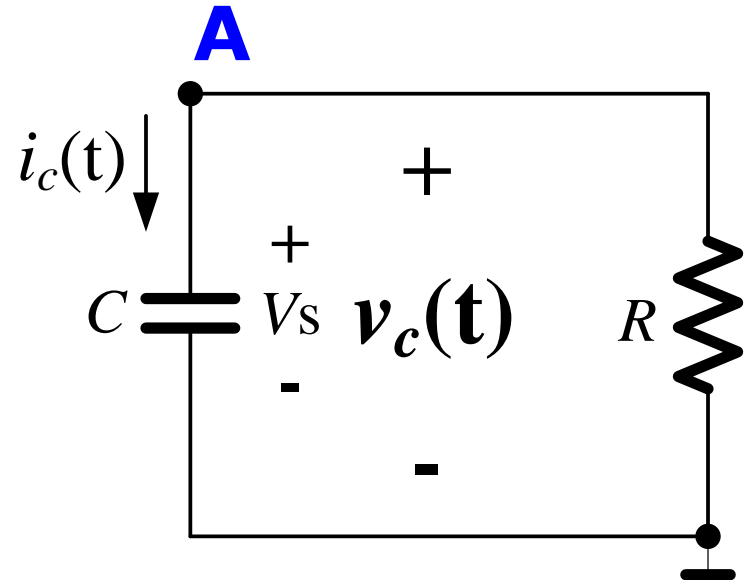
$$\Rightarrow v_C(t) = Ke^{-t/RC}, \quad t \geq 0$$





Natural Response of RC Circuits

$$v_C(t) = Ke^{-t/RC}, \quad t \geq 0$$

$$v_C(0^+) = v_C(0^-) = V_s$$

$$v_C(t) = V_s e^{-t/RC}, \quad t \geq 0$$



Natural Response of RC Circuits


■ The current through the capacitor:

$$i_C(t) = -\frac{v_C(t)}{R} = -\frac{V_s}{R} e^{-t/RC}, \quad t \geq 0^+$$

$$i_C(0^+) = -V_s/R$$

$$i_C(0^-) = 0 \quad \Rightarrow \quad i_C(0^+) \neq i_C(0^-)$$


Natural Response of RC Circuits

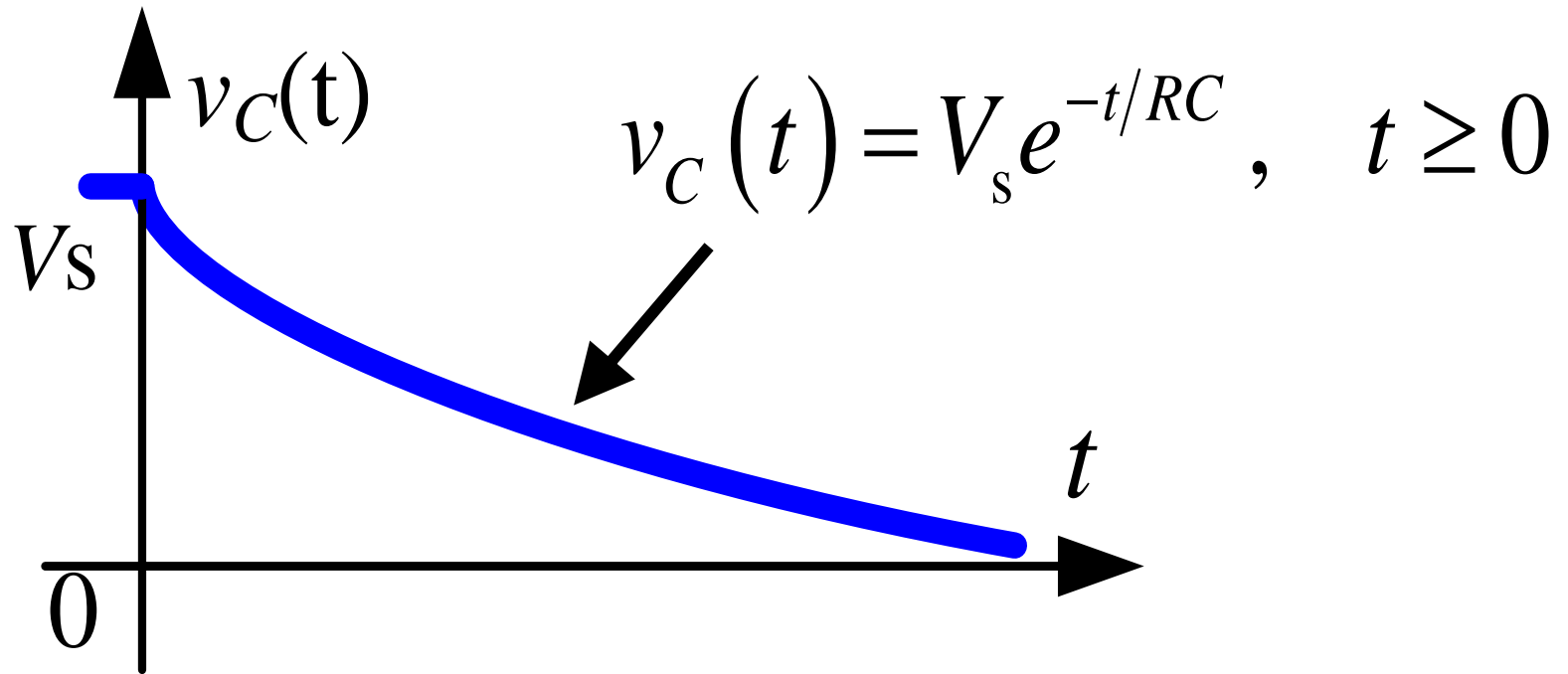

The voltage across the capacitor

Natural Response of RC Circuits

The current through the capacitor:

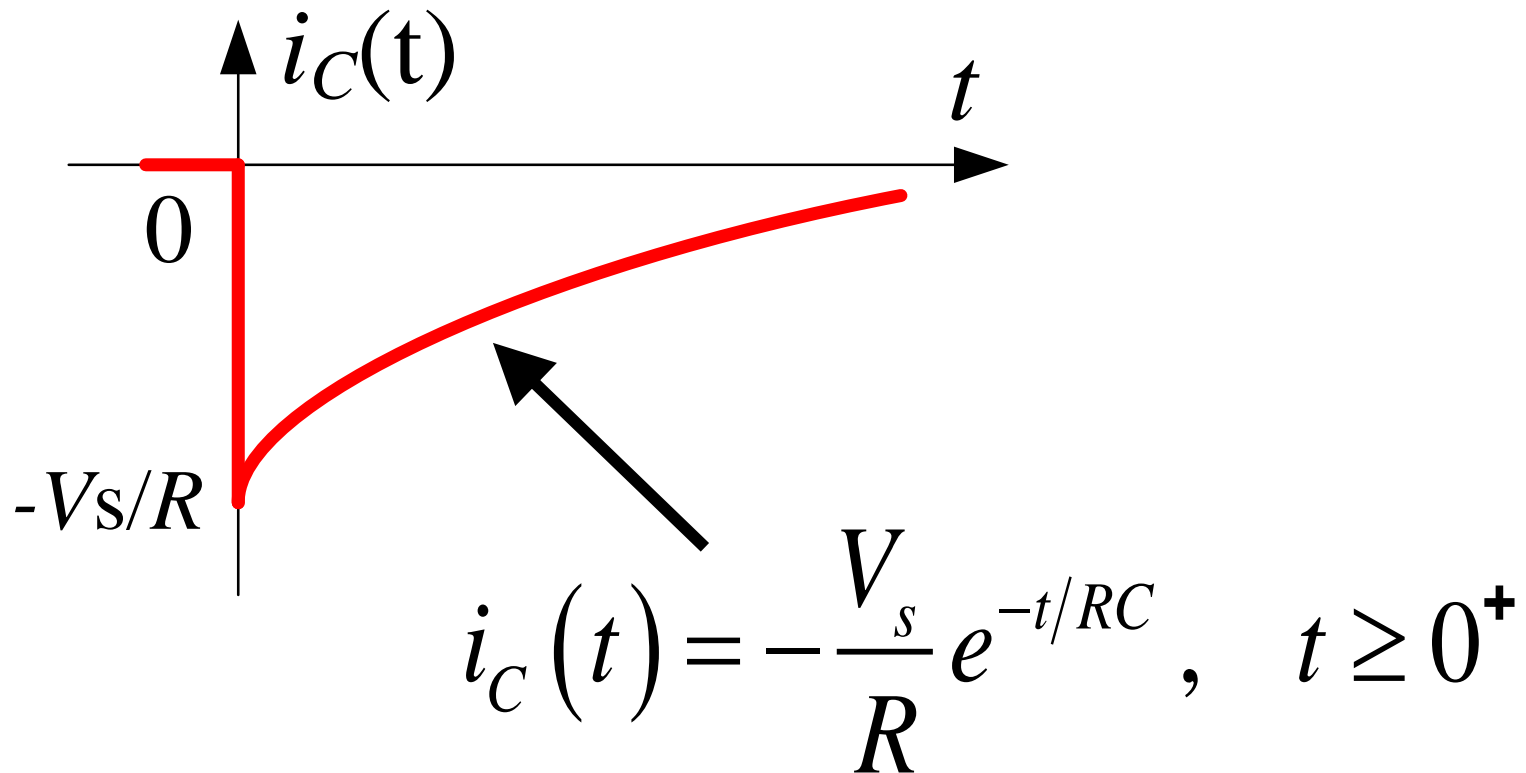



Voltage across the capacitor:

$$v_C(t) = V_s e^{-t/RC}, \quad t \geq 0$$

Current through the capacitor:

$$i_C(t) = -(V_s/R) e^{-t/RC}, \quad t \geq 0^+$$



Power delivered to the capacitor:


$$p_C(t) = v_C i_C = -\left(V_s^2 / R\right) e^{-2t/RC}, \quad t \geq 0^+$$

Energy stored in the capacitor:

$$w_C(t) = \int_0^t p_C(t) dt = \frac{1}{2} C V_s^2 \left(e^{-2t/RC} - 1 \right), \quad t \geq 0$$

$$w_C(t) = -\frac{1}{2} C V_s^2, \quad t \rightarrow \infty$$

Time Constant

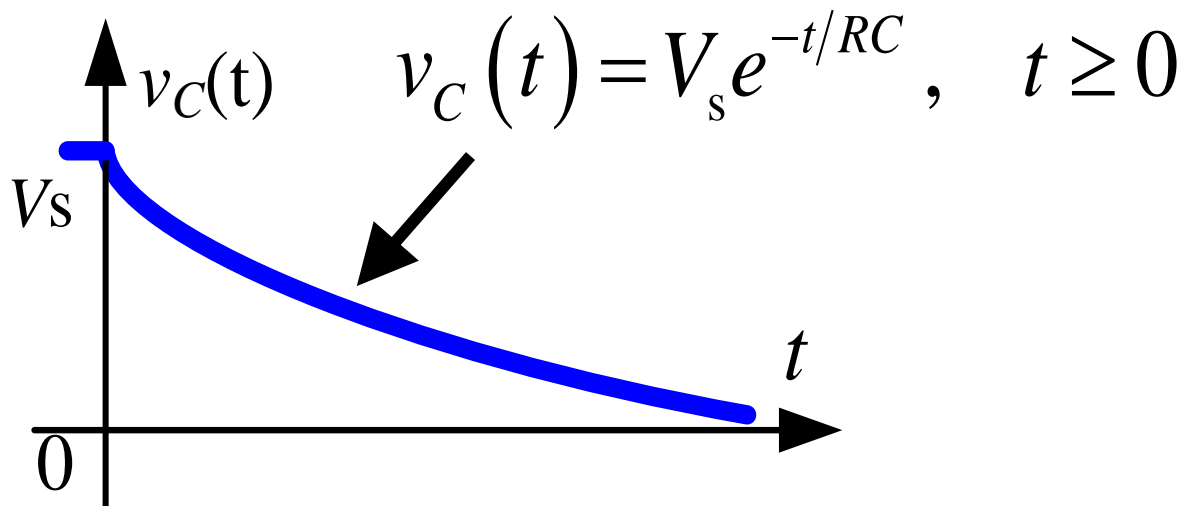


Time Constant: $\tau = RC$

- **Time Constant: Rate at which the capacitive voltage approaches zero.**


Time Constant
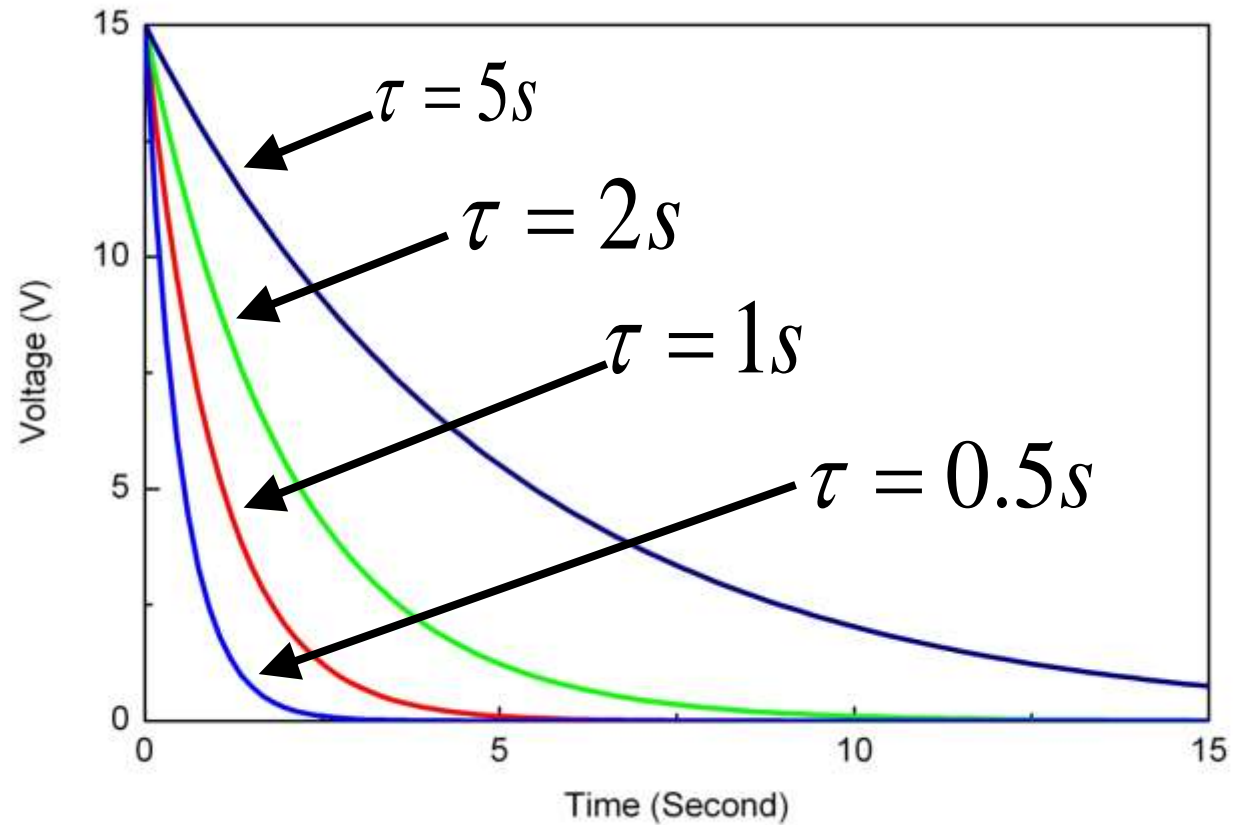
$$v_C(t) = V_s e^{-t/\tau}, \quad t \geq 0$$



Time Constant

$$\tau = RC$$

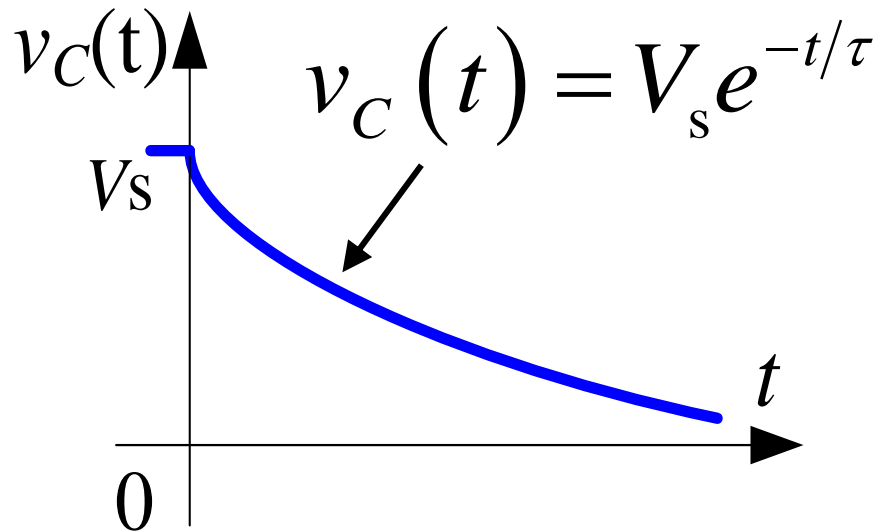

- Transient response
- Steady-state response

$$t=\tau: \quad v = 0.368 V_s$$

$$t=2\tau: \quad v = 0.135 V_s$$

$$t=3\tau: \quad v = 0.050 V_s$$

$$t=4\tau: \quad v = 0.018 V_s$$

$$t=5\tau: \quad v = 0.007 V_s$$

.....

$$t=\infty: \quad v = 0$$



Time Constant

Voltage: $v_C(t) = V_s e^{-t/\tau}, \quad t \geq 0$

Current: $i_C(t) = -(V_s/R) e^{-t/\tau}, \quad t \geq 0^+$

Power: $p_C(t) = -(V_s^2/R) e^{-2t/\tau}, \quad t \geq 0^+$

Energy: $w_C(t) = \frac{1}{2} C V_s^2 (e^{-2t/\tau} - 1), \quad t \geq 0$



Steps for find natural response of RC circuit

1. Find the initial voltage across the capacitor;
2. Find the time constant of the RC circuit:

$$\tau = R_{TH} C_{eq}$$

3. Use the following equation to get the natural response of RC circuit:

$$v_C(t) = v(0^+) e^{-t/\tau}, \quad t \geq 0$$




First-Order RC Circuit

$$\tau = R_{TH} C_{eq}$$

- R_{TH} is the Thévenin Equivalent resistance between the two terminals of the capacitor;
- C_{eq} is the equivalent capacitance (If multiple capacitors exist, they must be interconnected in such a way that they can be replaced by a single equivalent capacitor).

Natural Response of RL Circuits

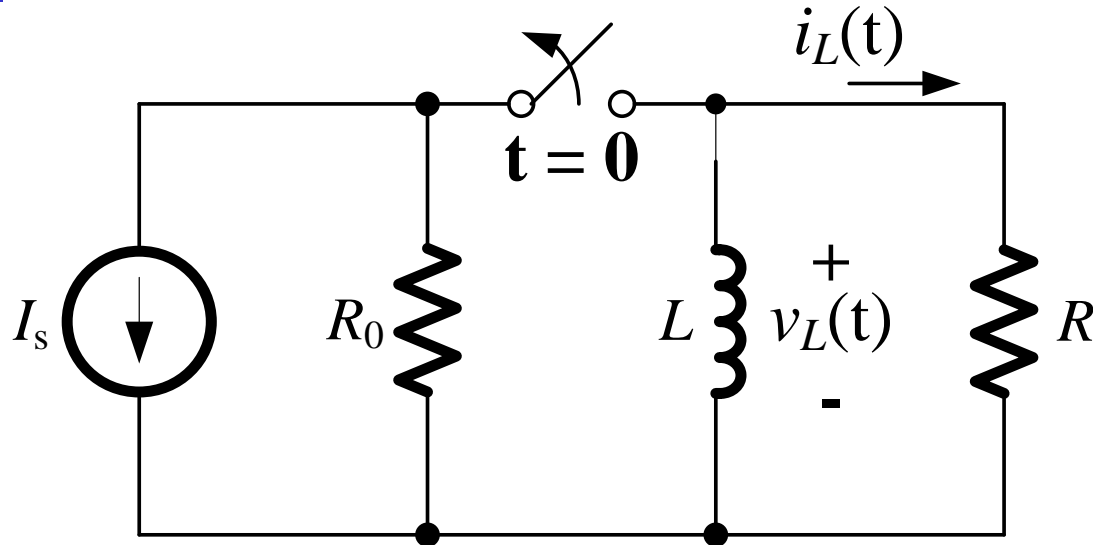

$$\begin{cases} i_L(0^-) = I_s \\ v_L(0^-) = 0 \end{cases}$$

- The switch has been closed for a long time;
- The switch is opened at the instant of $t = 0$;
- Energy stored in L is suddenly released to R .


Natural Response of RL Circuits

■ By KVL for the loop:

$$L \frac{di_L}{dt} + Ri_L = 0$$

$$\frac{di_L}{i_L} = -\frac{R}{L} dt$$
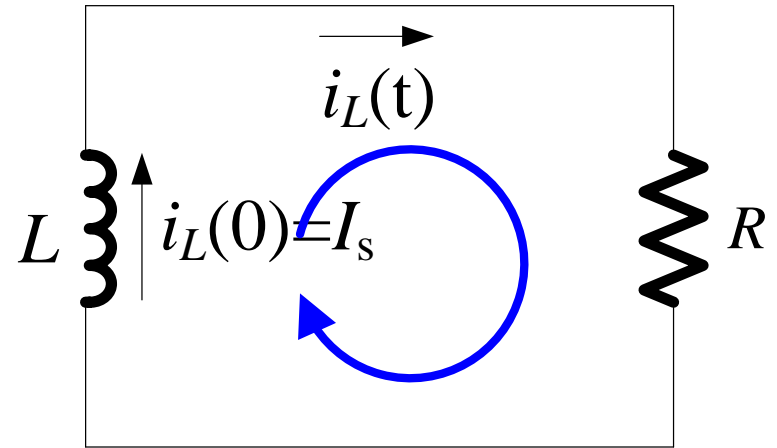
$$i_L(t) = Ke^{-(R/L)t}, \quad t \geq 0$$





Natural Response of RL Circuits

$$i_L(t) = Ke^{-(R/L)t}, \quad t \geq 0$$

$$i_L(0^+) = i_L(0^-) = I_s$$

$$i_L(t) = I_s e^{-(R/L)t}, \quad t \geq 0$$

Natural Response of RL Circuits


■ The voltage across the inductor:

$$v_L(t) = -Ri_L(t) = -RI_s e^{-(R/L)t}, \quad t \geq 0^+$$

$$v_L(0^+) = -RI_s$$

$$v_L(0^-) = 0 \quad \Rightarrow \quad v_L(0^+) \neq v_L(0^-)$$

Natural Response of RL Circuits

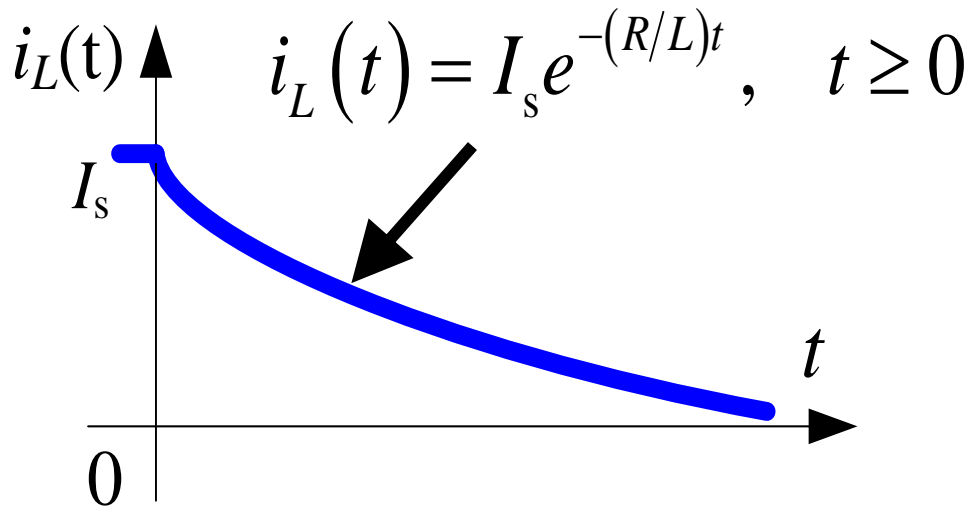

Time Constant :


$$\tau = \frac{L}{R}$$

The current through the inductor

- **Time Constant: Rate at which the inductive current approaches zero.**

Natural Response of RL Circuits

The voltage across the inductor:

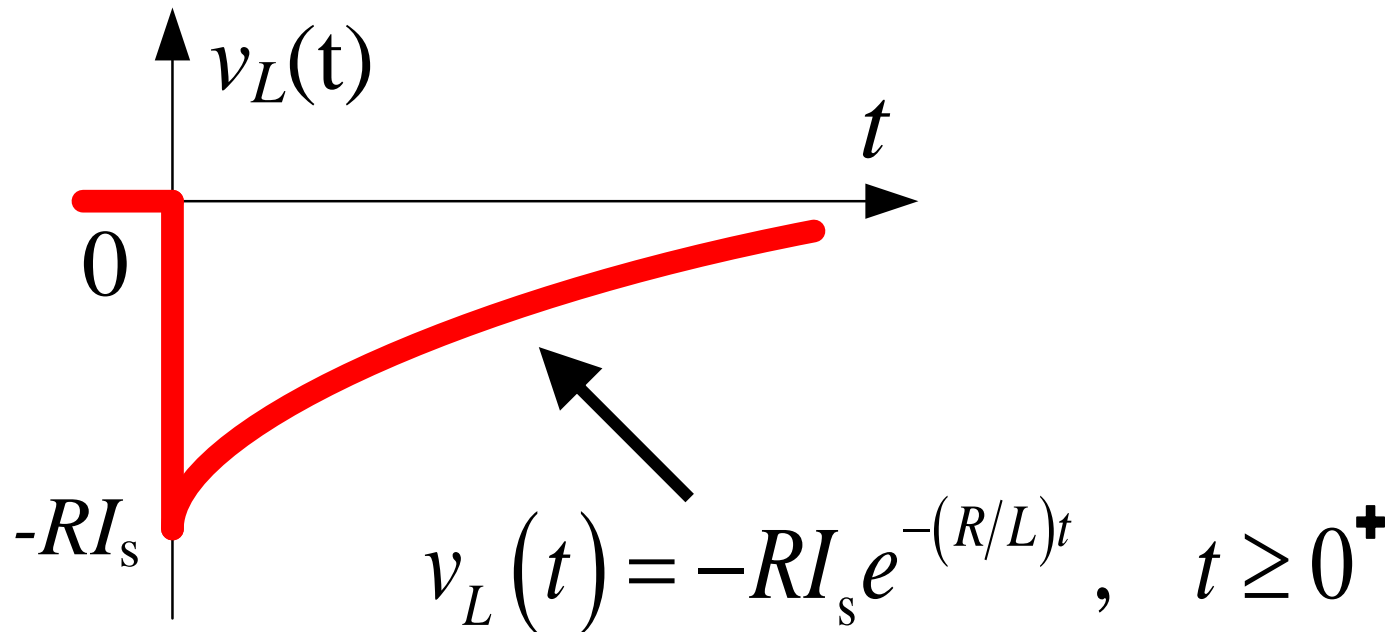



Time Constant

Current: $i_L(t) = I_s e^{-t/\tau}, \quad t \geq 0$

Voltage: $v_L(t) = -RI_s e^{-t/\tau}, \quad t \geq 0^+$

Power: $p_L(t) = RI_s^2 e^{-2t/\tau}, \quad t \geq 0^+$

Energy: $w_L(t) = \frac{1}{2} LI_s^2 (e^{-2t/\tau} - 1), \quad t \geq 0$



Steps for find natural response of RL circuit

1. Find the initial current through the inductor;
2. Find the time constant of the RL circuit:

$$\tau = L_{eq} / R_{TH}$$

3. Use the following equation to get the natural response of RL circuit:

$$i_L(t) = i(0^+) e^{-t/\tau}, \quad t \geq 0$$



First-Order RL Circuit

$$\tau = L_{eq} / R_{TH}$$


- R_{TH} is the Thévenin Equivalent resistance between the two terminals of the inductor;
- L_{eq} is the equivalent inductance (If multiple inductors exist, they must be interconnected so that they must be replaced by a single equivalent inductor).



6-4 Step Response

- **Step Response of RC Circuits**
- **Step Response of RL Circuits**

Step Response of RC Circuits

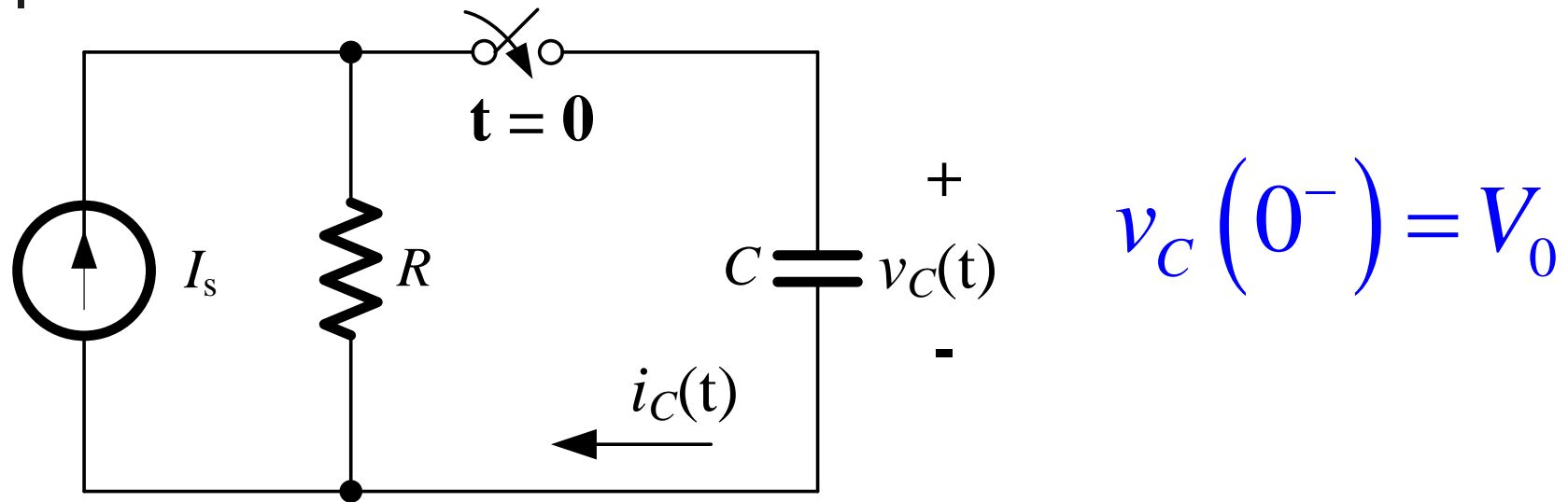

- The capacitor has a initial voltage V_0 ;
- The switch is closed at $t = 0$;
- Energy is being stored in the capacitor.

Step Response of RC Circuits


■ By KCL at node A:

$$C \frac{dv_C}{dt} + \frac{v_C}{R} = I_s$$

$$\frac{dv_C}{v_C - RI_s} = -\frac{1}{RC} dt$$



$$v_C(0^-) = V_0$$
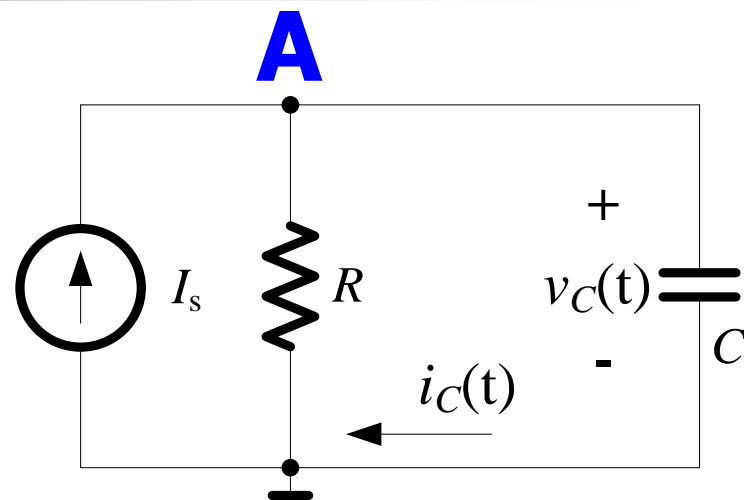
$$v_C(t) = I_s R + (V_0 - I_s R) e^{-t/RC}, \quad t \geq 0$$



Voltage across the capacitor:
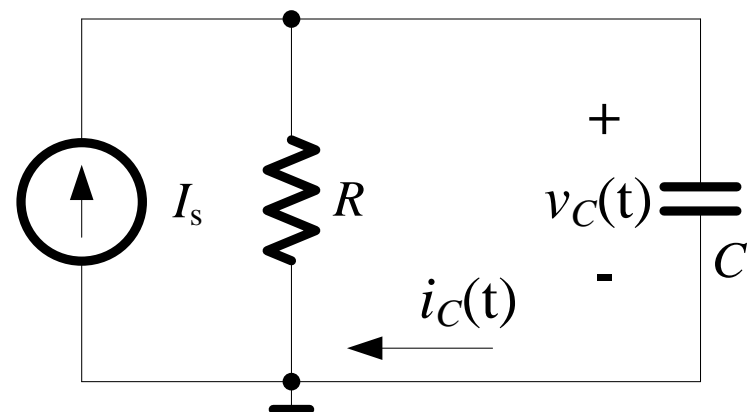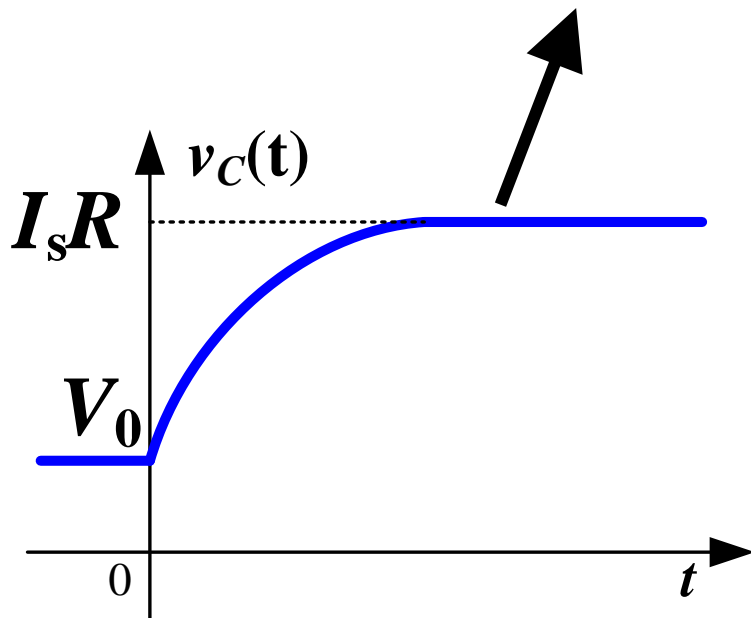
$$v_C(t) = I_s R + (V_0 - I_s R) e^{-t/RC}, \quad t \geq 0$$




$$\tau = RC$$

$$v_C(t) = I_s R + (V_0 - I_s R) e^{-t/\tau}, \quad t \geq 0$$

Another Method to Find $i_C(t)$

■ By KCL at node A:

$$i_C(t) + \frac{v_C(t)}{R} = I_s$$

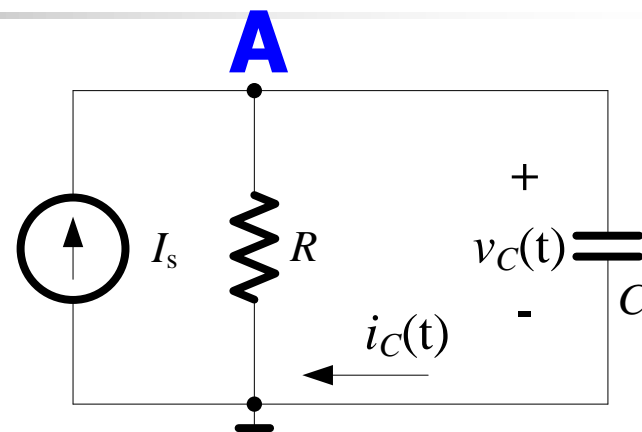


$$\frac{di_C(t)}{dt} = -\frac{1}{RC}i_C(t) \quad \begin{cases} v_C(0^+) = v_C(0^-) = V_0 \\ i_C(0^+) = I_s - V_0/R \end{cases}$$


$$i_C(t) = (I_s - V_0/R)e^{-t/RC}, \quad t \geq 0^+$$

Current through the capacitor:
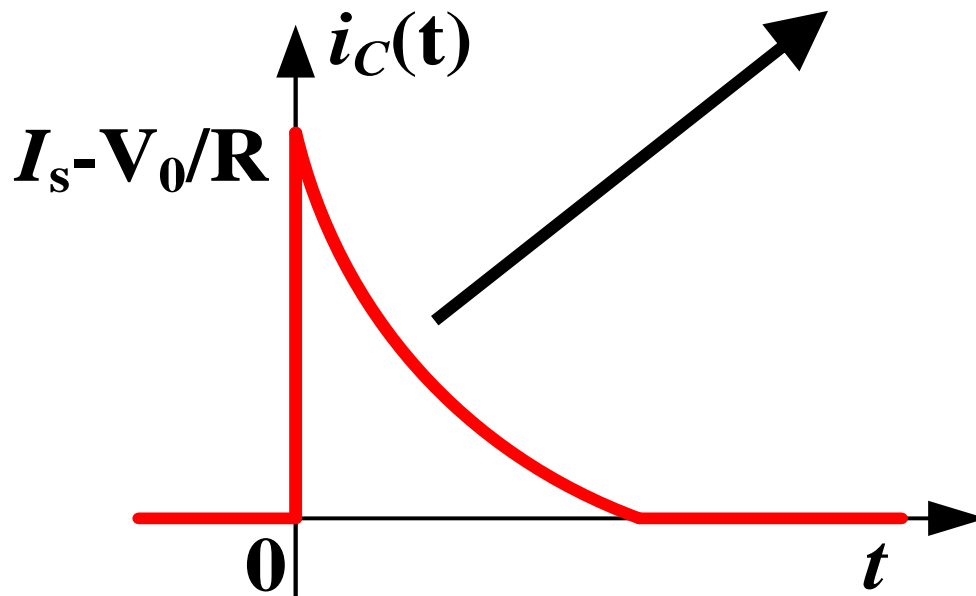
$$i_C(t) = \left(I_s - \frac{V_0}{R} \right) e^{-t/RC}, \quad t \geq 0^+$$




Step Response of RL Circuits

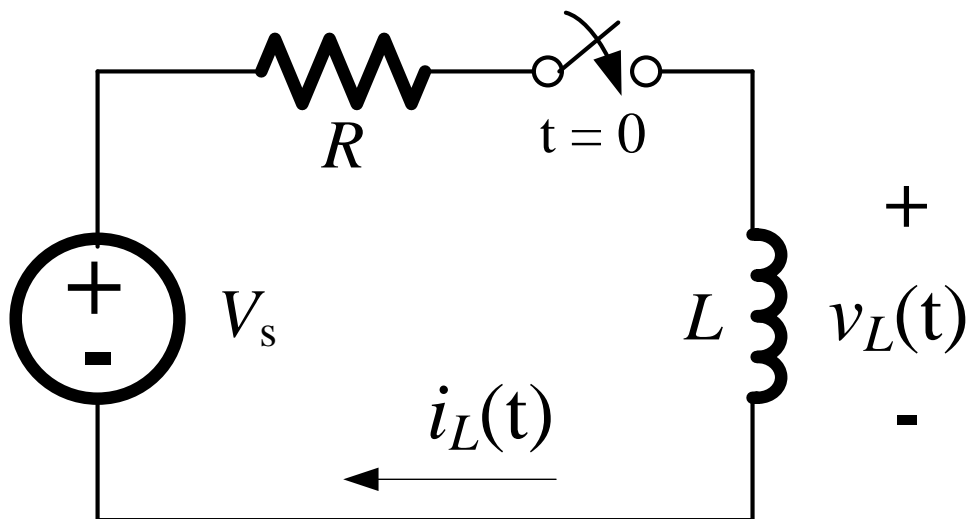

$$i_L(0^-) = I_0$$

- The switch is closed at $t = 0$;
- The inductor has a initial current I_0 ;
- Energy is being stored in the inductor.

Step Response of RL Circuits

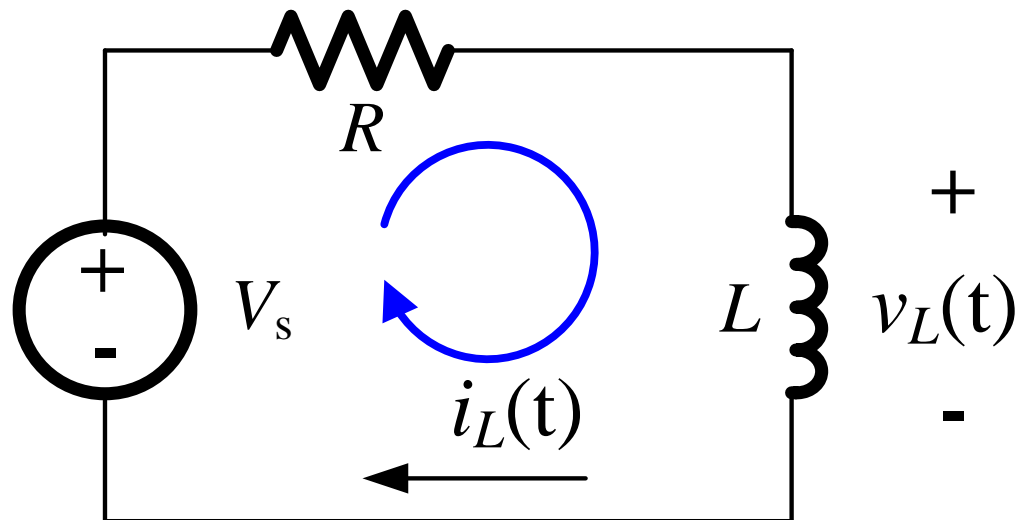

■ By KVL for the loop:
$$L \frac{di_L}{dt} + Ri_L = V_s$$



Step Response of RL Circuits

$$i_L(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-(R/L)t}, \quad t \geq 0$$

$$v_L(t) = L \frac{di_L(t)}{dt} = (V_s - RI_0) e^{-(R/L)t}, \quad t \geq 0^+$$

Time Constant: $\tau = \frac{L}{R}$



6-5 General Solution Method

- **General Solution Method for Natural and Step Response**
- **Sequential Switching**



General Solution Method

$$C \frac{dv_C}{dt} + \frac{v_C}{R} = 0 \quad \longrightarrow \quad \frac{dv_C}{dt} + \frac{v_C}{\tau} = 0$$

$$\tau = RC$$

$$L \frac{di_L}{dt} + Ri_L = 0 \quad \longrightarrow \quad \frac{di_L}{dt} + \frac{i_L}{\tau} = 0$$

$$\tau = L/R$$



General Solution Method

$$C \frac{dv_C}{dt} + \frac{v_C}{R} = I_s \quad \longrightarrow \quad \frac{dv_C}{dt} + \frac{v_C}{\tau} = \frac{I_s}{C}$$

$$\tau = RC$$

$$L \frac{di_L}{dt} + Ri_L = V_s \quad \longrightarrow \quad \frac{di_L}{dt} + \frac{i_L}{\tau} = \frac{V_s}{L}$$

$$\tau = L/R$$



General Solution Method

Natural

$$v_C(t) = v(0)e^{-t/\tau}, \quad t \geq 0$$

Response:

$$i_L(t) = i(0)e^{-t/\tau}, \quad t \geq 0$$

Step

$$v_C(t) = I_s R + (V_0 - I_s R)e^{-t/\tau}, \quad t \geq 0$$

Response:

$$i_L(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau}, \quad t \geq 0$$



General Solution Method

- Generally, response of first-order RC and RL circuit can be written as:

$$y(t) = y(+\infty) + \left[y(t_0^+) - y(+\infty) \right] e^{-(t-t_0)/\tau}$$



t_0 : Switching time



General Solution

$$y(t) = y(+\infty) + \left[y(t_0^+) - y(+\infty) \right] e^{-(t-t_0)/\tau}$$

$y(t)$: Response of *voltage or current*

$y(t_0^+)$: Initial value of *voltage or current*

$y(+\infty)$: Final value of *voltage or current*




General Solution Method

$y(+\infty)$: Final value of *voltage or current*,
which is the value as $t \rightarrow +\infty$.

$$\tau = \begin{cases} R_{TH} C_{eq} & : \text{Time constant for RC circuits} \\ L_{eq} / R_{TH} & : \text{Time constant for RL circuits} \end{cases}$$


Example

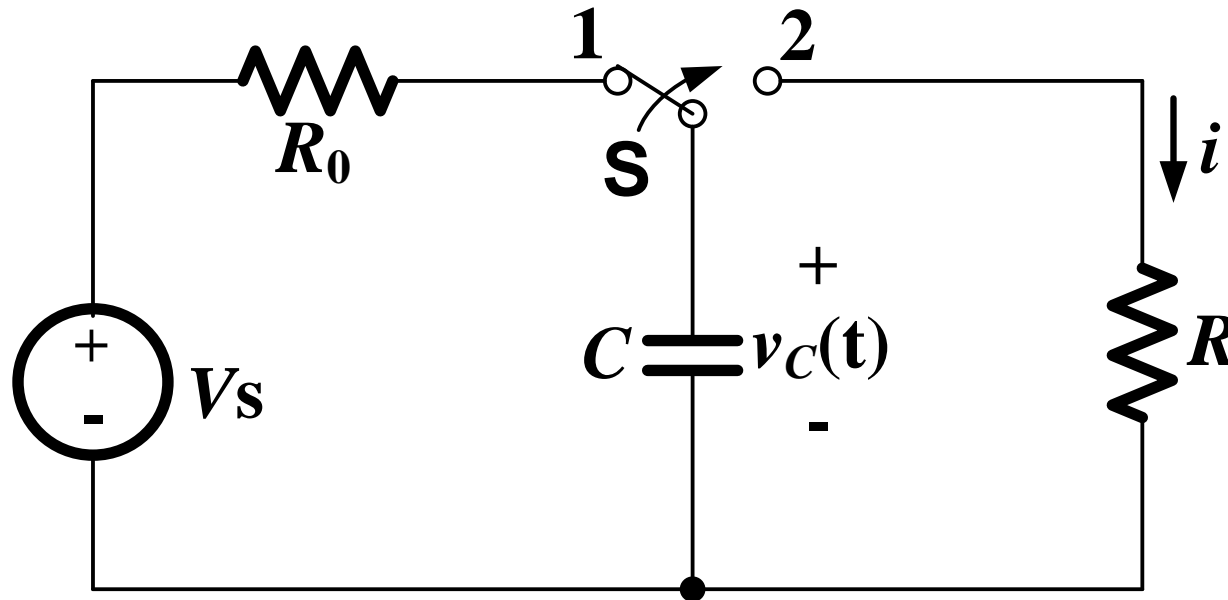

The switch has been in the position 1 for a long time, and is thrown to position 2 at $t = 0$. Find the voltage across the capacitor.

Solution:

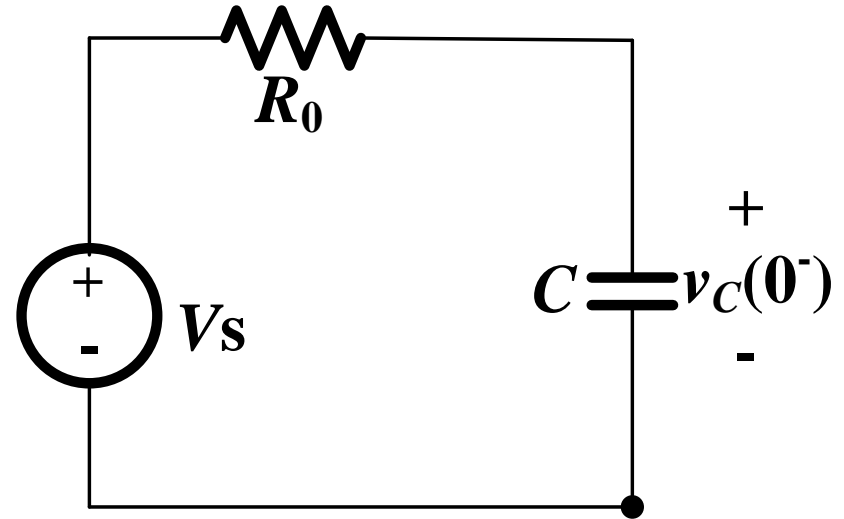At $t=0^-$, the equivalent circuit is redrawn as:



$$v_C(0^-) = V_s$$


$$v_C(0^+) = v_C(0^-) = V_s$$



At $t > 0^+$, the equivalent circuit is redrawn as:

$$v_C(+\infty) = 0$$

$$\tau = R_{TH}C = RC$$

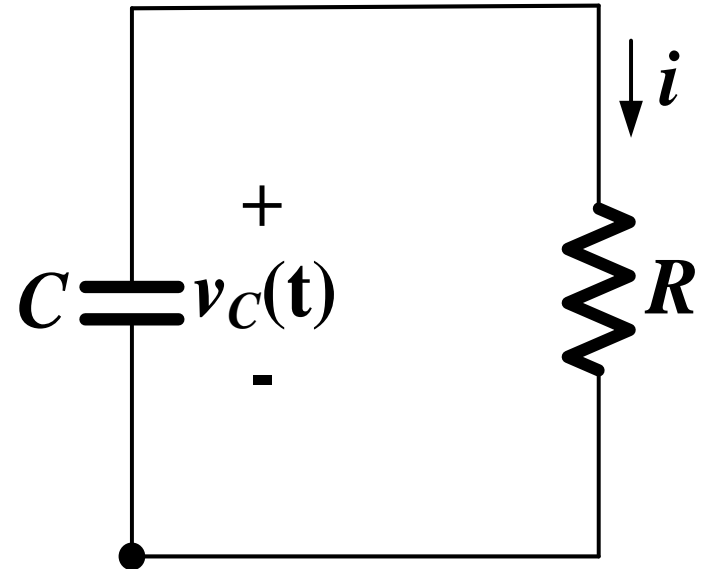




The voltage across the capacitor is:

$$\begin{aligned}v_C(t) &= v_C(+\infty) + \left[v_C(0^+) - v_C(+\infty) \right] e^{-t/\tau} \\&= 0 + [V_s - 0] e^{-t/RC} \\&= V_s e^{-t/RC}, \quad t \geq 0\end{aligned}$$

Example

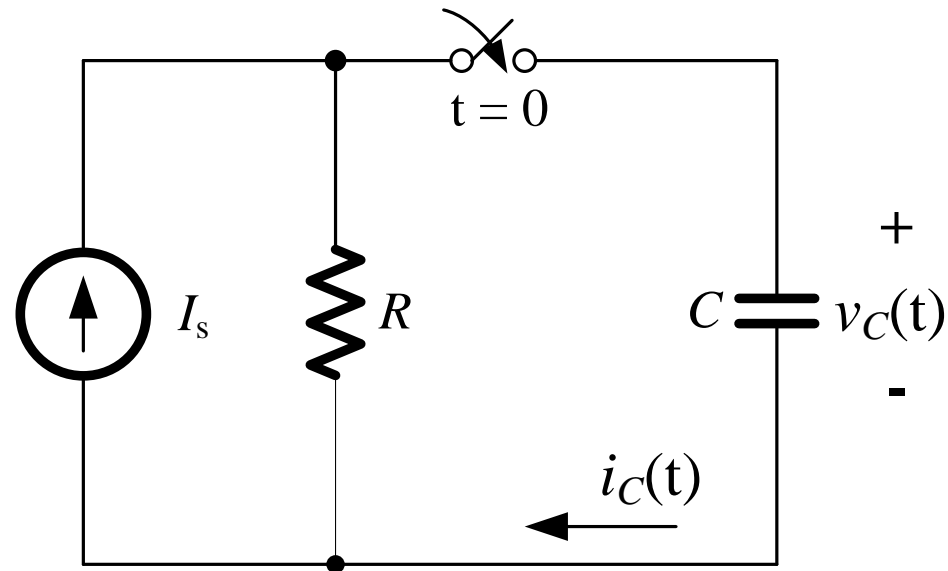

The capacitor has a initial voltage V_0 , the switch is closed at $t = 0$. Find the voltage across the capacitor.



Solution:


$$v_C(0^+) = v_C(0^-) = V_0, \quad v_C(+\infty) = RI_s$$

$$\tau = RC, \quad t_0 = 0$$

The voltage across the capacitor is:

$$\begin{aligned} v_C(t) &= v_C(+\infty) + \left[v_C(0^+) - v_C(+\infty) \right] e^{-t/\tau} \\ &= RI_s + (V_0 - RI_s) e^{-t/RC}, \quad t \geq 0 \end{aligned}$$

Example

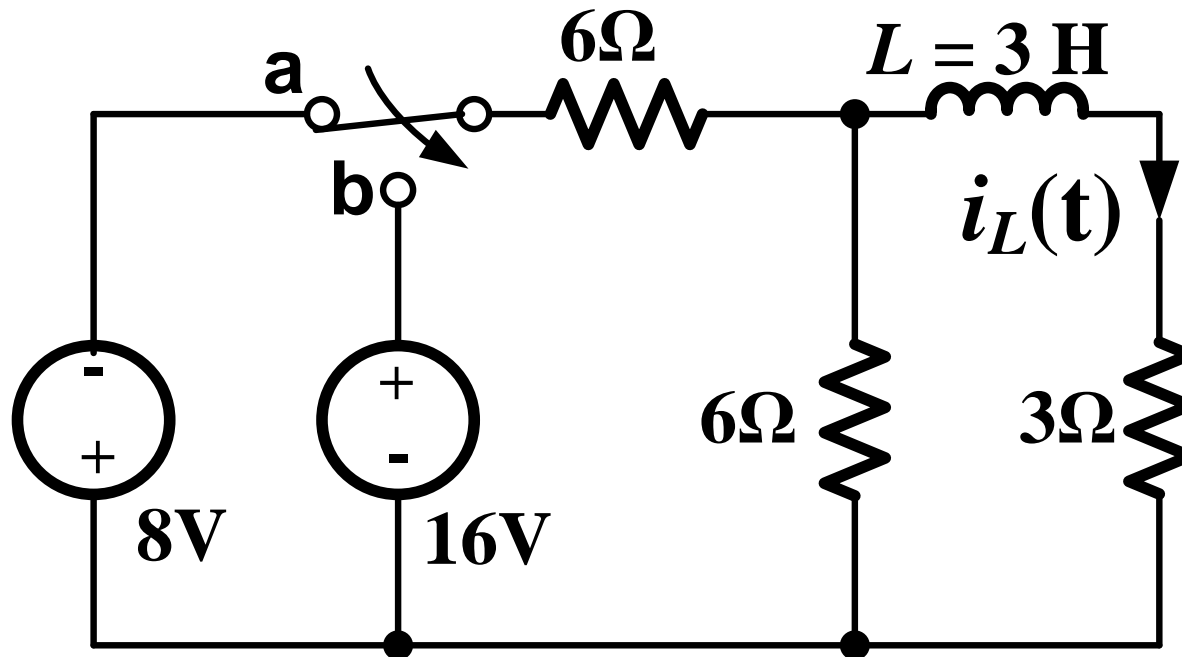


The switch is thrown from a to b at $t = 0$.
Find $i_L(t)$.

Solution:

At $t=0^-$, the equivalent circuit is redrawn as:

$$i_L(0^-) = -\frac{2}{3} \text{ A}$$

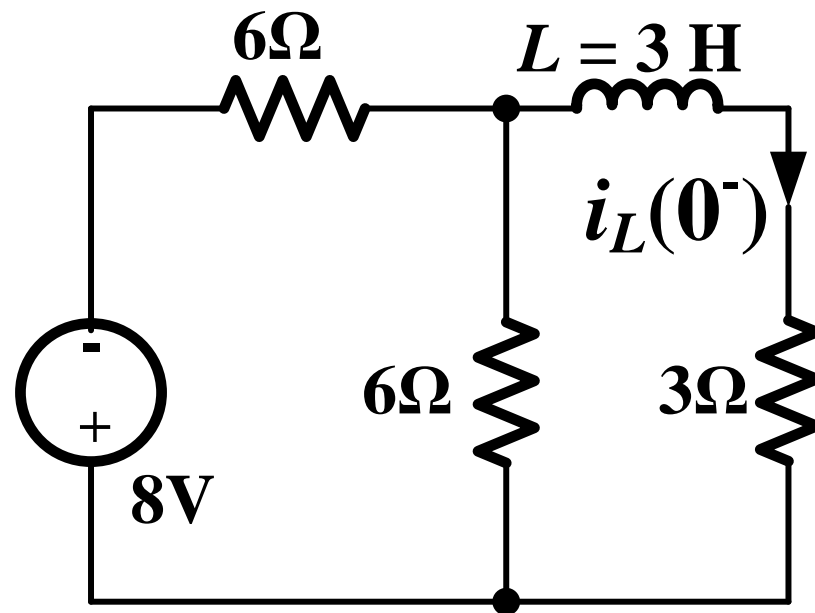
$$i_L(0^+) = i_L(0^-) = -\frac{2}{3} \text{ A}$$





At $t > 0^+$, the equivalent circuit is redrawn as:

$$i_L(+\infty) = \frac{4}{3} \text{ A}$$

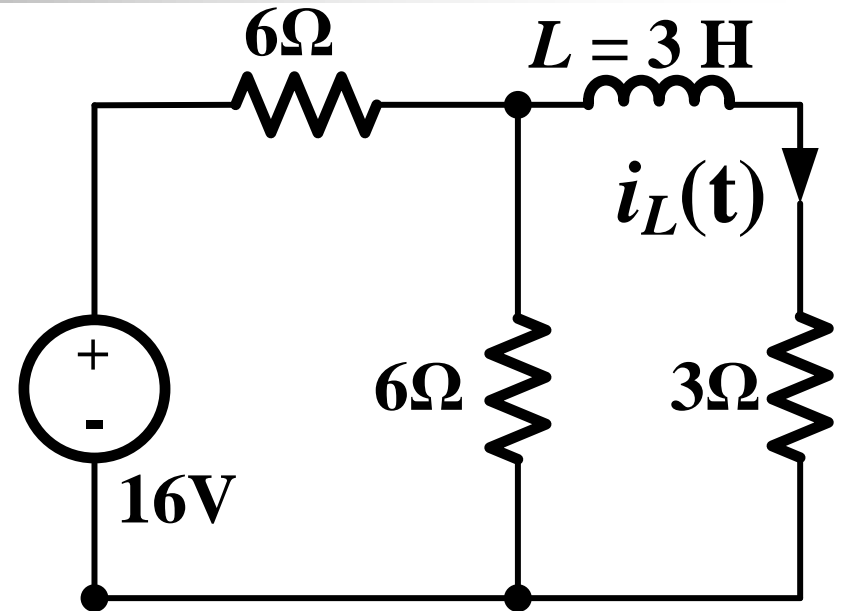

$$R_{TH} = (6\Omega \square 6\Omega) + 3\Omega = 6\Omega$$

$$\tau = L/R_{TH} = 3/6 = 0.5s$$



The current through the inductor is:


$$\begin{aligned} i_L(t) &= i_L(+\infty) + \left[i_L(0^+) - i_L(+\infty) \right] e^{-t/\tau} \\ &= \frac{4}{3} + \left(-\frac{2}{3} - \frac{4}{3} \right) e^{-t/0.5} \\ &= \frac{4}{3} - 2e^{-2t} \text{ A}, \quad t \geq 0 \end{aligned}$$



Sequential Switching

- **Switching occurs more than once in a circuit;**
- **A premium is placed on obtaining the initial values;**
- **Every time the circuit is switched, initial values should be determined for the switched circuit.**

Example

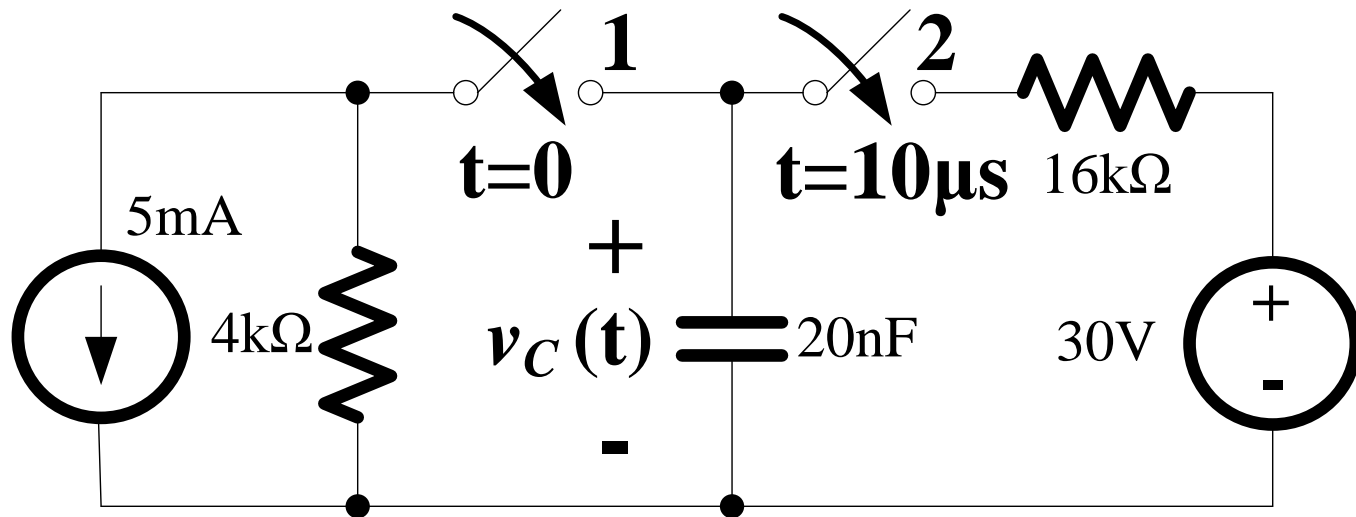

No energy stored in the capacitor when switch 1 is closed at $t = 0$. $10\mu s$ later, switch 2 is closed. Find $v_C(t)$ for $t \geq 0$.



Analysis:


- The circuit is switched two times: one is at the time $t=0$; the other is at the time $t=10\mu\text{s}$;
- At the time $t=0$, switch 1 is closed, and we obtain a circuit containing the capacitor;
- At the time $t=10\mu\text{s}$, switch 2 is closed, and we obtain a new circuit.

Solution:

At $t=0^-$, no energy is stored in the capacitor:

$$v_C(0^-) = 0, \text{ hence: } v_C(0^+) = v_C(0^-) = 0$$

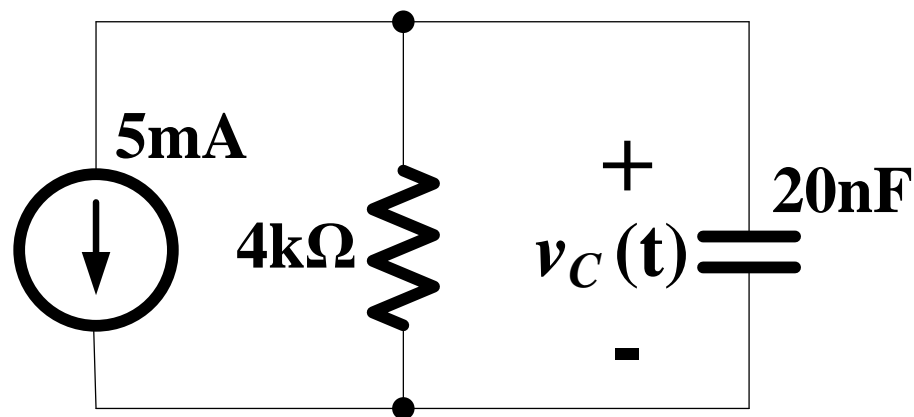At $t=0$, the switch 1 is closed. Then for the time $0^+ < t < 10\mu\text{s}$, the circuit is redrawn as:





For the capacitive voltage in such a circuit:

$$v_C(+\infty) = -20\text{V}, \quad R_{TH1} = 4\text{k}\Omega$$

$$\tau_1 = R_{TH1}C = 4\text{k}\Omega \times 20\text{nF} = 80\mu\text{s}$$

$$\begin{aligned} v_C(t) &= v_C(+\infty) + \left[v_C(0^+) - v_C(+\infty) \right] e^{-t/\tau} \\ &= -20 + \left[0 - (-20) \right] e^{-t/80} \\ &= 20 \left(e^{-t/80} - 1 \right) \text{V}, \quad (0 \leq t \leq 10\mu\text{s}) \end{aligned}$$




At the time $t=10^- \mu\text{s}$, the capacitive voltage is:


$$v_C \left(t = 10^- \mu\text{s} \right) = 20 \left(e^{-1/8} - 1 \right) \text{V}$$

At $t=10 \mu\text{s}$, the switch 2 is closed. Hence,

$$\begin{aligned} v_C \left(t = 10^+ \mu\text{s} \right) &= v_C \left(t = 10^- \mu\text{s} \right) \\ &= 20 \left(e^{-1/8} - 1 \right) \text{V} \end{aligned}$$

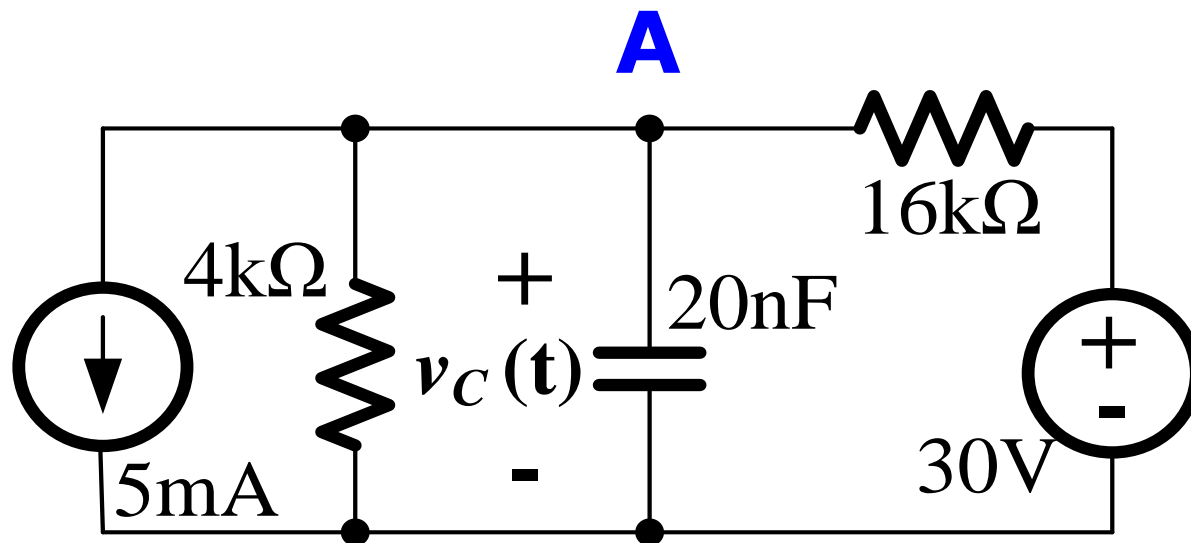Then for the time $t > 10^+ \mu\text{s}$, the circuit is redrawn as:



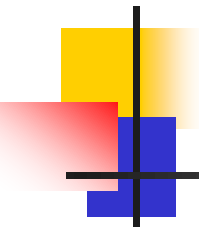

For the capacitive voltage in such a circuit:

$$v_C(+\infty) = -10V$$

$$R_{TH2} = \frac{16}{5} k\Omega$$

$$\tau_2 = R_{TH2}C = \frac{16}{5} k\Omega \times 20nF = 64\mu s$$




$$\begin{aligned}v_C(t) &= v_C(+\infty) + \left[v_C(10^+) - v_C(+\infty) \right] e^{-(t-10)/\tau} \\&= -10 + \left[20e^{-1/8} - 20 - (-10) \right] e^{-(t-10)/64} \\&= -10 + \left(20e^{-1/8} - 10 \right) e^{-(t-10)/64} \mathbf{V} \\&\quad (t \geq 10\mu s)\end{aligned}$$



Then, for $t \geq 0$, $v_C(t)$ can be expressed as:

$$v_C(t) = \begin{cases} 20(e^{-t/80} - 1) \text{ V}, & 0 \leq t \leq 10\mu\text{s} \\ -10 + (20e^{-1/8} - 10)e^{-(t-10)/64} \text{ V}, & t \geq 10\mu\text{s} \end{cases}$$

Example

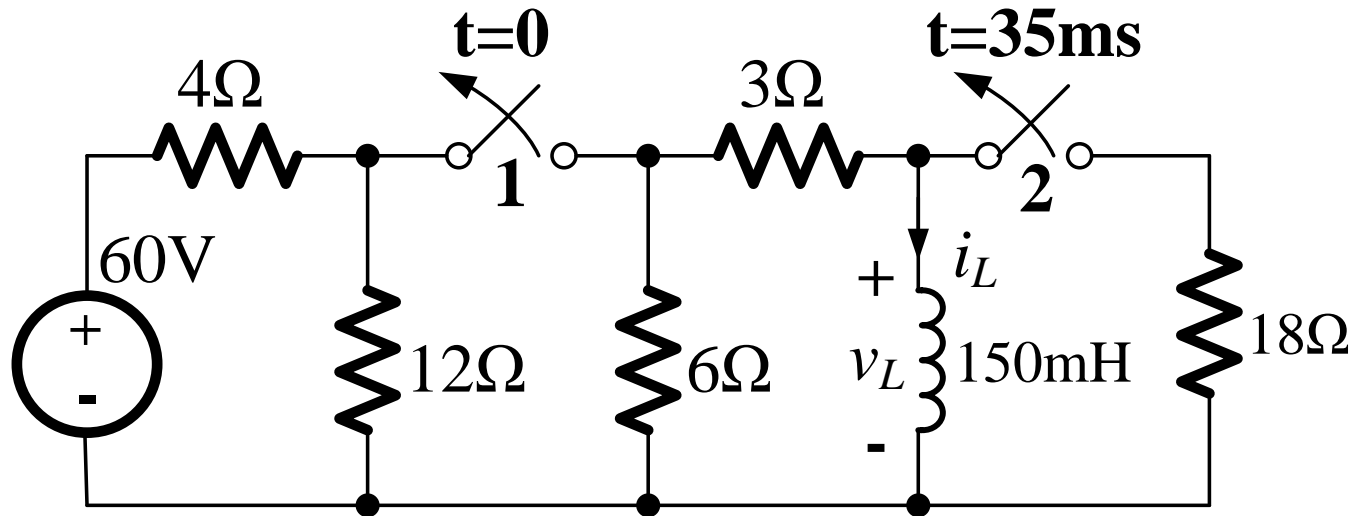


The two switches have been closed for a long time. At $t=0$, switch 1 is opened. Then 35ms later, switch 2 is opened.


1. Find $i_L(t)$ for $t \geq 0$;
2. What percentage of the initial energy stored in the inductor is dissipated in the 18Ω resistor?

Solution:

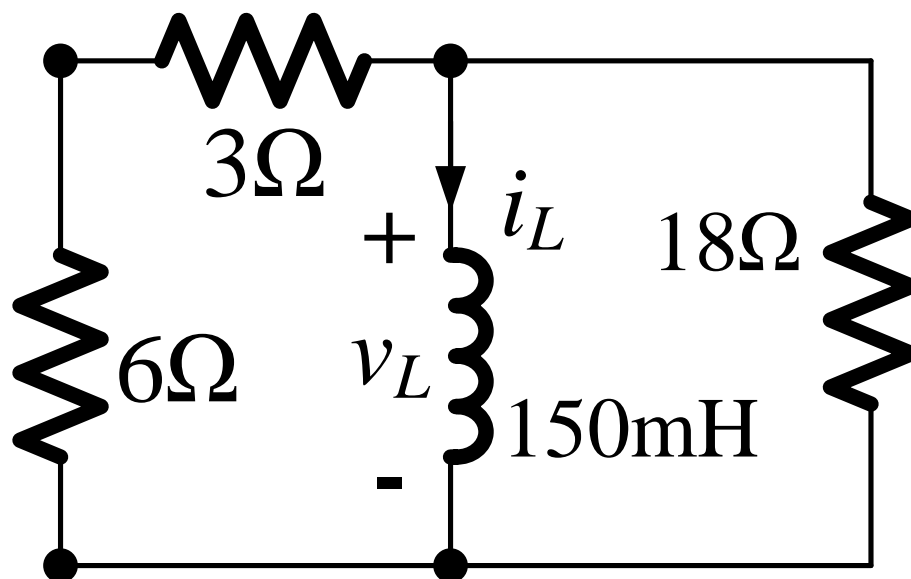1. $i_L(0^+) = i_L(0^-) = 6A$

For the time $0^+ < t < 35ms$, the circuit is redrawn as:







$$i_L(+\infty) = 0, \quad R_{TH1} = 6\Omega$$

$$\tau_1 = \frac{L}{R_{TH1}} = \frac{150\text{mH}}{6\Omega} = 25\text{ms}$$
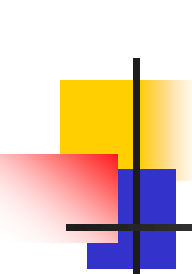
$$\begin{aligned} i_L(t) &= 6e^{-t/25\text{ms}} \\ &= 6e^{-40t} \text{ A}, \quad (0 \leq t \leq 35\text{ms}) \end{aligned}$$



$$i_L(t = 35\text{ms}) = 6e^{-1.4} = 1.48\text{A}$$

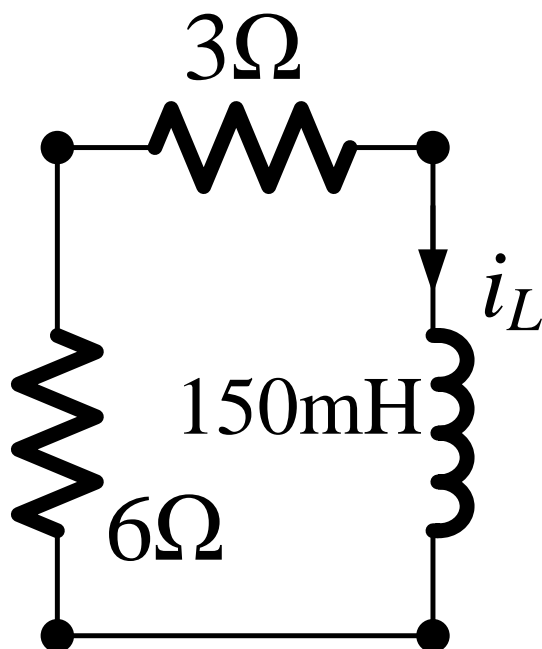For the time $t > 35\text{ms}$, the circuit is redrawn as:



$$i_L(+\infty) = 0, \quad R_{TH2} = 9\Omega$$


$$\tau_2 = \frac{L}{R_{TH2}} = \frac{150\text{mH}}{9\Omega} = \frac{50}{3}\text{ms}$$



$$i_L(t) = 1.48e^{-60(t-0.035)} \text{ A}, \quad (t \geq 35\text{ms})$$

Hence,

$$i_L(t) = \begin{cases} 6e^{-40t} \text{ A}, & (0 \leq t \leq 35\text{ms}) \\ 1.48e^{-60(t-0.035)} \text{ A}, & (t \geq 35\text{ms}) \end{cases}$$



2. The 18Ω resistor is in the circuit only during the first 35ms. During this interval, the voltage across the resistor is:

$$\begin{aligned} v_L(t) &= L \frac{dv_L(t)}{dt} = 0.15 \frac{d6e^{-40t}}{dt} \\ &= -36e^{-40t} \text{ V}, \quad (0 \leq t \leq 35\text{ms}) \end{aligned}$$



The power dissipated in 18Ω resistor is:

$$p = \frac{v_L^2}{18} = 72e^{-80t} \text{ W}, \quad (0 \leq t \leq 35\text{ms})$$

The energy dissipated in 18Ω resistor is:

$$w = \int_0^{0.035} 72e^{-80t} dt = -\frac{72}{80} e^{-80t} \bigg|_0^{0.035} = 845.27 \text{ mJ}$$



The initial energy stored in the inductor is:

$$w_i = \frac{1}{2} L i_L^2(0^-) = \frac{1}{2} \times 0.15 \times 6^2 = 2.7\text{J}$$

$$\frac{w}{w_i} = \frac{845.27\text{mJ}}{2.7\text{J}} \approx 31.31\%$$


Therefore, 31.31% of the initial energy stored in the inductor is dissipated in the 18Ω resistor.



6-6 Integrating Amplifier

- Integrating amplifier can generate an output voltage proportional to the integral of the input voltage;
- Generally, it contains a capacitor and an operational amplifier.

Example

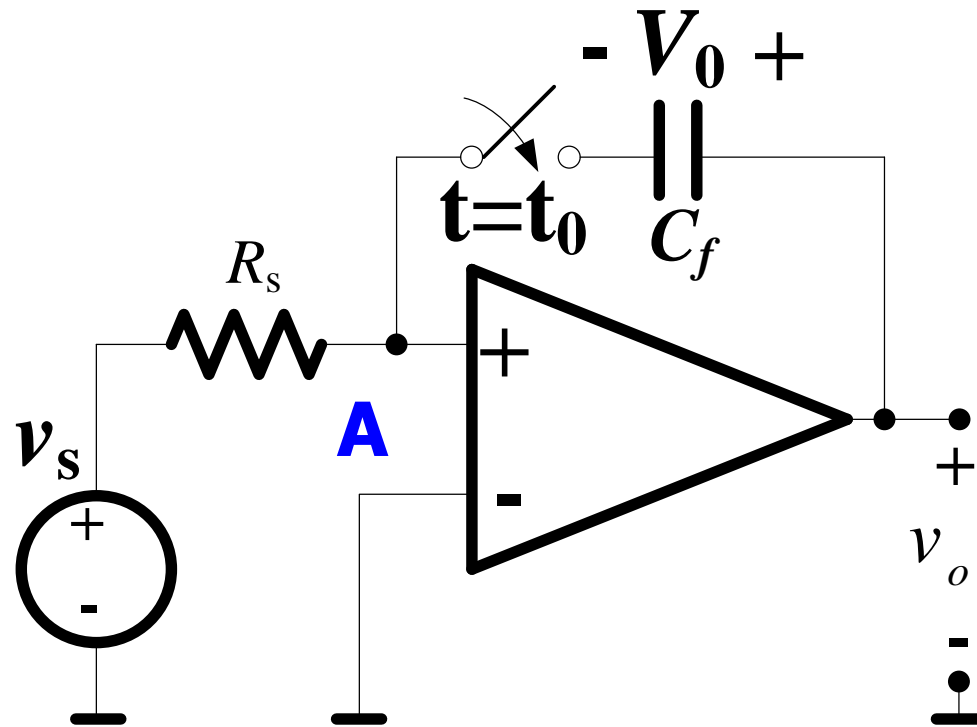

The initial voltage across the capacitor is V_0 .

The switch is closed at $t = t_0$. Express v_o by v_s .




Solution:

For node A, by KCL:

$$C_f \frac{dv_o}{dt} + \frac{v_s}{R_s} = 0 \quad v_o(t_0^+) = v_o(t_0^-) = V_0$$

$$v_o(t) = -\frac{1}{R_s C_f} \int_{t_0}^t v_s dt + V_0, \quad t \geq t_0$$

- 
- Specially, if $t_0 = 0$, and $V_0 = 0$, we have:

$$v_o(t) = -\frac{1}{R_s C_f} \int_0^t v_s dt$$

- Output voltage is an inverted, scaled replica of the integral of the input voltage.



Summary of Chapter 6

- Conception of **First-order RC** and **RL** circuits
- **Initial values** of circuits
- **Natural response** and **step response**
- Conception of **time constant**
- **General solution method** for natural and step responses for first-order RC and RL circuits
- **Responses for sequential switching** circuits