



Introduction to Electronic Systems

Zheng Feng



Part 3: Sinusoidal Steady-State Analysis

8. Sinusoidal Steady-State Analysis

9. Sinusoidal Steady-State Power Calculations


10. Frequency Selective Circuits *



Chapter 9

- **Instantaneous Power**
- **Average Power**
- **RMS and Effective Value**
- **Complex Power and Apparent Power**
- **Maximum Average Power Transfer**

9-1 Instantaneous Power

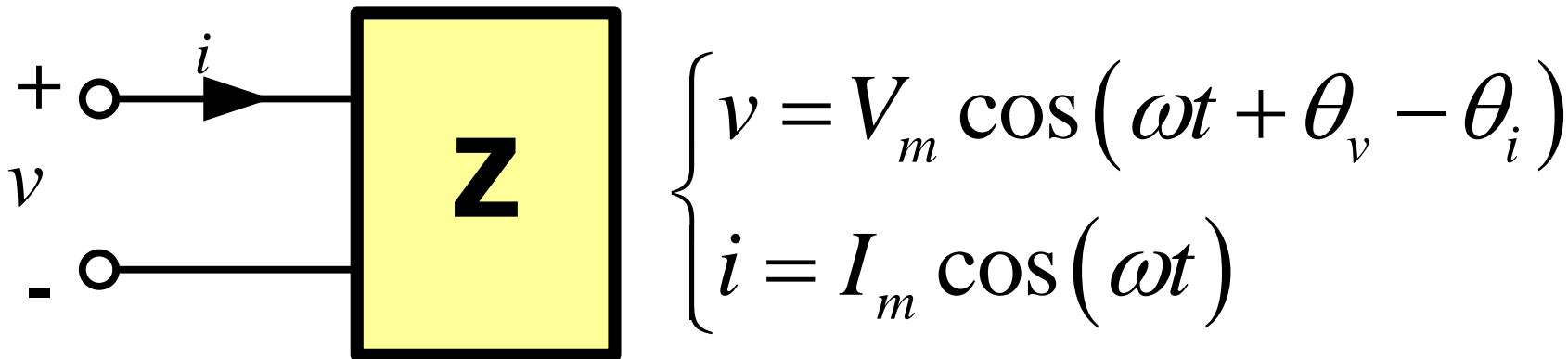

■ Instantaneous Power:


$$\begin{aligned} p &= vi = V_m \cos(\omega t + \theta_v - \theta_i) \cdot I_m \cos(\omega t) \\ &= V_m I_m \cos(\omega t + \theta_v - \theta_i) \cos(\omega t) \end{aligned}$$



Instantaneous Power

$$\begin{aligned} p = vi &= V_m I_m \cos(\omega t + \theta_v - \theta_i) \cos(\omega t) \\ &= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v - \theta_i) \\ &= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \\ &\quad + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos(2\omega t) - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin(2\omega t) \end{aligned}$$

9-2 Average and Reactive Power

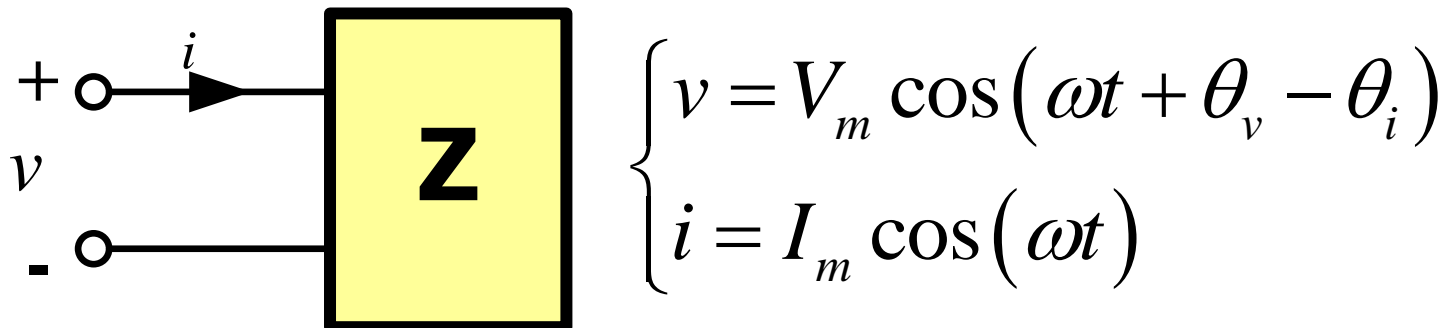

$$p = vi$$

$$= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$+ \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos(2\omega t) - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin(2\omega t)$$

$$= P + P \cos(2\omega t) - Q \sin(2\omega t)$$



Average Power

$$p = P + P \cos(2\omega t) - Q \sin(2\omega t)$$

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p dt = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

- P is defined as Average Power;
- P is also called Real Power, or Active Power;
- The unit for Average Power is Watt (W).



Reactive Power

$$p = P + P \cos(2\omega t) - Q \sin(2\omega t)$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

- Q is defined as Reactive Power;
- The unit for Reactive Power is VAR (*Volt-Amp Reactive*).



Power Factor


$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{V_m I_m}{2} \cos \phi$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = \frac{V_m I_m}{2} \sin \phi$$

$$\phi = \theta_v - \theta_i$$

: is defined as Power Factor Angle.

Example

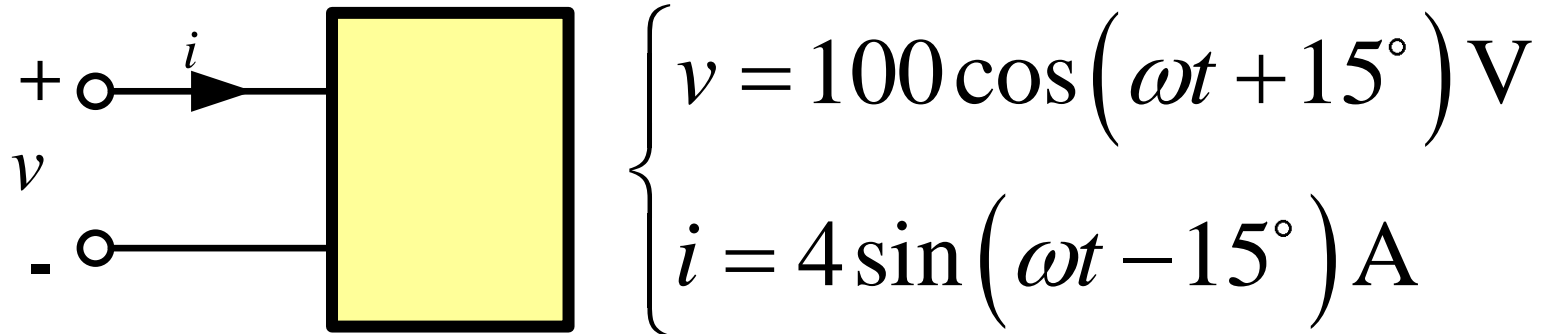

Calculate the average power and the reactive power at the terminals of the network shown above.



Solution:

$$\begin{cases} v = 100 \cos(\omega t + 15^\circ) \text{ V} \\ i = 4 \sin(\omega t - 15^\circ) = 4 \cos(\omega t - 105^\circ) \text{ A} \end{cases}$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{100 \times 4}{2} \times \cos[15^\circ - (-105^\circ)] = -100 \text{ W}$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = \frac{100 \times 4}{2} \sin[15^\circ - (-105^\circ)] = 173.21 \text{ VAR}$$



9-3 rms and Effective Value

rms value:

ROOT of the **MEAN** value of the **SQUARED** function


$$v(t) = V_m \cos(\omega t + \phi)$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v^2 dt} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt} = \frac{V_m}{\sqrt{2}}$$

Effective Value


- For the Sinusoidal voltage/current source, the **rms value** is also referred to as the **Effective Value**.

$$v(t) = V_m \cos(\omega t + \theta_v)$$

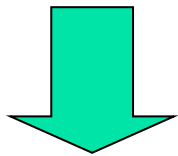

$$V_{eff} = \frac{V_m}{\sqrt{2}} = 0.707V_m$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

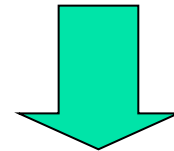

$$I_{eff} = \frac{I_m}{\sqrt{2}} = 0.707I_m$$



Effective Value and Power

■ Average power:

$$\begin{aligned} P &= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \\ &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) \\ &= V_{eff} I_{eff} \cos(\theta_v - \theta_i) \end{aligned}$$

■ Reactive power:


$$\begin{aligned} Q &= \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \\ &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \sin(\theta_v - \theta_i) \\ &= V_{eff} I_{eff} \sin(\theta_v - \theta_i) \end{aligned}$$



9-4 Complex Power and Apparent Power

$\hat{S} = P + jQ$: is defined as **Complex Power**.

- The unit for Complex Power is VA (*Volt-Amp*).
- The unit for Average Power is Watt;
- The unit for Reactive Power is VAR.

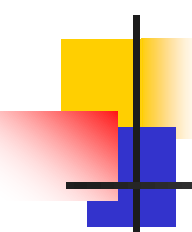
$$\hat{S} = P + jQ$$

Average Power: $P = \frac{V_m I_m}{2} \cos \phi = \text{Re}[\hat{S}]$

Reactive Power: $Q = \frac{V_m I_m}{2} \sin \phi = \text{Im}[\hat{S}]$

$$|\hat{S}| = \sqrt{P^2 + Q^2}, \quad \phi = \arctan \frac{Q}{P}$$



Complex Power Calculation

$$\hat{S} = P + jQ$$


$$= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + j \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$= \frac{V_m I_m}{2} [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$

$$= \frac{V_m I_m}{2} e^{j(\theta_v - \theta_i)} = \frac{1}{2} V_m e^{j\theta_v} I_m e^{-j\theta_i} = \frac{1}{2} \hat{V} \hat{I}^*$$



Complex Power Calculation

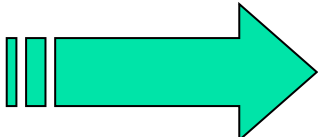
$$\hat{S} = P + jQ = \frac{1}{2} \hat{V} \hat{I}^*$$

$$\hat{S} = \frac{1}{2} \hat{V} \hat{I}^* = \frac{1}{2} (Z \hat{I}) \hat{I}^* = \frac{1}{2} Z |\hat{I}|^2 = \frac{1}{2} Z I_m^2$$



Apparent Power

$|\hat{S}| = \sqrt{P^2 + Q^2}$: is defined as Apparent Power.


- The unit for Apparent Power is VA (Volt-Amp);
- The unit for Average Power is Watt;
- The unit for Reactive Power is VAR.
- The unit for Complex Power is VA (*Volt-Amp*);

Apparent Power

$$P = \frac{V_m I_m}{2} \cos \phi, \quad Q = \frac{V_m I_m}{2} \sin \phi$$


$$|\hat{S}| = \sqrt{P^2 + Q^2} = \frac{1}{2} V_m I_m$$

$$\phi = \arctan \frac{Q}{P}$$

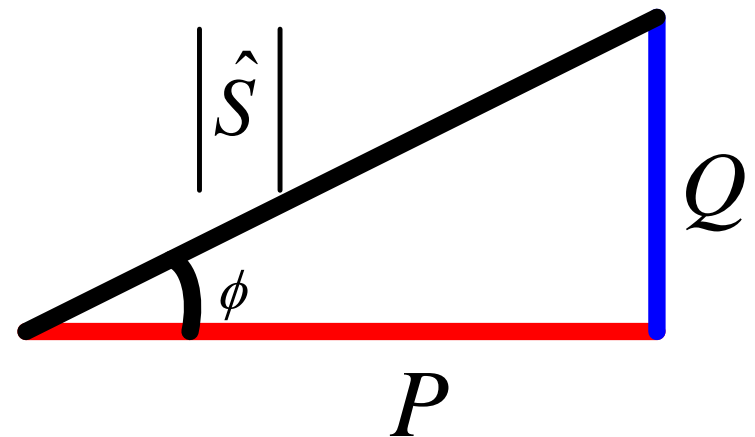

Power Triangle


Power for Resistive Circuits

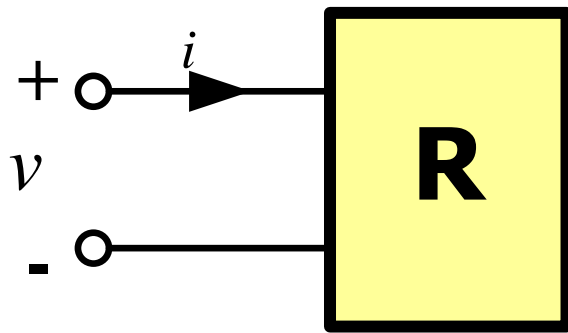

$$\begin{cases} \hat{I} = I_m e^{j\theta_i} \\ \hat{V} = R\hat{I} = RI_m e^{j\theta_i} \end{cases}$$


■ Complex Power:

$$\begin{aligned} \hat{S} &= \frac{1}{2} \hat{V} \hat{I}^* = \frac{1}{2} \hat{V} \left(\frac{\hat{V}^*}{R} \right) = \frac{V_m^2}{2R} \\ &= \frac{1}{2} R \hat{I} \hat{I}^* = \frac{1}{2} R |\hat{I}|^2 = \frac{1}{2} R I_m^2 \end{aligned}$$

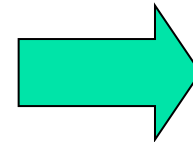

$$\begin{cases} P = \frac{V_m^2}{2R} = \frac{1}{2} R I_m^2 \\ Q = 0 \\ \phi = 0 \end{cases}$$


Power for Inductive Circuits

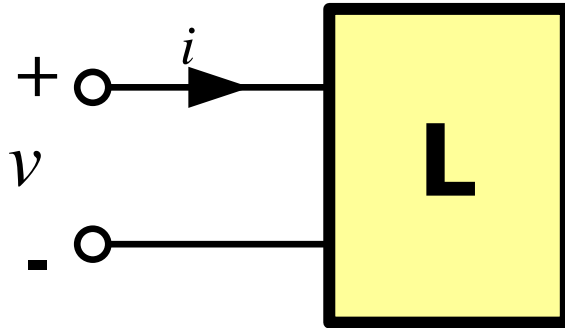


$$\begin{cases} \hat{I} = I_m e^{j\theta_i} \\ \hat{V} = Z\hat{I} = j\omega L\hat{I} \end{cases}$$

■ Complex Power:

$$\begin{aligned} \hat{S} &= \frac{1}{2} \hat{V} \hat{I}^* = \frac{1}{2} j\omega L \hat{I} \hat{I}^* \\ &= j \frac{1}{2} \omega L I_m^2 \end{aligned}$$

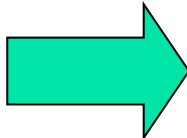
$$\begin{cases} P = 0 \\ Q = \frac{1}{2} \omega L I_m^2 \\ \phi = 90^\circ \end{cases}$$


Power for Capacitive Circuits

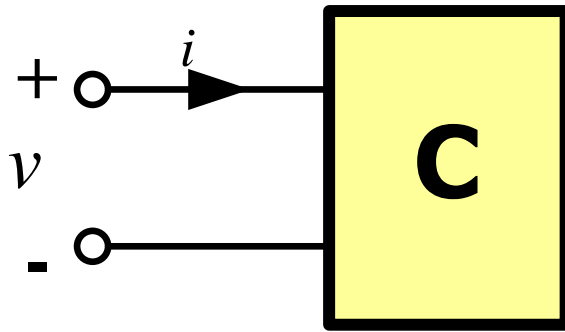

$$\begin{cases} \hat{I} = I_m e^{j\theta_i} \\ \hat{V} = Z\hat{I} = \frac{1}{j\omega C} \hat{I} \end{cases}$$

■ Complex Power:


$$\begin{aligned} \hat{S} &= \frac{1}{2} \hat{V} \hat{I}^* = \frac{1}{2} \frac{1}{j\omega C} \hat{I} \hat{I}^* \\ &= -j \frac{I_m^2}{2\omega C} \end{aligned}$$

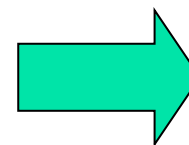
$$\begin{cases} P = 0 \\ Q = -\frac{I_m^2}{2\omega C} \\ \phi = -90^\circ \end{cases}$$



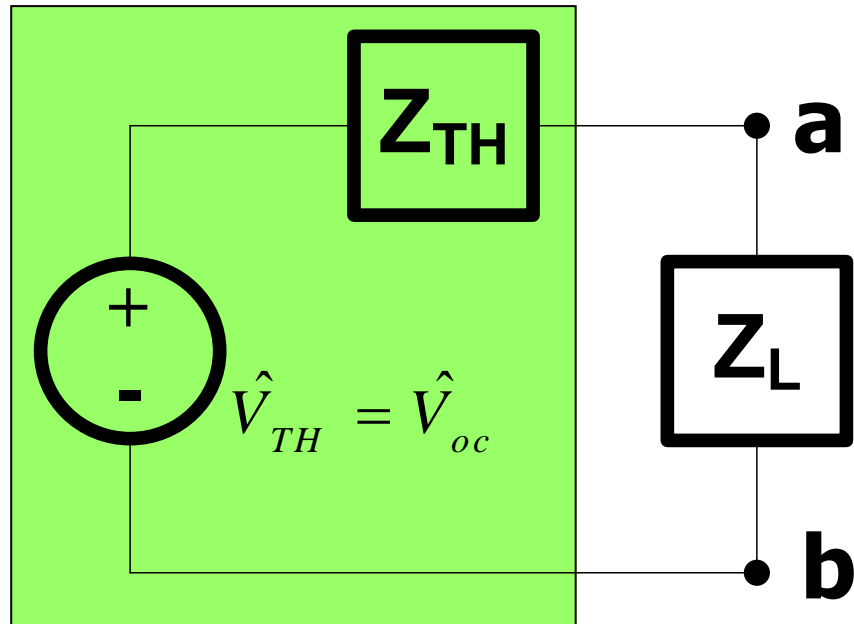
9-5 Maximum Average Power Transfer

- Any linear network may be viewed from the terminals of the load in terms of **Thévenin equivalents**;
- What is the load impedance required to deliver maximum **average power** to the load?
- What is the maximum average power?



$$Z_L = R_L + jX_L$$


Maximum Power Transfer

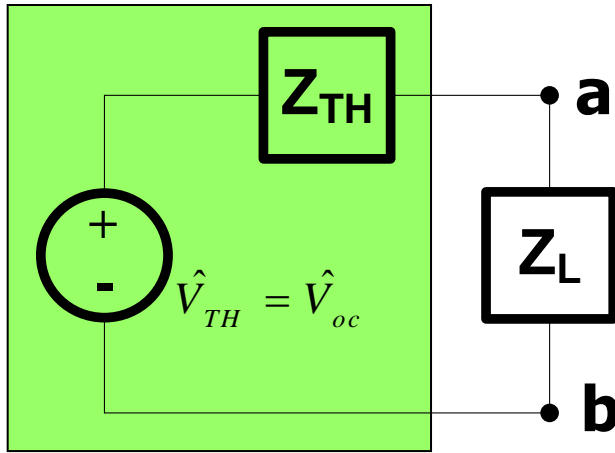



$$\begin{cases} Z_{TH} = R_{TH} + jX_{TH} \\ Z_L = R_L + jX_L \end{cases}$$

■ Complex Power:

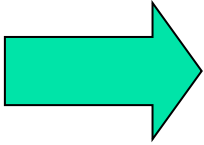
$$\begin{aligned} \hat{S} &= \frac{1}{2} \hat{V} \hat{I}^* = \frac{1}{2} Z_L \hat{I} \hat{I}^* = \frac{1}{2} Z_L |\hat{I}|^2 \\ &= \frac{1}{2} |\hat{I}|^2 (R_L + jX_L) \end{aligned}$$


$$P = \frac{1}{2} |\hat{I}|^2 R_L$$



$$\begin{aligned} P &= \frac{1}{2} |\hat{I}|^2 R_L = \frac{1}{2} \left| \frac{\hat{V}_{TH}}{Z_L + Z_{TH}} \right|^2 R_L \\ &= \frac{1}{2} \left| \frac{\hat{V}_{TH}}{(R_L + R_{TH}) + j(X_L + X_{TH})} \right|^2 R_L \\ &= \frac{1}{2} \frac{|\hat{V}_{TH}|^2 R_L}{(R_L + R_{TH})^2 + (X_L + X_{TH})^2} \end{aligned}$$



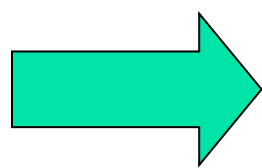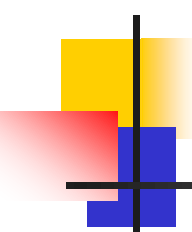
Let:
$$\begin{cases} \frac{\partial P}{\partial X_L} = 0 \\ \frac{\partial P}{\partial R_L} = 0 \end{cases} \quad \Rightarrow \quad \begin{cases} X_L = -X_{TH} \\ R_L = R_{TH} \end{cases}$$




$$Z_L = Z_{TH}^*$$


$$P_{\max} = \frac{1}{2} \frac{|\hat{V}_{TH}|^2 R_L}{(R_L + R_{TH})^2 + (R_{TH} + X_{TH})^2}$$
$$= \frac{1}{2} \frac{|\hat{V}_{TH}|^2 R_L}{(R_L + R_L)^2} = \frac{|\hat{V}_{TH}|^2}{8R_L}$$


$$P_{L\max} = \frac{|\hat{V}_{TH}|^2}{8R_L}$$


Example

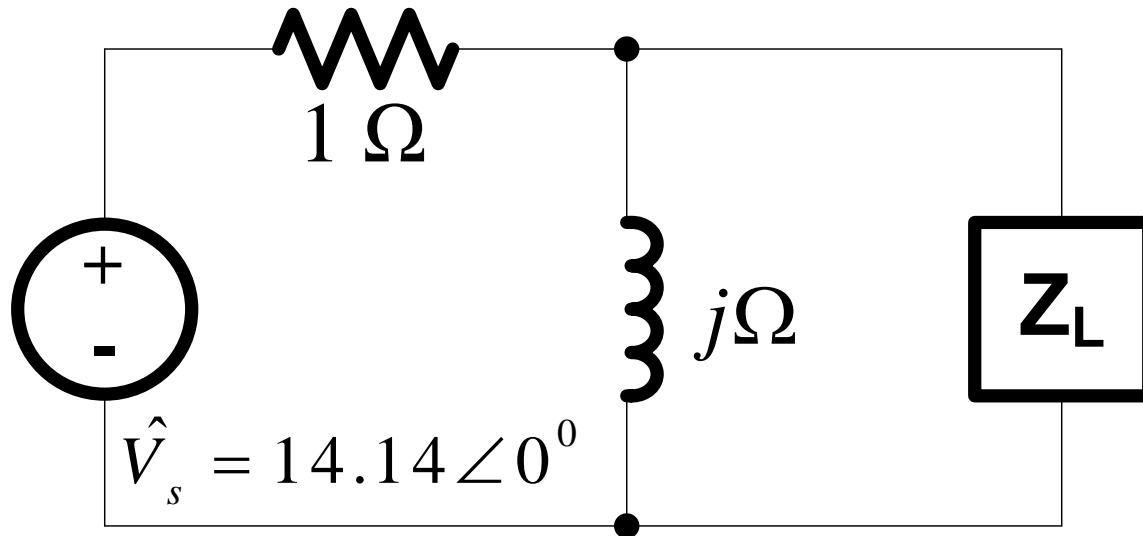

For the circuit shown, what value of Z_L results in maximum average power transferred to Z_L ? What is the maximum power?


Solution:

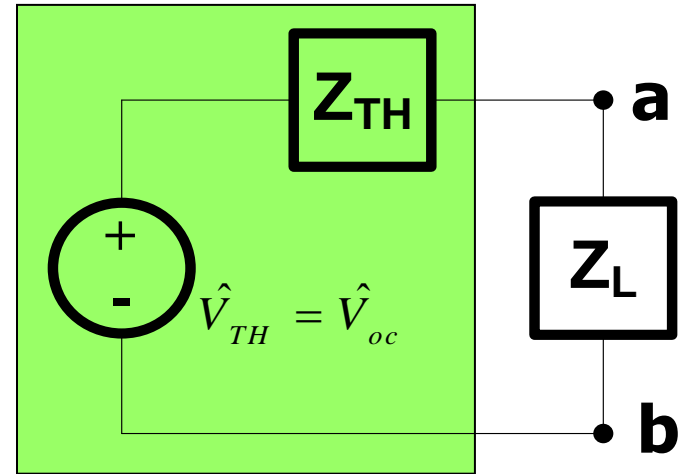The Thévenin equivalent with respect to the two terminals of the load is:



$$\hat{V}_{Th} = \hat{V}_{oc} = \frac{j}{1+j} 14.14 \angle 0^\circ \text{ V} = 10 \angle 45^\circ \text{ V}$$

$$Z_{Th} = \frac{j}{1+j} = \frac{1}{\sqrt{2}} \angle 45^\circ \Omega = (0.5 + j0.5) \Omega$$



$$Z_L = Z_{Th}^* = (0.5 - j0.5)\Omega$$

Hence, $Z_L = (0.5 - j0.5)\Omega$ can result in maximum average power transferred to Z_L . The maximum power is:

$$P_{L\max} = \frac{|\hat{V}_{Th}|^2}{8R_L} = \frac{|10\angle 45^\circ|^2}{8 \times 0.5} = 25\text{W}$$



Summary of Chapter 9

- **Definitions of instantaneous powers, average power, complex power, and apparent power**
- **Sinusoidal steady-state power calculation**
- **Maximum average power transfer**